

# Computer Architectures

## Lab Report 2

DATAPATH DESIGN

Y3839090 & Y3840426 | Computer Architectures | ELE000091

# ALL DataPaths

## ALUParam.vhd (From Lab 1)(Used for All DataPaths)

```
-----
--
-- Uni          :          University of York
-- Course       :          Electronic Engineering
-- Module       :          Computer Architectures
-- Engineers    :          Y3839090 & Y3840426
--
-- Create Date  :          13:19:20 02/17/2017
-- Design Name  :          ALU_param - Behavioral
-- Description   :          A paramateriable integer ALU.
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.DigEng.ALL;

entity ALU_param is
  Generic (
    N : natural := 8 -- data size in bits
  );
  Port (
    A : in  STD_LOGIC_VECTOR (N-1 downto 0);
    B : in  STD_LOGIC_VECTOR (N-1 downto 0);
    X : in  STD_LOGIC_VECTOR (log2(N)-1 downto 0); -- shift/rotate amount input
    ctrl : in STD_LOGIC_VECTOR (3 downto 0); -- control signals from opcode
    O : out STD_LOGIC_VECTOR (N-1 downto 0);
    flags : out STD_LOGIC_VECTOR (7 downto 0) -- flags
  );
end ALU_param;

architecture Behavioral of ALU_param is

  -- internal signed signal for A and B inpy=uts
  signal A_itrn : SIGNED (N-1 downto 0);
  signal B_itrn : SIGNED (N-1 downto 0);

  -- internal integer for X
  signal X_itrn : integer;

  -- internal signed signal for output
  signal O_itrn : SIGNED (N-1 downto 0);

  -- max positive and negative N bit signed numbers
  constant max_pos : SIGNED (N-1 downto 0) := to_signed(( 2 ** (N-1) ) - 1, N);
  constant max_neg : SIGNED (N-1 downto 0) := to_signed( -2 ** (N-1) , N);

begin

  A_itrn <= signed(A); -- converts A to signed and maps the result to A_itrn
  B_itrn <= signed(B); -- converts A to signed and maps the result to B_itrn

  -- converts X to integer and maps the result to X_itrn
  X_itrn <= to_integer(unsigned(X));

  -- converts O_itrn to a plain std_logic_vector and maps it to O
  O <= std_logic_vector(O_itrn);

  -- Main ALU multiplexer for each possible command
  O_itrn <=
    A_itrn
    when ctrl = "0000" else
    A_itrn and B_itrn
    when ctrl = "0100" else
    A_itrn or B_itrn
    when ctrl = "0101" else
    A_itrn xor B_itrn
    when ctrl = "0110" else
    not A_itrn
    when ctrl = "0111" else
    A_itrn + 1
    when ctrl = "1000" else
    A_itrn - 1
    when ctrl = "1001" else
    A_itrn + B_itrn
    when ctrl = "1010" else
    A_itrn - B_itrn
    when ctrl = "1011" else
    SHIFT_LEFT (A_itrn , X_itrn)
    when ctrl = "1100" else -- Output A sla X
    SHIFT_RIGHT (A_itrn , X_itrn)
    when ctrl = "1101" else -- Output A sra X
    ROTATE_LEFT (A_itrn , X_itrn)
    when ctrl = "1110" else -- Output A rotl X
    ROTATE_RIGHT (A_itrn , X_itrn)
    when ctrl = "1111" else -- Output A rotr X
    (others => 'U');
```

## (Continued.)

```
-- Overflow flag
flags(7) <=
    -- Will overflow if you add one to the max positive value
    '1' when ctrl = "1000" and A_itrn = max_pos else

    -- Will overflow if you minus one to the max negative value
    '1' when ctrl = "1001" and A_itrn = max_neg else

    -- Will overflow if two neg values added give a pos result
    '1' when ctrl = "1010" and A_itrn(N-1) = '1' and B_itrn(N-1) = '1' and O_itrn(N-1) = '0' else
    -- Will overflow if two pos values added give a neg result
    '1' when ctrl = "1010" and A_itrn(N-1) = '0' and B_itrn(N-1) = '0' and O_itrn(N-1) = '1' else

    -- Will overflow if a pos value is subtracted from a neg value gives a pos result
    '1' when ctrl = "1011" and A_itrn(N-1) = '1' and B_itrn(N-1) = '0' and O_itrn(N-1) = '0' else
    -- Will overflow if a neg value is subtracted from a pos value gives a neg result
    '1' when ctrl = "1011" and A_itrn(N-1) = '0' and B_itrn(N-1) = '1' and O_itrn(N-1) = '1'

    -- If none of the above are true then the result hasn't overflowed
    else '0';

-- Other flags
flags(6) <= '1'          when O_itrn >= 0          else '0'; -- grater than or equal to zero
flags(5) <= '1'          when O_itrn <= 0          else '0'; -- less than or equal to zero
flags(4) <= '1'          when O_itrn > 0           else '0'; -- grater than zero
flags(3) <= '1'          when O_itrn < 0           else '0'; -- less than zero
flags(2) <= '1'          when O_itrn = 1           else '0'; -- one flag
flags(1) <= '1'          when O_itrn /= 0          else '0'; -- not zero flag
flags(0) <= '1'          when O_itrn = 0           else '0'; -- zero flag
```

end Behavioral;

## EasyPrint.vhd (Used in testbenches)

A custom package that adds functions that make it easy to print std\_logic\_vectors in report statements. Two of these function are from stack overflow comments links to the origanl source of the functions are provided.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
USE ieee.numeric_std.ALL;

package easyprint is

function s_tostr(val : std_logic_vector) return string;
function u_tostr(val : std_logic_vector) return string;

function to_bstring(sl : std_logic) return string;
function to_bstring(slv : std_logic_vector) return string;

end easyprint;

package body easyprint is

    -- =====
    -- From http://stackoverflow.com/a/24336034 By Morten Zilmer
    -- Allows printing a std_logic_vector as a string that represents it's binary form.
    -- =====
    function to_bstring(sl : std_logic) return string is
        variable sl_str_v : string(1 to 3); -- std_logic image with quotes around
    begin
        sl_str_v := std_logic'image(sl);
        return "\"" & sl_str_v(2); -- "\"" & character to get string
    end function;

    function to_bstring(slv : std_logic_vector) return string is
        alias slv_norm : std_logic_vector(1 to slv'length) is slv;
        variable sl_str_v : string(1 to 1); -- String of std_logic
        variable res_v : string(1 to slv'length);
    begin
        for idx in slv_norm'range loop
            sl_str_v := to_bstring(slv_norm(idx));
```

## (Continued.)

```
        res_v(idx) := sl_str_v(1);
    end loop;
    return res_v;
end function;
-- =====

-- converts an std_logic_vector to a string that represents it's signed value
function s_tostr(val : std_logic_vector) return string is
begin
    return integer'image( to_integer(signed(val)) );
end function;

-- converts an std_logic_vector to a string that represents it's unsigned value
function u_tostr(val : std_logic_vector) return string is
begin
    return integer'image( to_integer(unsigned(val)) );
end function;

end easyprint;
```

## Reg.vhd (Used for all Datapaths)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- A parameterizable synchronous reset D-type registers with enable
entity Reg is
    Generic(
        data_size: natural := 8 -- How many bits will the register deal with
    );
    Port (
        clk : in  STD_LOGIC;
        rst : in  STD_LOGIC;    -- synchronus reset
        en  : in  STD_LOGIC;    -- synchronus reset
        data_in : in  STD_LOGIC_VECTOR (data_size-1 downto 0); -- input
        data_out : out STD_LOGIC_VECTOR (data_size-1 downto 0) -- output
    );
end Reg;

architecture Behavioral of Reg is
begin

    process(clk)
    begin
        -- Synchronise to the clock
        if (rising_edge(clk)) then
            if (rst = '1') then
                -- Reset to zero
                data_out <= (others => '0');
            elsif (en = '1') then
                -- Pass the input to the output
                data_out <= data_in;
            end if;
        end if;
    end process;

end Behavioral;
```

# Architecture B

## DataPathB.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.DigEng.all;

entity DataPath_B is
    GENERIC(
        data_size : natural := 16;
        num_registers : natural := 32
    );
    Port (
        clk : in STD_LOGIC;

        R_A : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Read address A
        R_B : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Read address B
        W_EN : in STD_LOGIC; -- Register write enable
        W_A : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Write address
        IMM : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Intermediate value
        AL : in STD_LOGIC_VECTOR (3 downto 0); -- ALU control
        SH : in STD_LOGIC_VECTOR (log2(data_size)-1 downto 0); -- Shift amount
        M_A : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory address
        S : in STD_LOGIC_VECTOR (4 downto 1); -- Selector control
        flags : out STD_LOGIC_VECTOR (7 downto 0); -- ALU flags
        M_B : out STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory output (write)
        M_DA : out STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory address
        M_in : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory input (read)
    );
end DataPath_B;

architecture Behavioral of DataPath_B is

    signal reg_in : STD_LOGIC_VECTOR (data_size-1 downto 0); -- register write data

    signal A_data : STD_LOGIC_VECTOR (data_size-1 downto 0); -- Data from register at address R_A
    signal B_data : STD_LOGIC_VECTOR (data_size-1 downto 0); -- Data from register at address R_B

    signal B_mux : STD_LOGIC_VECTOR (data_size-1 downto 0); -- B input to the ALU

    signal ALU_out : STD_LOGIC_VECTOR (data_size-1 downto 0); -- Output of the ALU

begin

    -- Multiplexer on the ALU's B input
    B_mux <= B_data when S(1) = '0' else IMM;

    -- Multiplexer for the memory address
    M_DA <= M_A when s(3) = '1' else ALU_out;

    -- Multiplexer for the register write data
    reg_in <= ALU_out when s(4) = '0' else M_in;

    -- Memory write (output) connection
    M_B <= B_data;

    -- The ALU
    ALU: entity work.ALU_param
    GENERIC MAP(
        N => data_size
    )
    PORT MAP(
        A => A_data,
        B => B_mux,
        X => SH,
        ctrl => AL,
        O => ALU_out,
        flags => flags
    );
end;
```

## (Continued.)

```
-- The register bank
Registers: entity work.regbank
PORT MAP(
    RSELA => R_A,
    RSELB => R_B,
    WSEL => W_A,
    D => reg_in,
    WEN => W_EN,
    clk => clk,
    A => A_data,
    B => B_data,
    rst => '0'
);

end Behavioral;
```

## Test Data for DataPath B

Here is the control signals and expected outputs that we are using to test datapath B.

Test Command	W_EN	AL[3:0]	R_A[4:0]	R_B[4:0]	W_A[4:0]	IMM[15:0]	SH[3:0]	M_A[3:0]	S[4:1]	M_in[3:0]	flags[7:0]	M_B[3:0]	M_DA[3:0]	OEN
inc R1, R0	1	1000	00000	000000	00001	0x0000	0000	0x0000	0000	0x0000	01010110	0x0000	0x0000	0
addi R2, R0, 0x0005	1	1010	00000	000000	00010	0x0005	0000	0x0000	0001	0x0000	01010010	0x0000	0x0000	0
shl R3, R1, 3	1	1100	00001	000000	00011	0x0000	0011	0x0000	0000	0x0000	01010010	0x0000	0x0000	0
storr R2, R3	0	0000	00011	00010	00000	0x0000	0000	0x0000	0000	0x0000	01010010	0x0005	0x0008	1
loadi R5, 1f1f	1	0000	00000	000000	00101	0x0000	0000	0x1f1f	1100	0xCCCC	00000000	0x0000	0x1f1f	0

# DataPathB-TB.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE work.DigEng.ALL;
USE work.easyprint.ALL;
USE ieee.numeric_std.ALL;

ENTITY DataPathB_TB IS
END DataPathB_TB;

ARCHITECTURE behavior OF DataPathB_TB IS

    -- Constants
    constant data_size : NATURAL := 16;
    constant num_registers : NATURAL := 32;

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT DataPath_B
        GENERIC(
            data_size : natural;
            num_registers : natural
        );
        PORT (
            R_A : IN  std_logic_vector(log2(num_registers)-1 downto 0);
            R_B : IN  std_logic_vector(log2(num_registers)-1 downto 0);
            W_EN : IN  std_logic;
            W_A : IN  std_logic_vector(log2(num_registers)-1 downto 0);
            clk : IN  std_logic;
            IMM : IN  std_logic_vector(data_size-1 downto 0);
            AL : IN  std_logic_vector(3 downto 0);
            SH : IN  std_logic_vector(log2(data_size)-1 downto 0);
            M_A : IN  std_logic_vector(data_size-1 downto 0);
            S : IN  std_logic_vector(4 downto 1);
            flags : OUT std_logic_vector(7 downto 0);
            M_B : OUT std_logic_vector(data_size-1 downto 0);
            M_DA : OUT std_logic_vector(data_size-1 downto 0);
            M_in : IN  std_logic_vector(data_size-1 downto 0)
        );
    END COMPONENT;

    --Inputs
    signal R_A : std_logic_vector(log2(num_registers)-1 downto 0) := (others => '0');
    signal R_B : std_logic_vector(log2(num_registers)-1 downto 0) := (others => '0');
    signal W_EN : std_logic := '0';
    signal W_A : std_logic_vector(log2(num_registers)-1 downto 0) := (others => '0');
    signal clk : std_logic := '0';
    signal IMM : std_logic_vector(data_size-1 downto 0) := (others => '0');
    signal AL : std_logic_vector(3 downto 0) := (others => '0');
    signal SH : std_logic_vector(log2(data_size)-1 downto 0) := (others => '0');
    signal M_A : std_logic_vector(data_size-1 downto 0) := (others => '0');
    signal S : std_logic_vector(4 downto 1) := (others => '0');
    signal M_in : std_logic_vector(data_size-1 downto 0) := (others => '0');
```

## (Continued.)

```
--Outputs
signal flags          : std_logic_vector      (7 downto 0);
signal M_B            : std_logic_vector      (data_size-1 downto 0);
signal M_DA : std_logic_vector      (data_size-1 downto 0);
signal OEN : std_logic := '0';

-- Clock period definitions
constant clk_period  : time  := 10 ns;
constant wait_time   : time  := clk_period;

-- Test data for self checking test bench
type TEST_VECTOR is RECORD
    W_EN : std_logic;
    AL : std_logic_vector(3 downto 0);
    R_A : STD_LOGIC_VECTOR(log2(num_registers)-1 downto 0);
    R_B : std_logic_vector(log2(num_registers)-1 downto 0);
    W_A : std_logic_vector(log2(num_registers)-1 downto 0);
    IMM : std_logic_vector(data_size-1 downto 0);
    SH : std_logic_vector(log2(data_size)-1 downto 0) ;
    M_A : std_logic_vector(data_size-1 downto 0);
    S : std_logic_vector(4 downto 1);
    M_in : std_logic_vector(data_size-1 downto 0);

    flags : std_logic_vector(7 downto 0);
    M_B : std_logic_vector(data_size-1 downto 0);
    M_DA : std_logic_vector(data_size-1 downto 0);

    OEN : std_logic;
end RECORD;

type TEST_VECTOR_ARRAY is ARRAY(NATURAL RANGE <>) of TEST_VECTOR;

constant test_vectors : TEST_VECTOR_ARRAY := (
    --W_EN,      AL,      R_A,      R_B,      W_A,      IMM,      flags,
    SH,      M_A,      S,      M_B,      M_DA,      M_in,      OEN
    ( '1',      "1000",      "00000",      "----",      "00001",      "-----",      "01010110",
      "----",      "-----",      "-----",      "0---",
      "-----",
      '0'),

    ('1',      "1010",      "00000",      "----",      "00010",      X"0005",      "01010010",
      "----",      "-----",      "-----",      "0--1",
      "-----",
      '0'),

    ('1',      "1100",      "00001",      "----",      "00011",      "-----",      "01010010",
      "0011",      "-----",      "-----",      "0---",
      "-----",
      '0'),

    ('0',      "0000",      "00011",      "00010",      "-----",      "-----",      "01010010",
      "-----",      "-----",      "0---",
      X"0005",      X"0008",
      '1'),

    ('1',      "----",      "----",      "----",      "00101",      "-----",
      "-----",      X"1f1f",      "11--",
      "-----",      X"1f1f",
      '0')
);
```



## (Continued.)

BEGIN

```
-- Instantiate the Unit Under Test (UUT)
ut: DataPath_B
Generic Map(
    data_size => data_size,
    num_registers => num_registers
)
PORT MAP (
    R_A => R_A,
    R_B => R_B,
    W_EN => W_EN,
    W_A => W_A,
    clk => clk,
    IMM => IMM,
    AL => AL,
    SH => SH,
    M_A => M_A,
    S => S,
    flags => flags,
    M_B => M_B,
    M_DA => M_DA,
    M_in => M_in
);

-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin

    -- hold reset state for 100 ns.
    wait for 100 ns;

    -- run the test for every set of data
    for i in test_vectors'range loop

        -- assign test inputs
        R_A <= test_vectors(i).R_A;
        R_B <= test_vectors(i).R_B;
        W_EN <= test_vectors(i).W_EN;
        W_A <= test_vectors(i).W_A;
        IMM <= test_vectors(i).IMM;
        AL <= test_vectors(i).AL;
        SH <= test_vectors(i).SH;
        M_A <= test_vectors(i).M_A;
        S <= test_vectors(i).S;
        M_in <= test_vectors(i).M_in;

        OEN <= test_vectors(i).OEN;

        wait until rising_edge(clk);

        -- Check that the actual outputs are the same as were expecting
        -- Have to use std_match when comparing meta values like '-'
        assert std_match(flags, test_vectors(i).flags)
        report lf & " [ERR!] Test " & integer'image(i) & lf &
            " Actual flags did not equal expected flags."&
            " Actual [ " & to_bstring(flags) & " ]" &
            " Expected [ " & to_bstring(test_vectors(i).flags) & " ]"
        severity error;

        assert std_match(test_vectors(i).M_B, M_B)
        report lf & " [ERR!] Test " & integer'image(i) & lf &
            " Actual value to memory did not equal expected value to memory."&
            " Actual [ " & u_tostr(M_B) & " ]" &
            " Expected [ " & u_tostr(test_vectors(i).M_B) & " ]"
        severity error;
    end loop;
end process;
```

## (Continued.)

```
assert std_match(M_DA , test_vectors(i).M_DA)
report if &" [ERR!] Test " & integer'image(i) & if &
    " Actual memory address did not equal expected memory address."&
    " Actual [ " & u_tostr(M_DA) & " ]" &
    " Expected [ " & u_tostr(test_vectors(i).M_DA) & " ]"
severity error;

-- If there were no issues report that the test was successful
assert not (
    std_match(flags, test_vectors(i).flags) and
    std_match(M_B, test_vectors(i).M_B) and
    std_match(M_DA, test_vectors(i).M_DA))
report if &" [ OK ] Test " & integer'image(i) & " was successful!"
severity note;

wait until falling_edge(clk);


end loop;

wait;

end process;
```

```
END;
```

## Simulations

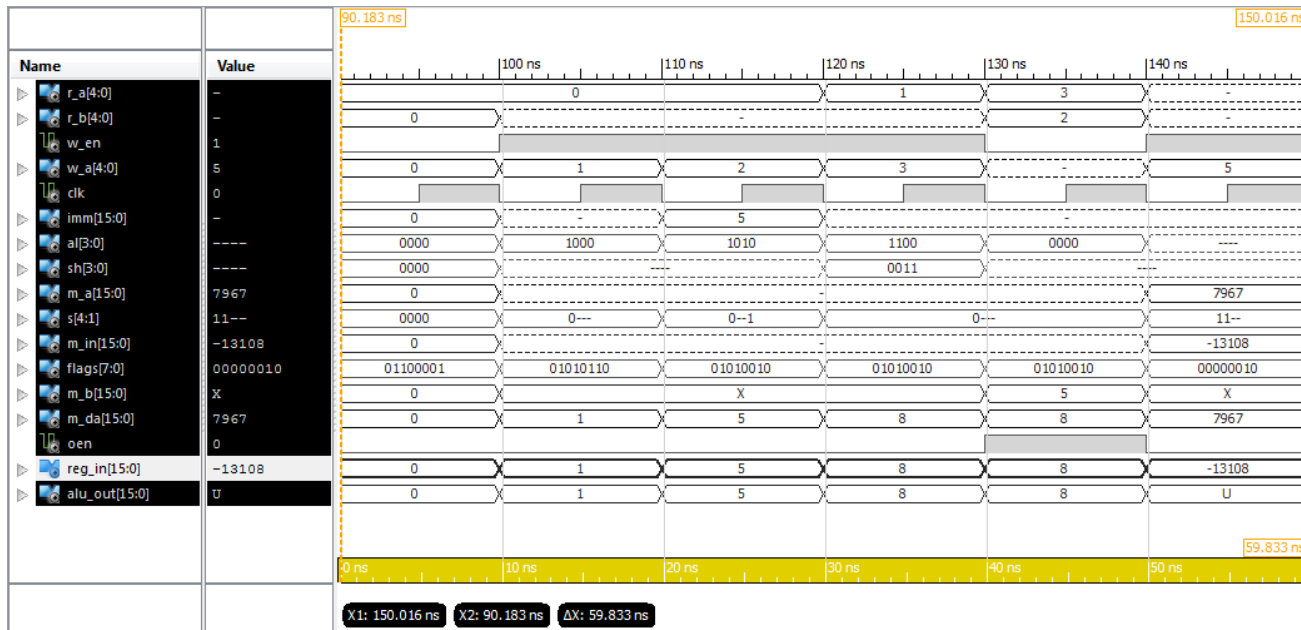

This Screenshot shows the entire simulation for DataPath B. The reg\_in signal is the data that will be written to the register bank.

## iSim Console Output

```
ISim P.28xd (signature 0xa0883be4)
This is a Full version of ISim.
Time resolution is 1 ps
WARNING: Simulation object /datapathb_tb/test_vectors was not traceable in the design for the following reason:
ISim does not yet support tracing of constant and generic multi-dimensional arrays.
Simulator is doing circuit initialization process.
at 0 ps, Instance /datapathb_tb/uut/ALU/ : Warning: NUMERIC_STD.">=": metavalue detected, returning FALSE
at 0 ps, Instance /datapathb_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapathb_tb/uut/ALU/ : Warning: NUMERIC_STD.">": metavalue detected, returning FALSE
at 0 ps, Instance /datapathb_tb/uut/ALU/ : Warning: NUMERIC_STD."<": metavalue detected, returning FALSE
at 0 ps, Instance /datapathb_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapathb_tb/uut/ALU/ : Warning: NUMERIC_STD.">=": metavalue detected, returning TRUE
at 0 ps, Instance /datapathb_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
Finished circuit initialization process.

at 105 ns(1): Note: [ OK ] Test 0 was successful! (/datapathb_tb/).
at 115 ns(1): Note: [ OK ] Test 1 was successful! (/datapathb_tb/).
at 125 ns(1): Note: [ OK ] Test 2 was successful! (/datapathb_tb/).
at 135 ns(1): Note: [ OK ] Test 3 was successful! (/datapathb_tb/).
at 145 ns(1): Note: [ OK ] Test 4 was successful! (/datapathb_tb/).
```

ISim>

*All but the first meta value warnings have been removed to improve readability.*

## HDL Synthesis

```
=====
*                               HDL Synthesis                               *
=====

Synthesizing Unit <DataPath B>.
  Related source file is "E:\University\Second Year\Computer Architectures\assesment\MyMicroProcessor\Lab_2\DataPaths -
  RegBankAlt\DataPath_B.vhd".
    data_size = 16
    num_registers = 32
WARNING:Xst:647 - Input <S<2:2>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it
  belongs to a sub-block and the hierarchy of this sub-block is preserved.
  Summary:
    inferred 3 Multiplexer(s).
```

```

Unit <DataPath_B> synthesized.

Synthesizing Unit <ALU_param>.
  Related source file is "E:\University\Second Year\Computer Architectures\assesment\MyMicroProcessor\Lab_2\DataPaths -
  RegBankAlt\ALU_param.vhd".
    N = 16
    Found 16-bit adder for signal <A_itrnr[15]_B_itrnr[15]_add_27_OUT> created at line 69.
    Found 16-bit adder for signal <A_itrnr[15]_GND_6_o_add_31_OUT> created at line 1253.
    Found 16-bit subtractor for signal <A_itrnr[15]_B_itrnr[15]_sub_26_OUT<15:0>> created at line 70.
    Found 16-bit subtractor for signal <A_itrnr[15]_GND_6_o_sub_30_OUT<15:0>> created at line 1320.
    Found 16-bit shifter rotate right for signal <A_itrnr[15]_X_itrnr[30]_rotate_right_17_OUT> created at line 3021
    Found 16-bit shifter rotate left for signal <A_itrnr[15]_X_itrnr[30]_rotate_left_19_OUT> created at line 3012
    Found 16-bit shifter arithmetic right for signal <A_itrnr[15]_X_itrnr[30]_shift_right_21_OUT> created at line 2982
    Found 16-bit shifter logical left for signal <A_itrnr[15]_X_itrnr[30]_shift_left_23_OUT> created at line 2973
    Found 16-bit 13-to-1 multiplexer for signal <O_itrnr> created at line 42.
    Found 16-bit comparator greater for signal <flags<3>> created at line 99
    Found 16-bit comparator greater for signal <flags<4>> created at line 100
    Summary:
      inferred 1 Adder/Subtractor(s).
      inferred 2 Comparator(s).
      inferred 16 Multiplexer(s).
      inferred 4 Combinational logic shifter(s).
Unit <ALU_param> synthesized.

Synthesizing Unit <regbank>.
  Related source file is "E:\University\Second Year\Computer Architectures\assesment\MyMicroProcessor\Lab_2\DataPaths -
  RegBankAlt\otherRegBank.vhd".
    Found 16-bit register for signal <REG02>.
    Found 16-bit register for signal <REG03>.
    Found 16-bit register for signal <REG04>.
    Found 16-bit register for signal <REG05>.
    Found 16-bit register for signal <REG06>.
    Found 16-bit register for signal <REG07>.
    Found 16-bit register for signal <REG08>.
    Found 16-bit register for signal <REG09>.
    Found 16-bit register for signal <REG10>.
    Found 16-bit register for signal <REG11>.
    Found 16-bit register for signal <REG12>.
    Found 16-bit register for signal <REG13>.
    Found 16-bit register for signal <REG14>.
    Found 16-bit register for signal <REG15>.
    Found 16-bit register for signal <REG16>.
    Found 16-bit register for signal <REG17>.
    Found 16-bit register for signal <REG18>.
    Found 16-bit register for signal <REG19>.
    Found 16-bit register for signal <REG20>.
    Found 16-bit register for signal <REG21>.
    Found 16-bit register for signal <REG22>.
    Found 16-bit register for signal <REG23>.
    Found 16-bit register for signal <REG24>.
    Found 16-bit register for signal <REG25>.
    Found 16-bit register for signal <REG26>.
    Found 16-bit register for signal <REG27>.
    Found 16-bit register for signal <REG28>.
    Found 16-bit register for signal <REG29>.
    Found 16-bit register for signal <REG30>.
    Found 16-bit register for signal <REG31>.
    Found 16-bit register for signal <REG01>.
    Found 16-bit 32-to-1 multiplexer for signal <A> created at line 30.
    Found 16-bit 32-to-1 multiplexer for signal <B> created at line 31.
    Summary:
      inferred 496 D-type flip-flop(s).
      inferred 2 Multiplexer(s).
Unit <regbank> synthesized.

```

# ``` ===== HDL Synthesis Report ```

```

Macro Statistics
# Adders/Subtractors      : 1
  16-bit addsub           : 1
# Registers               : 31
  16-bit register         : 31
# Comparators             : 2
  16-bit comparator greater : 2
# Multiplexers            : 21
  1-bit 2-to-1 multiplexer : 6
  16-bit 2-to-1 multiplexer : 13
  16-bit 32-to-1 multiplexer : 2
# Logic shifters          : 4
  16-bit shifter arithmetic right : 1
  16-bit shifter logical left : 1
  16-bit shifter rotate left : 1
  16-bit shifter rotate right : 1
# Xors                    : 1
  16-bit xor2             : 1

```

```

=====

```

# Architecture C

## DataPathC.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.DigEng.ALL;

entity DataPath_C is
  GENERIC(
    data_size : natural := 16;
    num_registers : natural := 32
  );
  Port (
    clk : in STD_LOGIC;
    rst : in STD_LOGIC;
    en : in STD_LOGIC;

    -- Inputs
    R_A : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Read address A
    R_B : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Read address B
    W_EN : in STD_LOGIC; -- Register write enable
    W_A : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Write address

    IMM : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Intermediate value
    M_A : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory address
    M_in : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory input (read)
    PC : in STD_LOGIC_VECTOR (15 downto 0); -- Current Program Counter
    S : in STD_LOGIC_VECTOR (4 downto 1); -- Selector control
    AL : in STD_LOGIC_VECTOR (3 downto 0); -- ALU control
    SH : in STD_LOGIC_VECTOR (log2(data_size)-1 downto 0); -- Shift amount

    -- Outputs
    PC_plus : out STD_LOGIC_VECTOR (15 downto 0); -- Next Program Counter
    Flags : out STD_LOGIC_VECTOR (7 downto 0); -- ALU flags
    M_DA : out STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory address
    M_out : out STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory output (write)
  );
end DataPath_C;

architecture Behavioral of DataPath_C is

  -- Data to write to the registers
  signal reg_in : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- Outputs of the registers
  signal A_data : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal B_data : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- Output of the register on the A and B buses
  signal A_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal B_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- The Outputs of the two Muxes on the input to the ALU
  signal A_mux : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal B_mux : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- The output of the combined ALU and shifter
  signal ALU_out : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal ALU_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- The output of the memory in register
  signal M_in_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

begin

  -- The two multiplexers on the input to the ALU
  A_mux <= A_reg_out when S(2) = '0' else PC;
  B_mux <= B_reg_out when S(1) = '0' else IMM;

  -- The address multiplexer for the memory
  M_DA <= M_A when s(3) = '1' else ALU_reg_out;

  M_out <= B_reg_out;
  PC_plus <= ALU_reg_out;
```

## (Continued.)

```
-- The register write multiplexer
reg_in <= ALU_reg_out when s(4) = '0' else M_in_reg_out;

-- The register on the A bus
A_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => A_data,
    data_out => A_reg_out
);

-- The register on the B bus
B_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => B_data,
    data_out => B_reg_out
);

-- The Register on the out put of the ALU
ALU_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => ALU_out,
    data_out => ALU_reg_out
);

-- The register on the memory read bus
M_in_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => M_in,
    data_out => M_in_reg_out
);

-- The ALU and shifter from Lab 1
ALU: entity work.ALU_param GENERIC MAP( N => data_size )
PORT MAP(
    A => A_mux,
    B => B_mux,
    X => SH,
    ctrl => AL,
    O => ALU_out,
    flags => flags
);

-- The register bank
Registers: entity work.regbank
PORT MAP(
    RSELA => R_A,
    RSELB => R_B,
    WSEL => W_A,
    D => reg_in,
    WEN => W_EN,
    clk => clk,
    A => A_data,
    B => B_data,
    rst => '0'
);

end Behavioral;
```

## Test Data for DataPath C

Here is the control signals and test data fro datapath C

Test Command	Stage	R_A [4:0]	R_B [4:0]	W_EN	W_A [4:0]	IMM [15:0]	M_A [15:0]	M_in [15:0]	[15:0 S ]	S [4:1]	AL [3:0]	SH [3:0]	[15:0 Flags ]	M_DA [15:0]	M_out [15:0]	OEN	
inc R1, R0	Fetch	000000	000000	0	000000	0x000000	0x000000	0x000000	00FF	0010	1000	0000	0000	01010010	0x000000	0x000000	0
	RegRd	000000	000000	0	000000	0x000000	0x000000	0x000000	00FF	0000	0000	0000	0100	00000000	0x000000	0x000000	0
	ALU	000000	000000	0	000000	0x000000	0x000000	0x000000	00FF	0000	1000	0000	0000	01010110	0x000000	0x000000	0
	RegWr	000000	000000	1	00001	0x000000	0x000000	0x000000	00FF	0000	0000	0000	0000	00000000	0x000000	0x000000	0
addi R2, R0, 0x0005	Fetch	000000	000000	0	000000	0x000000	0x000000	0x000000	0100	0010	1000	0000	0000	01010010	0x000000	0x000000	0
	RegRd	000000	000000	0	000000	0x000000	0x000000	0x000000	0100	0000	0000	0000	0101	00000000	0x000000	0x000000	0
	ALU	000000	000000	0	000000	0x000005	0x000000	0x000000	0100	0001	1010	0000	0000	01010010	0x000000	0x000000	0
	RegWr	000000	000000	1	00010	0x000000	0x000000	0x000000	0100	0000	0000	0000	0000	00000000	0x000000	0x000000	0
shl R3, R1, 3	Fetch	000000	000000	0	000000	0x000000	0x000000	0x000000	0101	0010	1000	0000	0000	01010010	0x000000	0x000000	0
	RegRd	000001	000000	0	000000	0x000000	0x000000	0x000000	0101	0000	0000	0000	0102	00000000	0x000000	0x000000	0
	ALU	000000	000000	0	000000	0x000000	0x000000	0x000000	0101	0000	1100	0011	0000	01010010	0x000000	0x000000	0
	RegWr	000000	000000	1	00011	0x000000	0x000000	0x000000	0101	0000	0000	0000	0000	00000000	0x000000	0x000000	0
storr R2, R3	Fetch	000000	000000	0	000000	0x000000	0x000000	0x000000	0102	0010	1000	0000	0000	01010010	0x000000	0x000000	0
	RegRd	000011	000000	0	000000	0x000000	0x000000	0x000000	0102	0000	0000	0000	0103	00000000	0x000000	0x000000	0
	ALU	000000	000010	0	000000	0x000000	0x000000	0x000000	0102	0000	0000	0000	0000	01010010	0x000000	0x000000	0
	Mem Acc	000000	000000	0	000000	0x000000	0x000000	0x000000	0102	0000	0000	0000	0000	00000000	0x000008	0x000005	1
loadi R5, 1f1f	Fetch	000000	000000	0	000000	0x000000	0x000000	0x000000	0103	0010	1000	0000	0000	01010010	0x000000	0x000000	0
	Mem Acc	000000	000000	0	000000	0x000000	1F1F	CCCC	0103	0100	0000	0000	0104	00000000	0x1f1f	0x000000	0
	RegWrite	000000	000000	1	00101	0x000000	0x000000	0x000000	0103	1000	0000	0000	0000	00000000	0x000000	0x000000	0
brneq R2, 010F	Fetch	000000	000000	0	000000	0x000000	0x000000	0x000000	0104	0010	1000	0000	0000	01010010	0x000000	0x000000	0
	RegRd	000010	000000	0	000000	0x0010F	0x000000	0x000000	0104	0011	1010	0000	0105	01010010	0x000000	0x000000	0
	ALU	000000	000000	0	000000	0x000000	0x000000	0x000000	0104	0000	1010	0000	0213	-----10	0x000000	0x000000	0

# DataPathC-TB.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE work.DigEng.ALL;
USE work.easyprint.ALL;
USE ieee.numeric_std.ALL;

ENTITY DataPath_C_TB IS
END DataPath_C_TB;

ARCHITECTURE behavior OF DataPath_C_TB IS

    -- Constants
    constant data_size : NATURAL := 16;
    constant num_registers : NATURAL := 32;

    -- Clock period definitions
    constant clk_period : time := 10 ns;

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT DataPath_C
        GENERIC (
            data_size : natural;
            num_registers : natural
        );
        PORT (
            clk      : IN      std_logic;
            rst      : IN      std_logic;
            en       : IN      std_logic;

            R_A      : IN      std_logic_vector (log2(num_registers)-1 downto 0);
            R_B      : IN      std_logic_vector (log2(num_registers)-1 downto 0);
            W_EN     : IN      std_logic;
            W_A      : IN      std_logic_vector (log2(num_registers)-1 downto 0);
            IMM      : IN      std_logic_vector (data_size-1 downto 0);
            M_A      : IN      std_logic_vector (data_size-1 downto 0);
            M_in     : IN      std_logic_vector (data_size-1 downto 0);
            PC       : IN      std_logic_vector (15 downto 0);
            S        : IN      std_logic_vector (4 downto 1);
            AL       : IN      std_logic_vector (3 downto 0);
            SH       : IN      std_logic_vector (log2(data_size)-1 downto 0);

            PC_plus  : OUT     std_logic_vector (15 downto 0);
            Flags    : OUT     std_logic_vector (7 downto 0);
            M_DA     : OUT     std_logic_vector (data_size-1 downto 0);
            M_out    : OUT     std_logic_vector (data_size-1 downto 0)
        );
    END COMPONENT;

    --Inputs
    signal clk      : std_logic := '0';
    signal rst      : std_logic := '1';
    signal en       : std_logic := '0';

    signal R_A      : std_logic_vector (log2(num_registers)-1 downto 0) := (others => '0');
    signal R_B      : std_logic_vector (log2(num_registers)-1 downto 0) := (others => '0');
    signal W_EN     : std_logic := '0';
    signal W_A      : std_logic_vector (log2(num_registers)-1 downto 0) := (others => '0');
    signal IMM      : std_logic_vector (data_size-1 downto 0) := (others => '0');
    signal M_A      : std_logic_vector (data_size-1 downto 0) := (others => '0');
    signal M_in : std_logic_vector (data_size-1 downto 0) := (others => '0');
    signal PC       : std_logic_vector (15 downto 0) := (others => '0');
    signal S        : std_logic_vector (4 downto 1) := (others => '0');
    signal AL       : std_logic_vector (3 downto 0) := (others => '0');
    signal SH       : std_logic_vector (log2(data_size)-1 downto 0) := (others => '0');

    --Outputs
    signal PC_plus  : std_logic_vector (15 downto 0);
    signal Flags    : std_logic_vector (7 downto 0);
    signal M_DA     : std_logic_vector (data_size-1 downto 0);
    signal M_out    : std_logic_vector (data_size-1 downto 0);
    signal OEN : std_logic := '0';

    -- Test data definitions
    type TEST_VECTOR is RECORD
        R_A      : STD_LOGIC_VECTOR(log2(num_registers)-1 downto 0);
        R_B      : std_logic_vector(log2(num_registers)-1 downto 0);
```



## (Continued.)

```
W_EN : std_logic;
W_A  : std_logic_vector(log2(num_registers)-1 downto 0);

IMM  : std_logic_vector(data_size-1 downto 0);
M_A  : std_logic_vector(data_size-1 downto 0);
M_in : std_logic_vector(data_size-1 downto 0);
PC   : std_logic_vector(15 downto 0);
S    : std_logic_vector(4 downto 1);
AL   : std_logic_vector(3 downto 0);
SH   : std_logic_vector(log2(data_size)-1 downto 0);

PC_plus: std_logic_vector(15 downto 0);
flags  : std_logic_vector(7 downto 0);
M_DA   : std_logic_vector(data_size-1 downto 0);
M_out  : std_logic_vector(data_size-1 downto 0);

OEN : std_logic;
end RECORD;
type TEST_VECTOR_ARRAY is ARRAY(NATURAL RANGE <>) of TEST_VECTOR;

-- Test Data
constant test_vectors : TEST_VECTOR_ARRAY := (
--R_A,      R_B,      W_EN,  W_A,      IMM,      AL,      M_A,
M_in,      PC,      S,      PC_plus,  M_DA,      SH,      M_out,
OEN --

-- inc R1, R0
( "-----", "-----", '0', "-----", "-----", "-----", "-----",
"-----", "-----", X"00FF", "-----1-", "1000", "-----",
"-----", "-----", "01010010", "-----", "-----",
'0' ),

( "00000", "-----", '0', "-----", "-----", "-----", "-----",
"-----", "-----", X"00FF", "-----", "-----", "-----",
X"0100", "-----", "-----", "-----", "-----",
'0' ),

( "-----", "-----", '0', "-----", "-----", "-----", "-----",
"-----", "-----", X"00FF", "-----0-", "1000", "-----",
"-----", "-----", "01010110", "-----", "-----",
'0' ),

( "-----", "-----", '1', "00001", "-----", "-----", "-----",
"-----", "-----", X"00FF", "0-----", "-----", "-----",
"-----", "-----", "-----", "-----",
'0' ),

-- addi R2, R0, 0x0005
( "-----", "-----", '0', "-----", "-----", "-----", "-----",
"-----", "-----", X"0100", "-----1-", "1000", "-----",
"-----", "-----", "01010010", "-----", "-----",
'0' ),

( "00000", "-----", '0', "-----", "-----", "-----", "-----",
"-----", "-----", X"0100", "-----", "-----", "-----",
X"0101", "-----", "-----", "-----",
'0' ),

( "-----", "-----", '0', "-----", X"0005", "-----", "-----",
"-----", "-----", X"0100", "-----01-", "1010", "-----",
"-----", "-----", "01010010", "-----", "-----",
'0' ),

( "-----", "-----", '1', "00010", "-----", "-----", "-----",
"-----", "-----", X"0100", "0-----", "-----", "-----",
"-----", "-----", "-----", "-----",
'0' ),

-- shl R3, R1, 3
( "-----", "-----", '0', "-----", "-----", "-----", "-----",
"-----", "-----", X"0101", "-----1-", "1000", "-----",
"-----", "-----", "01010010", "-----", "-----",
'0' ),

( "00001", "-----", '0', "-----", "-----", "-----", "-----",
"-----", "-----", X"0101", "-----", "-----", "-----",
X"0102", "-----", "-----", "-----",
'0' ),
```

## (Continued.)

```
( "-----", "-----", '0', "-----", "-----", "-----", "-----",  
"-----", "-----", X"0101", "-----", "--0-", "1100", "0011",  
"-----", "-----", "01010010", "-----", "-----",  
'0' ),  
  
( "-----", "-----", '1', "00011", "-----", "-----",  
"-----", "-----", X"0101", "-----", "0--", "-----",  
"-----", "-----", "-----",  
'0' ),  
  
-- storr R2, R3  
( "-----", "-----", '0', "-----", "-----", "-----",  
"-----", "-----", X"0102", "-----", "--1-", "1000",  
"-----", "-----", "01010010", "-----", "-----",  
'0' ),  
  
( "00011", "-----", '0', "-----", "-----", "-----",  
"-----", "-----", X"0102", "-----", "-----", "-----",  
X"0103", "-----", "-----",  
'0' ),  
  
( "-----", "00010", '0', "-----", "-----", "-----",  
"-----", "-----", X"0102", "-----", "--00", "0000",  
"-----", "-----", "01010010", "-----", "-----",  
'0' ),  
  
( "-----", "-----", '0', "-----", "-----", "-----",  
"-----", "-----", X"0102", "-----", "0--", "-----",  
"-----", "-----", X"0008", "-----", X"0005",  
'1' ),  
  
-- loadi R5, 1f1f  
( "-----", "-----", '0', "-----", "-----", "-----",  
"-----", "-----", X"0103", "-----", "--1-", "1000",  
"-----", "-----", "01010010", "-----", "-----",  
'0' ),  
  
( "-----", "-----", '0', "-----", "-----", "-----",  
X"CCCC", "-----", X"0103", "-----", "1--", "-----", X"1F1F",  
X"0104", "-----", "-----", X"1f1f", "-----",  
'0' ),  
  
( "-----", "-----", '1', "00101", "-----", "-----",  
"-----", "-----", X"0103", "-----", "1--", "-----",  
"-----", "-----", "-----",  
'0' ),  
  
-- brneq R2, 010F  
( "-----", "-----", '0', "-----", "-----", "-----",  
"-----", "-----", X"0104", "-----", "--1-", "1000",  
"-----", "-----", "01010010", "-----", "-----",  
'0' ),  
  
( "00010", "00000", '0', "-----", "-----", "-----",  
"-----", "-----", X"0104", "-----", "--11", "1010",  
X"0105", "-----", "01010010", "-----", "-----",  
'0' ),  
  
( "-----", "-----", '0', "-----", "-----", "-----",  
"-----", "-----", X"0104", "-----", "--00", "1010",  
X"0213", "-----", "-----10", "-----",  
'0' )  
);
```

## (Continued.)

BEGIN

```
-- Instantiate the Unit Under Test (UUT)
 uut: DataPath_C
Generic Map(
    data_size => data_size,
    num_registers => num_registers
)
PORT MAP (
    clk => clk,
    rst => rst,
    en => en,

    -- Inputs
    R_A => R_A,
    R_B => R_B,

    W_EN => W_EN,
    W_A => W_A,

    IMM => IMM,
    M_A => M_A,
    M_in => M_in,
    PC => PC,
    S => S,
    AL => AL,
    SH => SH,

    -- Outputs
    PC_plus => PC_plus,
    Flags => Flags,
    M_DA => M_DA,
    M_out => M_out
);

-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin

    -- hold reset state for 100 ns.
    wait for 100 ns;

    -- enable the system
    rst <= '0';
    en <= '1';
    wait for 2*clk_period;

    -- run the test for every set of data
    for i in test_vectors'range loop

        wait until rising_edge(clk);

        -- assign test inputs
        R_A <= test_vectors(i).R_A;
        R_B <= test_vectors(i).R_B;

        W_EN <= test_vectors(i).W_EN;
        W_A <= test_vectors(i).W_A;

        IMM <= test_vectors(i).IMM;
        M_A <= test_vectors(i).M_A;
        M_in <= test_vectors(i).M_in;
        PC <= test_vectors(i).PC;
        S <= test_vectors(i).S;
        AL <= test_vectors(i).AL;
        SH <= test_vectors(i).SH;

        OEN <= test_vectors(i).OEN;
```

## (Continued.)

```
wait until falling_edge(clk);

-- Check to see if the out put was what we were expecting
-- Have to use std_match() instead of = when comparing meta values like '-'
assert std_match(test_vectors(i).flags, flags)
report if & " [ERR!] Test " & integer'image(i) &
    " Actual flags did not equal expected flags."&
    " Actual [ " & to_bstring(flags) & " ]" &
    " Expected [ " & to_bstring(test_vectors(i).flags) & " ]" & if
severity error;

assert std_match(test_vectors(i).M_out, M_out)
report if & " [ERR!] Test " & integer'image(i) &
    " Actual value to memory did not equal expected value to memory."&
    " Actual [ " & u_tostr(M_out) & " ]" &
    " Expected [ " & u_tostr(test_vectors(i).M_out) & " ]" & if
severity error;

assert std_match(M_DA , test_vectors(i).M_DA)
report if & " [ERR!] Test " & integer'image(i) &
    " Actual memory address did not equal expected memory address."&
    " Actual [ " & u_tostr(M_DA) & " ]" &
    " Expected [ " & u_tostr(test_vectors(i).M_DA) & " ]" & if
severity error;

assert std_match(PC_plus, test_vectors(i).PC_plus)
report if & " [ERR!] Test " & integer'image(i) &
    " Actual program counter did not equal expected program counter."&
    " Actual [ " & u_tostr(PC_plus) & " ]" &
    " Expected [ " & u_tostr(test_vectors(i).PC_plus) & " ]" & if
severity error;


-- if there were no issues report that the test was successful
assert not (
    std_match(flags, test_vectors(i).flags) and
    std_match(M_out, test_vectors(i).M_out) and
    std_match(M_DA, test_vectors(i).M_DA) and
    std_match(PC_plus, test_vectors(i).PC_plus)
)
report if & " [ OK ] Test " & integer'image(i) & " was successful!" & if
severity note;

end loop;


-- End of test
wait;
end process;
```

END;


## Simulations

 


Screenshot showing the 'inc' instruction

 

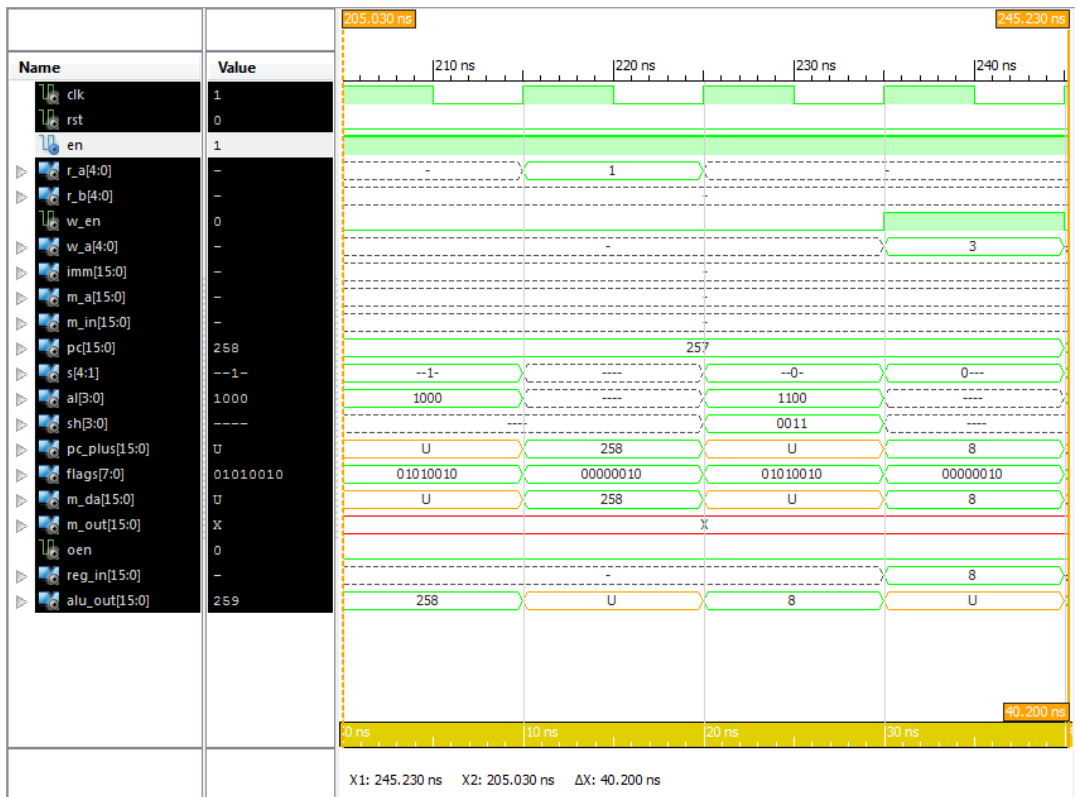
Screenshot showing the 'addi' instruction




Screenshot showing the 'shl' instruction

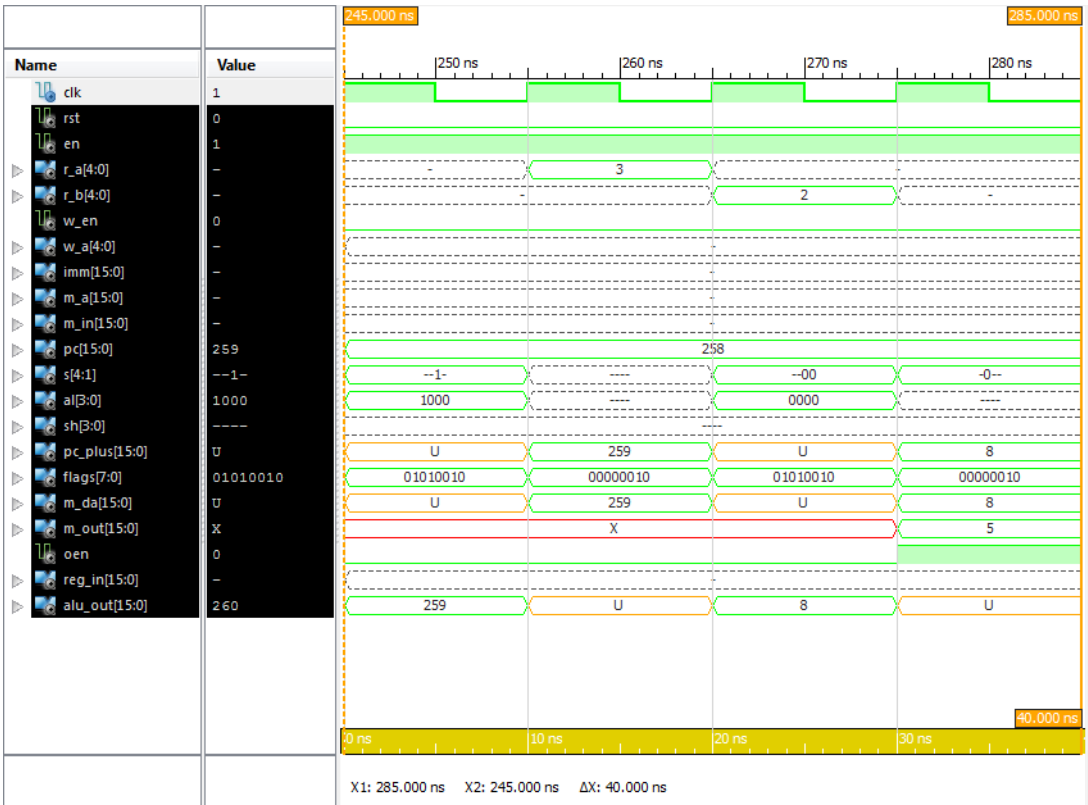

 Screenshot showing the 'storr' instruction



 Screenshot showing the 'loadi' instruction



Screenshot showing the 'brneq' instruction

## iSim Console Output

iSim P.28xd (signature 0xa0883be4)

This is a Full version of iSim.

Time resolution is 1 ps

WARNING: Simulation object /datapath\_c\_tb/test\_vectors was not traceable in the design for the following reason:  
iSim does not yet support tracing of constant and generic multi-dimensional arrays.

Simulator is doing circuit initialization process.

```
at 0 ps, Instance /datapath_c_tb/uut/ALU/ : Warning: NUMERIC_STD.">=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_c_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_c_tb/uut/ALU/ : Warning: NUMERIC_STD.">": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_c_tb/uut/ALU/ : Warning: NUMERIC_STD."<": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_c_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_c_tb/uut/ALU/ : Warning: NUMERIC_STD.">=": metavalue detected, returning TRUE
at 0 ps, Instance /datapath_c_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
Finished circuit initialization process.
```

```
at 130 ns(1): Note: [ OK ] Test 0 was successful! (/datapath_c_tb/).
at 140 ns(1): Note: [ OK ] Test 1 was successful! (/datapath_c_tb/).
at 150 ns(1): Note: [ OK ] Test 2 was successful! (/datapath_c_tb/).
at 160 ns(1): Note: [ OK ] Test 3 was successful! (/datapath_c_tb/).
at 170 ns(1): Note: [ OK ] Test 4 was successful! (/datapath_c_tb/).
at 180 ns(1): Note: [ OK ] Test 5 was successful! (/datapath_c_tb/).
at 190 ns(1): Note: [ OK ] Test 6 was successful! (/datapath_c_tb/).
at 200 ns(1): Note: [ OK ] Test 7 was successful! (/datapath_c_tb/).
at 210 ns(1): Note: [ OK ] Test 8 was successful! (/datapath_c_tb/).
at 220 ns(1): Note: [ OK ] Test 9 was successful! (/datapath_c_tb/).
at 230 ns(1): Note: [ OK ] Test 10 was successful! (/datapath_c_tb/).
at 240 ns(1): Note: [ OK ] Test 11 was successful! (/datapath_c_tb/).
at 250 ns(1): Note: [ OK ] Test 12 was successful! (/datapath_c_tb/).
at 260 ns(1): Note: [ OK ] Test 13 was successful! (/datapath_c_tb/).
at 270 ns(1): Note: [ OK ] Test 14 was successful! (/datapath_c_tb/).
at 280 ns(1): Note: [ OK ] Test 15 was successful! (/datapath_c_tb/).
at 290 ns(1): Note: [ OK ] Test 16 was successful! (/datapath_c_tb/).
at 300 ns(1): Note: [ OK ] Test 17 was successful! (/datapath_c_tb/).
at 310 ns(1): Note: [ OK ] Test 18 was successful! (/datapath_c_tb/).
at 320 ns(1): Note: [ OK ] Test 19 was successful! (/datapath_c_tb/).
at 330 ns(1): Note: [ OK ] Test 20 was successful! (/datapath_c_tb/).
at 340 ns(1): Note: [ OK ] Test 21 was successful! (/datapath_c_tb/).
```

iSim>

***All but the first meta value warnings have been removed to improve readability.***

## HDL Synthesis

```
=====
*                               HDL Synthesis                               *
=====
```

Synthesizing Unit <DataPath\_C>.

Related source file is "E:\University\Second Year\Computer Architectures\assessment\MyMicroProcessor\Lab\_2\DataPaths - RegBankAlt\DataPath\_C.vhd".

data\_size = 16

num\_registers = 32

Summary:

inferred 4 Multiplexer(s).

Unit <DataPath\_C> synthesized.

Synthesizing Unit <Reg>.

Related source file is "E:\University\Second Year\Computer Architectures\assessment\MyMicroProcessor\Lab\_2\DataPaths - RegBankAlt\Reg.vhd".

data\_size = 16

Found 16-bit register for signal <data\_out>.

Summary:

inferred 16 D-type flip-flop(s).

Unit <Reg> synthesized.

Synthesizing Unit <ALU\_param>.

Related source file is "E:\University\Second Year\Computer Architectures\assessment\MyMicroProcessor\Lab\_2\DataPaths - RegBankAlt\ALU\_param.vhd".

N = 16

Found 16-bit adder for signal <A\_itr[n][15]\_B\_itr[n][15]\_add\_27\_OUT> created at line 69.

Found 16-bit adder for signal <A\_itr[n][15]\_GND\_7\_o\_add\_31\_OUT> created at line 1253.

Found 16-bit subtractor for signal <A\_itr[n][15]\_B\_itr[n][15]\_sub\_26\_OUT<15:0>> created at line 70.

Found 16-bit subtractor for signal <A\_itr[n][15]\_GND\_7\_o\_sub\_30\_OUT<15:0>> created at line 1320.

Found 16-bit shifter rotate right for signal <A\_itr[n][15]\_X\_itr[n][30]\_rotate\_right\_17\_OUT> created at line 3021

Found 16-bit shifter rotate left for signal <A\_itr[n][15]\_X\_itr[n][30]\_rotate\_left\_19\_OUT> created at line 3012

Found 16-bit shifter arithmetic right for signal <A\_itr[n][15]\_X\_itr[n][30]\_shift\_right\_21\_OUT> created at line 2982



```

Found 16-bit shifter logical left for signal <A_itr[15]_X_itr[30]_shift_left_23_OUT> created at line 2973
Found 16-bit 13-to-1 multiplexer for signal <O_itr> created at line 42.
Found 16-bit comparator greater for signal <flags<3>> created at line 99
Found 16-bit comparator greater for signal <flags<4>> created at line 100
Summary:
    inferred    1 Adder/Subtractor(s).
    inferred    2 Comparator(s).
    inferred   16 Multiplexer(s).
    inferred    4 Combinational logic shifter(s).
Unit <ALU_param> synthesized.

Synthesizing Unit <regbank>.
    Related source file is "E:\University\Second Year\Computer
Architectures\assessment\MyMicroProcessor\Lab_2\DataPaths - RegBankAlt\otherRegBank.vhd".
Found 16-bit register for signal <REG02>.
Found 16-bit register for signal <REG03>.
Found 16-bit register for signal <REG04>.
Found 16-bit register for signal <REG05>.
Found 16-bit register for signal <REG06>.
Found 16-bit register for signal <REG07>.
Found 16-bit register for signal <REG08>.
Found 16-bit register for signal <REG09>.
Found 16-bit register for signal <REG10>.
Found 16-bit register for signal <REG11>.
Found 16-bit register for signal <REG12>.
Found 16-bit register for signal <REG13>.
Found 16-bit register for signal <REG14>.
Found 16-bit register for signal <REG15>.
Found 16-bit register for signal <REG16>.
Found 16-bit register for signal <REG17>.
Found 16-bit register for signal <REG18>.
Found 16-bit register for signal <REG19>.
Found 16-bit register for signal <REG20>.
Found 16-bit register for signal <REG21>.
Found 16-bit register for signal <REG22>.
Found 16-bit register for signal <REG23>.
Found 16-bit register for signal <REG24>.
Found 16-bit register for signal <REG25>.
Found 16-bit register for signal <REG26>.
Found 16-bit register for signal <REG27>.
Found 16-bit register for signal <REG28>.
Found 16-bit register for signal <REG29>.
Found 16-bit register for signal <REG30>.
Found 16-bit register for signal <REG31>.
Found 16-bit register for signal <REG01>.
Found 16-bit 32-to-1 multiplexer for signal <A> created at line 30.
Found 16-bit 32-to-1 multiplexer for signal <B> created at line 31.
Summary:
    inferred 496 D-type flip-flop(s).
    inferred    2 Multiplexer(s).
Unit <regbank> synthesized.

```

# ===== HDL Synthesis Report

## Macro Statistics

```

# Adders/Subtractors          : 1
  16-bit addsub               : 1
# Registers                   : 35
  16-bit register             : 35
# Comparators                 : 2
  16-bit comparator greater   : 2
# Multiplexers                : 22
  1-bit 2-to-1 multiplexer    : 6
  16-bit 2-to-1 multiplexer   : 14
  16-bit 32-to-1 multiplexer  : 2
# Logic shifters              : 4
  16-bit shifter arithmetic right : 1
  16-bit shifter logical left   : 1
  16-bit shifter rotate left    : 1
  16-bit shifter rotate right   : 1
# Xors                        : 1
  16-bit xor2                  : 1

```

=====

## Test Data for Architecture C

Here is our control logic for Arch C as well as the expected outputs.

	Fetch	Reg Read				ALU+						Mem Acc						Reg Write		
		RA	RB	SEL (6)[7]	SEL (5)[6]	SEL (2)[3:2]	SEL (1)[1:0]	AL	IMM	SH	Flags	MA	M_in	SEL (3)[4]	M_DA	M_out	OEN	WA	W_EN	SEL (4)[5]
inc R1, R0		00000	00000	0	0	01	00	1000	0x0000	0000	01010110	0x0000	0x0000	0	0x0000	0x0000	0	00001	1	1
addi R2, R0, 0x0005		00000	00000	0	0	01	10	1010	0x0005	0000	01010110	0x0000	0x0000	0	0x0000	0x0000	0	00010	1	1
nop																	0		0	
shl R3, R1, 3		00000	00000	1	0	01	00	1100	0x0000	00011	01010110	0x0000	0x0000	0	0x0000	0x0000	0	00011	1	1
storr R2, R3		00000	00000	0	1	11	00	0000	0x0000	0000	01010110	0x0000	0x0000	0	0x0008	0x0005	1	0	0	0
loadi R5, 1f1f		00000	00000	0	0	00	00	0000	0x0000	0000	00000000	0x1f1f	0xCCCC	1	0x1f1f	0x0000	0	00101	1	0

The instruction time line below shows how we used a nop instruction as a pipeline stall between the addi instruction and the shl instruction. We had to use a pipeline stall in this case rather forwarding, as there was no way to use any of the forwarding paths to get the value to be in the correct location at the time when we needed it.

Test command	TimeLine					
inc R1, R0	Fetch	Reg Read	ALU+	Mem Acc	Reg Write	
addi R2, R0, 0x0005		Fetch	Reg Read	ALU+	Mem Acc	Reg Write
nop						
shl R3, R1, 3			Fetch	Reg Read	ALU+	Mem Acc
storr R2, R3				Fetch	Reg Read	ALU+
loadi R5, 1f1f					Fetch	Reg Read

We also used forwarding in our control logic. In fact, the only time we take a value directly from a register is when the value of R Zero is used for the first two instruction. Both the shift left and the store instruction use forwarding in order to execute sooner than they would of other wise.

You can see in the table below that the only time RA has a definite value is during the first two clock cycles. You can also see use of select 5 and 6 to forward data ( that has not yet been write to the register) into the A and B registers. Select 2 has also been used to forward data from the output of the alu back to the input of the alu.

	Fetch	Reg Read				ALU+						Mem Acc						Reg Write		
		RA	RB	SEL (6)[7]	SEL (5)[6]	SEL (2)[3:2]	SEL (1)[1:0]	AL	IMM	SH	Flags	MA	M_in	SEL (3)[4]	M_DA	M_out	OEN	WA	W_EN	SEL (4)[5]
1		00000	00000	0	0	00	00	0000	0x0000	0000	00000000	0x0000	0x0000	0	0x0000	0x0000	0	0	0	0
2		00000	00000	0	0	01	00	1000	0x0000	0000	01010110	0x0000	0x0000	0	0x0000	0x0000	0	0	0	0
3		00000	00000	0	0	01	10	1010	0x0005	0000	01010010	0x0000	0x0000	0	0x0000	0x0000	0	0	0	0
4		00000	00000	1	0	00	00	0000	0x0000	0000	00000000	0x0000	0x0000	0	0x0000	0x0000	0	00001	1	1
5		00000	00000	0	1	01	00	1100	0x0000	00011	01010010	0x0000	0x0000	0	0x0000	0x0000	0	00010	1	1
6		00000	00000	0	0	11	00	0000	0x0000	0000	01010010	0x0000	0x0000	0	0x0000	0x0000	0	0	0	0
7		00000	00000	0	0	00	00	0000	0x0000	0000	00000000	0x0000	0x0000	0	0x0008	0x0005	1	00011	1	1
8		00000	00000	0	0	00	00	0000	0x0000	0000	00000000	0x1f1f	0xCCCC	1	0x1f1f	0x0000	0	0	0	0
9		00000	00000	0	0	00	00	0000	0x0000	0000	00000000	0x0000	0x0000	0	0x0000	0x0000	0	00101	1	0

# Architecture D

## DataPathD.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.DigEng.ALL;

entity DataPath_D is
  Generic(
    data_size : natural := 16;
    num_registers : natural := 32
  );
  Port (
    clk : in STD_LOGIC;
    rst : in STD_LOGIC;
    en : in STD_LOGIC;

    R_A : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Read address A
    R_B : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Read address B
    W_EN : in STD_LOGIC; -- Register write enable

    W_A : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Write address
    IMM : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Immediate value
    M_A : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory address
    M_in : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory input (read)
    SEL : in STD_LOGIC_VECTOR (7 downto 0); -- Selector control
    AL : in STD_LOGIC_VECTOR (3 downto 0); -- ALU control
    SH : in STD_LOGIC_VECTOR (log2(data_size)-1 downto 0); -- Shift amount

    Flags : out STD_LOGIC_VECTOR (7 downto 0); -- ALU flags
    M_DA : out STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory address
    M_out : out STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory output (write)
  );
end DataPath_D;

architecture Behavioral of DataPath_D is

  -- Data to write to the registers
  signal reg_in : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- Outputs of the registers
  signal A_data : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal B_data : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- The two multiplexers for A and B
  signal A_mux : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal B_mux : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- Output of the register on the A and B buses
  signal A_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal B_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- The inputs to the ALU
  signal A_ALU : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal B_ALU : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- The output of the combined ALU and shifter
  signal ALU_out : STD_LOGIC_VECTOR (data_size-1 downto 0);
  signal ALU_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- The ALU output after it passes through a second register
  signal ALU_reg_out_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

  -- Signals for memory registers
  signal M_in_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

begin

  -- The two multiplexers for A and B
  A_mux <= A_data when SEL(7) = '0' else reg_in;
  B_mux <= B_data when SEL(6) = '0' else reg_in;
```

## (Continued.)

```
-- The multiplexers on the input of the ALU
A_ALU <=
    ALU_reg_out      when SEL(3 downto 2) = "11" else
    (others => 'U') when SEL(3 downto 2) = "10" else
    A_reg_out        when SEL(3 downto 2) = "01" else
    reg_in           when SEL(3 downto 2) = "00" else
    (others => 'U');

B_ALU <=
    ALU_reg_out      when SEL(1 downto 0) = "11" else
    IMM              when SEL(1 downto 0) = "10" else
    B_reg_out        when SEL(1 downto 0) = "01" else
    reg_in           when SEL(1 downto 0) = "00" else
    (others => 'U');

-- The address multiplexer for the memory
M_DA <= M_A when SEL(4) = '1' else ALU_reg_out;

-- The register write multiplexer
reg_in <= ALU_reg_out_reg_out when SEL(5) = '1' else M_in_reg_out;

-- The register on the A bus
A_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => A_mux,
    data_out => A_reg_out
);

-- The register on the B bus
B_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => B_mux,
    data_out => B_reg_out
);

-- The Register on the out put of the ALU
ALU_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => ALU_out,
    data_out => ALU_reg_out
);

-- The register on the memory read bus
M_in_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => M_in,
    data_out => M_in_reg_out
);

-- The second register on the ALU out
ALU_reg_out_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => ALU_reg_out,
    data_out => ALU_reg_out_reg_out
);

-- The register on the memory read bus
M_out_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => B_reg_out,
    data_out => M_out
);
```

## (Continued.)

```
-- The ALU
ALU: entity work.ALU_param GENERIC MAP( N => data_size )
PORT MAP(
    A => A_ALU,
    B => B_ALU,
    X => SH,
    ctrl => AL,
    O => ALU_out,
    flags => flags
);

-- The register bank
Registers: entity work.regbank
PORT MAP(
    RSEL_A => R_A,
    RSEL_B => R_B,
    WSEL => W_A,
    D => reg_in,
    WEN => W_EN,
    clk => clk,
    A => A_data,
    B => B_data,
    rst => '0'
);

end Behavioral;
```

# DataPathD-TB.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE work.DigEng.ALL;
USE work.easyprint.ALL;
USE ieee.numeric_std.ALL;

ENTITY DataPathB_TB IS
END DataPathB_TB;

ARCHITECTURE behavior OF DataPathB_TB IS

    -- Constants
    constant data_size : NATURAL := 16;
    constant num_registers : NATURAL := 32;

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT DataPath_B
        GENERIC (
            data_size : natural;
            num_registers : natural
        );
        PORT (
            R_A : IN std_logic_vector(log2(num_registers)-1 downto 0);
            R_B : IN std_logic_vector(log2(num_registers)-1 downto 0);
            W_EN : IN std_logic;
            W_A : IN std_logic_vector(log2(num_registers)-1 downto 0);
            clk : IN std_logic;
            IMM : IN std_logic_vector(data_size-1 downto 0);
            AL : IN std_logic_vector(3 downto 0);
            SH : IN std_logic_vector(log2(data_size)-1 downto 0);
            M_A : IN std_logic_vector(data_size-1 downto 0);
            S : IN std_logic_vector(4 downto 1);
            flags : OUT std_logic_vector(7 downto 0);
            M_B : OUT std_logic_vector(data_size-1 downto 0);
            M_DA : OUT std_logic_vector(data_size-1 downto 0);
            M_in : IN std_logic_vector(data_size-1 downto 0)
        );
    END COMPONENT;

    --Inputs
    signal R_A : std_logic_vector(log2(num_registers)-1 downto 0) := (others => '0');
    signal R_B : std_logic_vector(log2(num_registers)-1 downto 0) := (others => '0');
    signal W_EN : std_logic := '0';
    signal W_A : std_logic_vector(log2(num_registers)-1 downto 0) := (others => '0');
    signal clk : std_logic := '0';
    signal IMM : std_logic_vector(data_size-1 downto 0) := (others => '0');
    signal AL : std_logic_vector(3 downto 0) := (others => '0');
    signal SH : std_logic_vector(log2(data_size)-1 downto 0) := (others => '0');
    signal M_A : std_logic_vector(data_size-1 downto 0) := (others => '0');
    signal S : std_logic_vector(4 downto 1) := (others => '0');
    signal M_in : std_logic_vector(data_size-1 downto 0) := (others => '0');

    --Outputs
    signal flags : std_logic_vector(7 downto 0);
    signal M_B : std_logic_vector(data_size-1 downto 0);
    signal M_DA : std_logic_vector(data_size-1 downto 0);
    signal OEN : std_logic := '0';

    -- Clock period definitions
    constant clk_period : time := 10 ns;
    constant wait_time : time := clk_period;

    -- Test data for self checking test bench
    type TEST_VECTOR is RECORD
        W_EN : std_logic;
        AL : std_logic_vector(3 downto 0);
        R_A : STD_LOGIC_VECTOR(log2(num_registers)-1 downto 0);
        R_B : std_logic_vector(log2(num_registers)-1 downto 0);
        W_A : std_logic_vector(log2(num_registers)-1 downto 0);
```

## (Continued.)

```
    IMM : std_logic_vector(data_size-1 downto 0);
    SH : std_logic_vector(log2(data_size)-1 downto 0) ;
    M_A : std_logic_vector(data_size-1 downto 0);
    S : std_logic_vector(4 downto 1);
    M_in : std_logic_vector(data_size-1 downto 0);

    flags : std_logic_vector(7 downto 0);
    M_B : std_logic_vector(data_size-1 downto 0);
    M_DA : std_logic_vector(data_size-1 downto 0);

    OEN : std_logic;
end RECORD;

type TEST_VECTOR_ARRAY is ARRAY(NATURAL RANGE <>) of TEST_VECTOR;

constant test_vectors : TEST_VECTOR_ARRAY := (
--
    (
        '1', "1000", "00000", "-----", "00001", "-----",
        "-----", "-----", "0---", "-----",
        "01010110", "-----", "-----",
        '0'),

    (
        '1', "1010", "00000", "-----", "00010", "X"0005",
        "-----", "-----", "0--1", "-----",
        "01010010", "-----", "-----",
        '0'),

    (
        '1', "1100", "00001", "-----", "00011", "-----",
        "0011", "-----", "0---", "-----",
        "01010010", "-----", "-----",
        '0'),

    (
        '0', "0000", "00011", "00010", "-----", "-----",
        "-----", "-----", "0---", "-----",
        "01010010", "X"0005", "X"0008",
        '1'),

    (
        '1', "-----", "-----", "-----", "00101", "-----",
        "-----", "X"1f1f", "11--", "X"CCCC",
        "-----", "-----", "X"1f1f",
        '0')
);

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: DataPath_B
  Generic Map(
    data_size => data_size,
    num_registers => num_registers
  )
  PORT MAP (
    R_A => R_A,
    R_B => R_B,
    W_EN => W_EN,
    W_A => W_A,
    clk => clk,
    IMM => IMM,
    AL => AL,
    SH => SH,
    M_A => M_A,
    S => S,
    flags => flags,
    M_B => M_B,
    M_DA => M_DA,
    M_in => M_in
  );
```

## (Continued.)

```
-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin

    -- hold reset state for 100 ns.
    wait for 100 ns;

    -- run the test for every set of data
    for i in test_vectors'range loop

        -- assign test inputs
        R_A <= test_vectors(i).R_A;
        R_B <= test_vectors(i).R_B;
        W_EN <= test_vectors(i).W_EN;
        W_A <= test_vectors(i).W_A;
        IMM <= test_vectors(i).IMM;
        AL <= test_vectors(i).AL;
        SH <= test_vectors(i).SH;
        M_A <= test_vectors(i).M_A;
        S <= test_vectors(i).S;
        M_in <= test_vectors(i).M_in;

        OEN <= test_vectors(i).OEN;

        wait until rising_edge(clk);

        -- Check that the actual outputs are the same as were expecting
        -- Have to use std_match when comparing meta values like '-'
        assert std_match(flags, test_vectors(i).flags)
        report lf & " [ERR!] Test " & integer'image(i) & lf &
            " Actual flags did not equal expected flags."&
            " Actual [ " & to_bstring(flags) & " ]" &
            " Expected [ " & to_bstring(test_vectors(i).flags) & " ]"
        severity error;

        assert std_match(test_vectors(i).M_B, M_B)
        report lf & " [ERR!] Test " & integer'image(i) & lf &
            " Actual value to memory did not equal expected value to memory."&
            " Actual [ " & u_tostr(M_B) & " ]" &
            " Expected [ " & u_tostr(test_vectors(i).M_B) & " ]"
        severity error;

        assert std_match(M_DA , test_vectors(i).M_DA)
        report lf & " [ERR!] Test " & integer'image(i) & lf &
            " Actual memory address did not equal expected memory address."&
            " Actual [ " & u_tostr(M_DA) & " ]" &
            " Expected [ " & u_tostr(test_vectors(i).M_DA) & " ]"
        severity error;

        -- If there were no issues report that the test was successful
        assert not (
            std_match(flags, test_vectors(i).flags) and
            std_match(M_B, test_vectors(i).M_B) and
            std_match(M_DA, test_vectors(i).M_DA))
        report lf & " [ OK ] Test " & integer'image(i) & " was successful!"
        severity note;

        wait until falling_edge(clk);

    end loop;


    wait;

end process;

END;
```



## Simulations

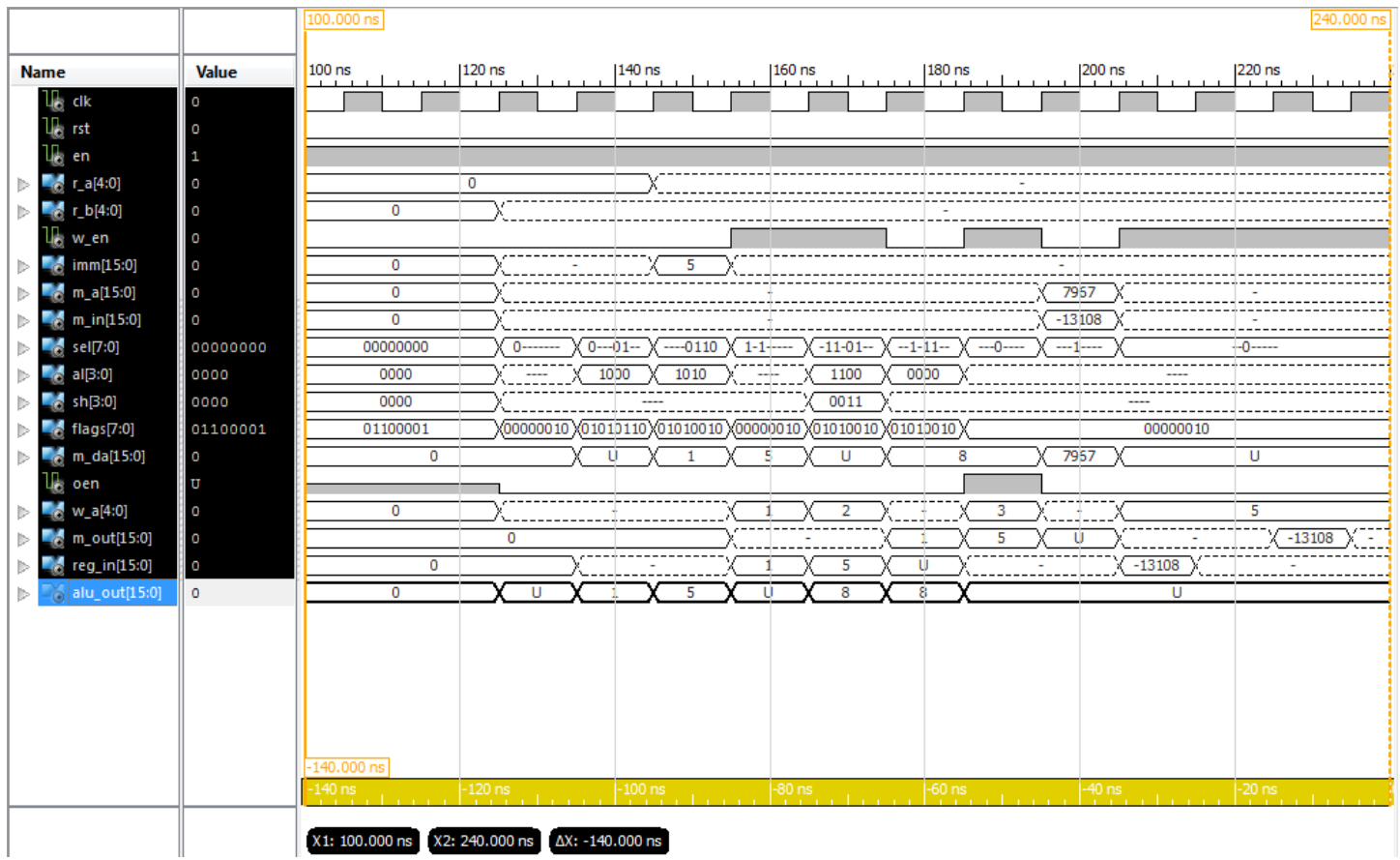

Screenshot showing entire simulation of Architecture D. The signal reg\_in is the data data that will be written to the register bank.

## iSim Console Output

```
ISim P.28xd (signature 0xa0883be4)
This is a Full version of ISim.
Time resolution is 1 ps
WARNING: Simulation object /datapath_d_tb/test_vectors was not traceable in the design for the following reason:
ISim does not yet support tracing of constant and generic multi-dimensional arrays.
Simulator is doing circuit initialization process.
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD.">=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD.">": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD."<": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
at 0 ps, Instance /datapath_d_tb/uut/ALU/ : Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
Finished circuit initialization process.

at 130 ns(1): Note: [ OK ] Test 0 was successful! (/datapath_d_tb/).
at 140 ns(1): Note: [ OK ] Test 1 was successful! (/datapath_d_tb/).
at 150 ns(1): Note: [ OK ] Test 2 was successful! (/datapath_d_tb/).
at 160 ns(1): Note: [ OK ] Test 3 was successful! (/datapath_d_tb/).
at 170 ns(1): Note: [ OK ] Test 4 was successful! (/datapath_d_tb/).
at 180 ns(1): Note: [ OK ] Test 5 was successful! (/datapath_d_tb/).
at 190 ns(1): Note: [ OK ] Test 6 was successful! (/datapath_d_tb/).
at 200 ns(1): Note: [ OK ] Test 7 was successful! (/datapath_d_tb/).
at 210 ns(1): Note: [ OK ] Test 8 was successful! (/datapath_d_tb/).
```

ISim>

*All but the first meta value warnings have been removed to improve readability.*

# HDL Synthesis

```
=====
*                               HDL Synthesis                               *
=====
```

```
Synthesizing Unit <DataPath D>.
  Related source file is "E:\University\Second Year\Computer
Architectures\assessment\MyMicroProcessor\Lab_2\DataPaths - RegBankAlt\DataPath_D.vhd".
  data_size = 16
  num_registers = 32
  Found 16-bit 3-to-1 multiplexer for signal <A ALU> created at line 52.
  Found 16-bit 4-to-1 multiplexer for signal <B ALU> created at line 53.
  Summary:
    inferred 6 Multiplexer(s).
Unit <DataPath_D> synthesized.
```

```
Synthesizing Unit <Reg>.
  Related source file is "E:\University\Second Year\Computer
Architectures\assessment\MyMicroProcessor\Lab_2\DataPaths - RegBankAlt\Reg.vhd".
  data_size = 16
  Found 16-bit register for signal <data_out>.
  Summary:
    inferred 16 D-type flip-flop(s).
Unit <Reg> synthesized.
```

```
Synthesizing Unit <ALU_param>.
  Related source file is "E:\University\Second Year\Computer
Architectures\assessment\MyMicroProcessor\Lab_2\DataPaths - RegBankAlt\ALU_param.vhd".
  N = 16
  Found 16-bit adder for signal <A_itr[15]_B_itr[15]_add_27_OUT> created at line 69.
  Found 16-bit adder for signal <A_itr[15]_GND_7_o_add_31_OUT> created at line 1253.
  Found 16-bit subtractor for signal <A_itr[15]_B_itr[15]_sub_26_OUT<15:0>> created at line 70.
  Found 16-bit subtractor for signal <A_itr[15]_GND_7_o_sub_30_OUT<15:0>> created at line 1320.
  Found 16-bit shifter rotate right for signal <A_itr[15]_X_itr[30]_rotate_right_17_OUT> created at line 3021
  Found 16-bit shifter rotate left for signal <A_itr[15]_X_itr[30]_rotate_left_19_OUT> created at line 3012
  Found 16-bit shifter arithmetic right for signal <A_itr[15]_X_itr[30]_shift_right_21_OUT> created at line 2982
  Found 16-bit shifter logical left for signal <A_itr[15]_X_itr[30]_shift_left_23_OUT> created at line 2973
  Found 16-bit 13-to-1 multiplexer for signal <O_itr> created at line 42.
  Found 16-bit comparator greater for signal <flags<3>> created at line 99
  Found 16-bit comparator greater for signal <flags<4>> created at line 100
  Summary:
    inferred 1 Adder/Subtractor(s).
    inferred 2 Comparator(s).
    inferred 16 Multiplexer(s).
    inferred 4 Combinational logic shifter(s).
Unit <ALU_param> synthesized.
```

```
Synthesizing Unit <regbank>.
  Related source file is "E:\University\Second Year\Computer
Architectures\assessment\MyMicroProcessor\Lab_2\DataPaths - RegBankAlt\otherRegBank.vhd".
  Found 16-bit register for signal <REG02>.
  Found 16-bit register for signal <REG03>.
  Found 16-bit register for signal <REG04>.
  Found 16-bit register for signal <REG05>.
  Found 16-bit register for signal <REG06>.
  Found 16-bit register for signal <REG07>.
  Found 16-bit register for signal <REG08>.
  Found 16-bit register for signal <REG09>.
  Found 16-bit register for signal <REG10>.
  Found 16-bit register for signal <REG11>.
  Found 16-bit register for signal <REG12>.
  Found 16-bit register for signal <REG13>.
  Found 16-bit register for signal <REG14>.
  Found 16-bit register for signal <REG15>.
  Found 16-bit register for signal <REG16>.
  Found 16-bit register for signal <REG17>.
  Found 16-bit register for signal <REG18>.
  Found 16-bit register for signal <REG19>.
  Found 16-bit register for signal <REG20>.
  Found 16-bit register for signal <REG21>.
  Found 16-bit register for signal <REG22>.
  Found 16-bit register for signal <REG23>.
  Found 16-bit register for signal <REG24>.
  Found 16-bit register for signal <REG25>.
  Found 16-bit register for signal <REG26>.
  Found 16-bit register for signal <REG27>.
  Found 16-bit register for signal <REG28>.
  Found 16-bit register for signal <REG29>.
  Found 16-bit register for signal <REG30>.
  Found 16-bit register for signal <REG31>.
```

```
Found 16-bit register for signal <REG01>.
Found 16-bit 32-to-1 multiplexer for signal <A> created at line 30.
Found 16-bit 32-to-1 multiplexer for signal <B> created at line 31.
Summary:
    inferred 496 D-type flip-flop(s).
    inferred 2 Multiplexer(s).
Unit <regbank> synthesized.
```

=====

#### HDL Synthesis Report

```
Macro Statistics
# Adders/Subtractors          : 1
  16-bit addsub                : 1
# Registers                    : 37
  16-bit register              : 37
# Comparators                  : 2
  16-bit comparator greater    : 2
# Multiplexers                 : 24
  1-bit 2-to-1 multiplexer     : 6
  16-bit 2-to-1 multiplexer     : 14
  16-bit 3-to-1 multiplexer     : 1
  16-bit 32-to-1 multiplexer    : 2
  16-bit 4-to-1 multiplexer     : 1
# Logic shifters               : 4
  16-bit shifter arithmetic right : 1
  16-bit shifter logical left    : 1
  16-bit shifter rotate left    : 1
  16-bit shifter rotate right   : 1
# Xors                         : 1
  16-bit xor2                   : 1
```