



UNIVERSITY
of York

Computer Architectures Project


32/16 BIT PROCESSOR

Y3840426 & Y3839090 | ELE00009I | 22/05/2017

Contents

Processor Block Diagram.....	2
Instruction Coding.....	3
Test Program.....	7
VHDL CODE.....	8
Component Simulations.....	64
Top Level Processor Testing.....	70
HDL Synthesis	72
Synthesis Warnings	77
UCF File.....	77

Processor Block Diagram

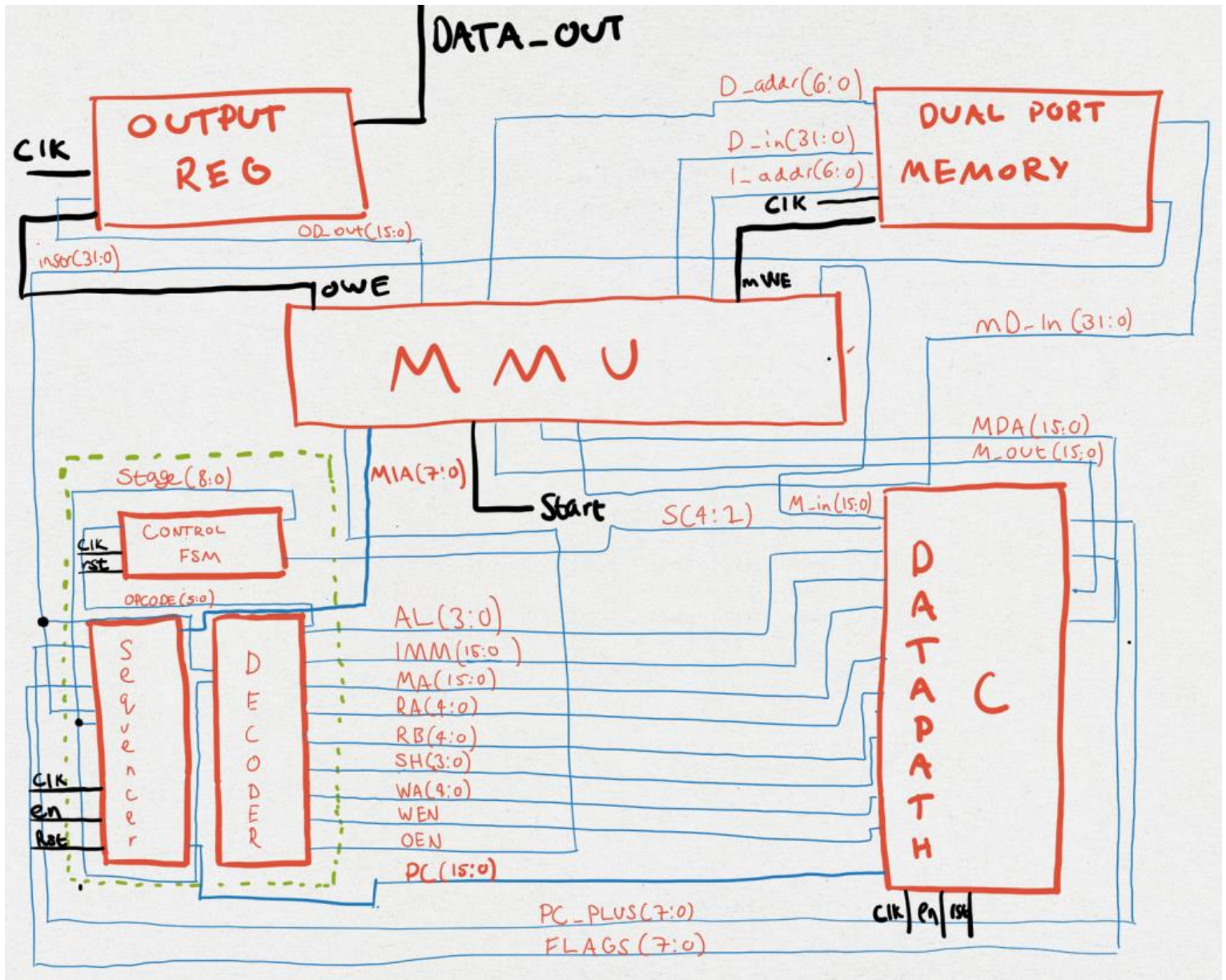

Instruction Coding

There are several things to consider when doing instruction coding. First of all, it must be considered that the instructions need to have a certain amount of uniformity. As seen in the table below displaying our instruction sets, the operands are placed in the same place throughout. This means that it is easier to use them for decoding, as well as allowing for a faster, smaller and more efficient design of processor. Also seen below is that we have split the operands for the instruction from the opcode. This adds to readability of the instruction as the opcode is the first 6 bits that the reader will see.

Another important aspect of the instruction coding is preventing overlap. This is very important as assigning certain bits of an operand to the same location in the instruction as another will cause serious errors in the architecture as the instructions will not be carried through correctly. This is the most important aspect, so if necessary, uniformity can be lost in order to stop overlapping of operands.

One final thing to consider is grouping instructions together that contain the same operands. This is useful as if they have exactly the same operands, they can have exactly the same instruction formations. This is seen in the table below, for example with 'shl/shr/rol/ror'.

add/sub/and/or/xor rt, ra, rb	OPCODE	x	x	x	x	x	B	B	B	B	B	x	x	x	x	x	x	A	A	A	A	A	T	T	T	T	T
inc/dec/not/move/loadr rt,ra ; storr rb,ra	OPCODE	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	A	A	A	A	A	T	T	T	T	T
addi/subi/amdi/ori/xori rt, ra, imm	OPCODE	I	I	I	I	I	I	I	I	I	I	I	I	I	I	I	I	A	A	A	A	A	T	T	T	T	T
shl/shr/rol/ror rt,ra,n	OPCODE	x	x	x	x	x	x	n	n	n	n	x	x	x	x	x	x	A	A	A	A	A	T	T	T	T	T
loadi rt, imm ; stori rb, imm	OPCODE	I	I	I	I	I	I	I	I	I	I	I	I	I	I	I	I	x	x	x	x	x	T/B	T/B	T/B	T/B	T/B
loado rt, ra, off; storo rt, ra, off	OPCODE	x	x	x	x	x	x	O	O	O	O	O	O	O	O	O	O	A	A	A	A	A	T/B	T/B	T/B	T/B	T/B
jmp off	OPCODE	x	O	O	O	O	O	O	O	O	O	O	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x
brc ra, cond, off	OPCODE	x	O	O	O	O	O	O	O	O	O	O	x	x	x	x	x	A	A	A	A	A	x	x	x	x	x

Table showing the instruction sets used

Instruction	OPCODE	STEP	STATE[4,1]	AL	OEN	WEN
add rt, ra, rb	000100	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx00	1010	0	0
		RegWr	0xxx	xxxx	0	1
sub rt, ra, rb	000101	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx00	1011	0	0
		RegWr	0xxx	xxxx	0	1
addi rt, ra, imm	000110	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx01	1010	0	0
		RegWr	0xxx	xxxx	0	1
subi rt, ra, imm	000111	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx01	1011	0	0
		RegWr	0xxx	xxxx	0	1
inc rt, ra	001000	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	1000	0	0
		RegWr	0xxx	xxxx	0	1
dec rt, ra	001001	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	1001	0	0
		RegWr	0xxx	xxxx	0	1
not rt, ra	01 0000	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	0111	0	0
		RegWr	0xxx	xxxx	0	1
and rt, ra, rb	01 0001	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx00	0100	0	0
		RegWr	0xxx	xxxx	0	1
or rt, ra, rb	01 0010	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx00	0101	0	0
		RegWr	0xxx	xxxx	0	1
xor rt, ra, rb	01 0011	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx00	0110	0	0
		RegWr	0xxx	xxxx	0	1
andi rt, ra, imm	01 0100	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx01	0100	0	0
		RegWr	0xxx	xxxx	0	1
ori rt, ra, imm	01 0101	FETCH	xx1x	1000	0	0

		RegRd	xxxx	xxxx	0	0
		ALU	xx01	0101	0	0
		RegWr	0xxx	xxxx	0	1
xori rt, ra, imm	01 0110	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx01	0110	0	0
		RegWr	0xxx	xxxx	0	1
shl rt, ra, n	01 0000	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	1100	0	0
		RegWr	0xxx	xxxx	0	1
shr rt, ra, n	01 1001	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	1101	0	0
		RegWr	0xxx	xxxx	0	1
rotr rt, ra, n	01 1010	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	1110	0	0
		RegWr	0xxx	xxxx	0	1
rotr rt, ra, n	01 1011	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	1111	0	0
		RegWr	0xxx	xxxx	0	1
move rt, ra	10 0000	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	0000	0	0
		RegWr	0xxx	xxxx	0	0
loadi rt, imm	10 0001	FETCH	xx1x	1000	0	0
		MemAcc	x1xx	xxxx	0	0
		RegWr	1xxx	xxxx	0	1
loadr rt, ra	10 0010	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	0000	0	0
		MemAcc	x0xx	xxxx	0	0
		RegWr	1xxx	xxxx	0	1
loado rt, ra, off	10 0011	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx01	1010	0	0
		MemAcc	x0xx	xxxx	0	0
		Regwr	1xxx	xxxx	0	1
stori rb, imm	10 0101	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		MemAcc	x1xx	xxxx	1	0
storr rb, ra	10 0110	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	0000	0	0
		MemAcc	x1xx	xxxx	1	0
storo rb, ra, off	10 0111	FETCH	xx1x	1000	0	0

		RegRd	xxxx	xxxx	0	0
		ALU	xx01	1010	0	0
		MemAcc	x1xx	xxxx	1	0
jmp off	11 0111	FETCH	xx1x	1000	0	0
		ALU	xx11	1010	0	0
brc ra, cond, off	11 0ccc	FETCH	xx1x	1000	0	0
		RegRd	xxxx	xxxx	0	0
		ALU	xx0x	0000	0	0

Table showing the control signals for all instruction types

Category	Instruction	Operands	Opcode
No-operation	nop	N/A	00 0000
Arithmetic	add	rt,ra,rb	00 0100
	sub	rt,ra,rb	00 0101
	addi	rt,ra,imm	00 0110
	subi	rt,ra,imm	00 0111
	inc	rt,ra	00 1000
	dec	rt,ra	00 1001
Logic	not	rt,ra	01 0000
	and	rt,ra,rb	01 0001
	or	rt,ra,rb	01 0010
	xor	rt,ra,rb	01 0011
	andi	rt,ra,imm	01 0100
	ori	rt,ra,imm	01 0101
	xori	rt,ra,imm	01 0110
	shl	rt,ra,n	01 1000
	shr	rt,ra,n	01 1001
	rol	rt,ra,n	01 1010
	ror	rt,ra,n	01 1011
Transfer	move	rt,ra	10 0000
	loadi	rt,imm	10 0001
	loadr	rt,ra	10 0010
	loado	rt,ra,off	10 0011
	stori	rb,imm	10 0101
	storr	rb,ra	10 0110
	storo	rb,ra,off	10 0111
control	jmp	off	11 0111
	brc ra = 0	ra,cond,off	11 0000
	brc ra != 0	ra,cond,off	11 0001
	brc ra = 1	ra,cond,off	11 0010
	brc ra < 0	ra,cond,off	11 0011
	brc ra > 0	ra,cond,off	11 0100
	brc ra <= 0	ra,cond,off	11 0101
	brc ra >= 0	ra,cond,off	11 0101

Table showing Opcodes for every instruction type

Test Program

Assembler

Machine Language (Hexadecimal)

Nop	00000000
loadi r15, h01f0	8407C00F
brz r15, -1	C1FF800F
addi r31, r0, 000000011111	18AD9C1F
add r1, r0, r0	00000001
inc r1, r1	20000021
brlz r31, +5	CC02801F
storr r1, r31	980003E1
inc r1, r1	20000021
dec r31, r31	240003FF
jmp -4 (L1)	1DDFE0000
loadi r2, 00000000000000100	184019002
ori r30, r0, 00000000000000100	15400101E
loadr r3, r30	1880003C3
loado r4, r30, 3	18C000FC4
xori r29, r0, 1111111111111111	15BFFFFC1D
move r7, r0	180000007
andi r5, r29, 0000000000010000	1500043A5
andi r6, r4, 0000000000000001	150000486
brz r6, +2	1C0010006
add r7, r3, r7	200038067
shr r4, r4, 1	264010084
shl r3, r3, 1	260010063
dec r5, r5	2240000A5
brnz r5, -6	2C5FD0005
stori r7, 0	294000007
rol r7, r7, 9	2680900E7
ror r7, r7, 3	26C0300E7
not r8, r7	2400000E8
xor r8, r29, r8	24C0403A8
sub r9, r8, r7	314038109
subi r10, r9, 0000000000000001	31C00052A
brgz r10, +9	3D004800A
brz r10, +8	3C004000A
addi r11, r10, 0000000000000010	31800294B
brz r11, +6	3C003000B
or r12, r7, r11	3480580EC
storo r12, r0, 1	39C00040C
and r12, r12, r11	34405818C
bro r12, =1, +3	3C800800C
jmp +0	4DC000000
jmp +0	4DC000000
stori r7, 000000011111000	4940FFC07
jmp +0	4DC000000

VHDL CODE

PROCESSOR.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- ====
-- Processor
-- Top level schematic that connects all of the main blocks of the
-- CPU together.
-- ====

entity Processor is
    Port (
        clk : in  STD_LOGIC;
        en  : in  STD_LOGIC;
        rst : in  STD_LOGIC;

        start : in  STD_LOGIC;
        data_out : out STD_LOGIC_VECTOR (15 downto 0)
    );
end Processor;

architecture Behavioral of Processor is

    --signal data_in : STD_LOGIC_VECTOR(15 downto 0);
    signal mWE : STD_LOGIC;
    signal oWE : STD_LOGIC;
    signal mDAddress : STD_LOGIC_VECTOR(6 downto 0);
    signal DPD_out : STD_LOGIC_VECTOR(31 downto 0);
    signal DPD_in : STD_LOGIC_VECTOR(31 downto 0);
    signal I_addr : STD_LOGIC_VECTOR(6 downto 0);
    signal I_out : STD_LOGIC_VECTOR(31 downto 0);
    signal oD_out : STD_LOGIC_VECTOR(15 downto 0);
    signal Instr_Addr : STD_LOGIC_VECTOR(7 downto 0);

    signal D_addr : STD_LOGIC_VECTOR(6 downto 0);

    signal Flags : STD_LOGIC_VECTOR(7 downto 0);
    signal PC : STD_LOGIC_VECTOR(7 downto 0);
    signal S : STD_LOGIC_VECTOR (4 downto 1);
    signal RA : STD_LOGIC_VECTOR (4 downto 0);
    signal RB : STD_LOGIC_VECTOR (4 downto 0);
    signal WA : STD_LOGIC_VECTOR (4 downto 0);
    signal MA : STD_LOGIC_VECTOR (15 downto 0);
    signal IMM : STD_LOGIC_VECTOR (15 downto 0);
    signal AL : STD_LOGIC_VECTOR (3 downto 0);
    signal SH : STD_LOGIC_VECTOR (3 downto 0);

    signal OEN : STD_LOGIC;
    signal WEN : STD_LOGIC;
```

```

signal MDA : STD_LOGIC_VECTOR (15 downto 0);
signal M_in : STD_LOGIC_VECTOR (15 downto 0);
signal M_out : STD_LOGIC_VECTOR (15 downto 0);

signal PC_PLUS_16 : STD_LOGIC_VECTOR(15 downto 0) := (others => '0' );
signal PC_16 : STD_LOGIC_VECTOR(15 downto 0) := (others => '0' );
signal PC_PLUS : STD_LOGIC_VECTOR(7 downto 0);

```

begin

```

Inst_OutputReg: entity work.OutputReg PORT MAP(
    clk => clk,
    data_in => oD_out,
    WE => oWE,
    data_out => data_out
);

```

--DUAL PORT MEMORY

```

Inst_DualPortMemory: entity work.DualPortMemory PORT MAP(
    clk => clk,
    I_addr => I_addr,
    D_addr => mDAddress,
    D_in => DPD_in,
    WE => mWE,
    D_out => DPD_out,
    I_out => I_out
);

```

-- MMU

```

Inst_MMU: entity work.MMU PORT MAP(
    I_addr => Instr_addr,
    OEn => OEN,
    D_in => M_out,
    D_out => M_in,
    D_addr => MDA,
    start => start,
    oWE => oWE,
    oD_out => oD_out,
    mWE => mWE,
    mD_addr => mDAddress,
    mD_in => DPD_out,
    mD_out => DPD_in,
    mI_addr => I_addr
);

```

```

Inst_DataPath_C: entity work.DataPath_C PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    R_A => RA,
    R_B => RB,
    W_EN => WEN,
    W_A => WA,
    IMM => IMM,
    M_A => MA,
    M_in => M_in,
    PC => PC_16,
    S => S,
    AL => AL,
    SH => SH,

```

```

    PC_plus => PC_Plus_16,
    Flags => Flags,
    M_DA => MDA,
    M_out => M_out
);
PC_16(7 downto 0) <= PC;
PC_Plus <= PC_Plus_16(7 downto 0);

Inst_ControlUnit: entity work.ControlUnit PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    PC_Plus => PC_Plus,
    instr => I_out,
    Flags => Flags,
    Instr_addr => Instr_addr,
    PC => PC,
    S => S,
    RA => RA,
    RB => RB,
    WA => WA,
    MA => MA,
    IMM => IMM,
    AL => AL,
    SH => SH,
    WEN => WEN,
    OEN => OEN
);

```

```

end Behavioral;

```

OUTPUTREG.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- ====
-- OutputReg
-- A simple 16bit register
-- ====

entity OutputReg is
  Port (
    clk : in STD_LOGIC;
    data_in : in STD_LOGIC_VECTOR (15 downto 0);
    WE : in STD_LOGIC;
    data_out : out STD_LOGIC_VECTOR (15 downto 0)
  );
end OutputReg;

architecture Behavioral of OutputReg is

begin

  -- simple register proccess

  update : process(clk, WE)
  begin
    if (rising_edge(clk) and WE = '1') then
      data_out <= data_in;
    end if;
  end process;

end Behavioral;
```

DUALPORTMEMORY.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
USE ieee.numeric_std.ALL;

-- ====
-- DualPortMemory
-- A Dual ASync read, single Sync write RAM block. With 128, 32 bit words.
-- Pre loaded with the instruction data.
-- ====
entity DualPortMemory is
    Port (
        clk : in std_logic; -- clock
        I_addr : in STD_LOGIC_VECTOR (6 downto 0); -- Instruction read address
        D_addr : in STD_LOGIC_VECTOR (6 downto 0); -- Data address
        D_in : in STD_LOGIC_VECTOR (31 downto 0); -- Data to write
        WE : in STD_LOGIC; -- Data write enable
        D_out : out STD_LOGIC_VECTOR (31 downto 0); -- Data output
        I_out : out STD_LOGIC_VECTOR (31 downto 0) -- Instruction output
    );
end DualPortMemory;

architecture Behavioral of DualPortMemory is
    type ram_type is array (0 to (2**7)-1) of std_logic_vector(31 downto 0);
    signal ram : ram_type := (
-- simple branches test program
        0 => X"00000000",
        1 => X"00000000",
        2 => X"CDF8000",
        3 => X"00000000",
        4 => X"C1FF8000",

-- simple adds test program
        0 => X"00000000",
        1 => X"18003C01",
        2 => X"00000000",
        3 => X"00000022",
        4 => X"C1FF8002",

-- main test program
        0 => X"00000000",
        1 => X"8407C00F",
        2 => X"C1FF800F",
        3 => X"18007C1F",
        4 => X"00000001",
        5 => X"20000021",
        6 => X"CC02801F",
        7 => X"980003E1",
        8 => X"20000021",
        9 => X"240003FF",
        10 => X"DDFE0000",
        11 => X"84019002",
        12 => X"5400101E",
        13 => X"880003C3",
        14 => X"8C000FC4",
```

```

15 => X"5BFFFC1D",
16 => X"80000007",
17 => X"500043A5",
18 => X"50000486",
19 => X"C0010006",
20 => X"00038067",
21 => X"64010084",
22 => X"60010063",
23 => X"240000A5",
24 => X"C5FD0005",
25 => X"94000007",
26 => X"680900E7",
27 => X"6C0300E7",
28 => X"400000E8",
29 => X"4C0403A8",
30 => X"14038109",
31 => X"1C00052A",
32 => X"D004800A",
33 => X"C004000A",
34 => X"1800294B",
35 => X"C003000B",
36 => X"480580EC",
37 => X"9C00040C",
38 => X"4405818C",
39 => X"C800800C",
40 => X"DC000000",
41 => X"DC000000",
42 => X"940FFC07",
43 => X"DC000000",
others => X"00000000"
);
begin

-- Instruction reads
I_out <= ram(to_integer(unsigned(I_addr)));

-- Data reads
D_out <= ram(to_integer(unsigned(D_addr)));

-- Data writes
write_proc : process(clk, WE)
begin
    if (rising_edge(clk) and WE = '1') then
        ram(to_integer(unsigned(D_addr))) <= D_in;
    end if;
end process;

end Behavioral;

```

MMU.VHD

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

-- ====
-- MMU
-- The memory management unit is responsible for mapping the datapath's full 16 bit
-- Addresses to the hardware's smaller address space and memory mapped peripherals
-- ====

entity MMU is
  Port (
    I_addr : in  STD_LOGIC_VECTOR (7 downto 0); -- Instruction address from control
unit

    OEn : in  STD_LOGIC; -- Memory write enable from data path
    D_in : in  STD_LOGIC_VECTOR (15 downto 0); -- data in from datapath
    D_out : out STD_LOGIC_VECTOR (15 downto 0); -- data out to datapath
    D_addr : in  STD_LOGIC_VECTOR (15 downto 0); -- data address from datapath

    start : in  STD_LOGIC; -- memory mapped push button

    oWE : out STD_LOGIC; -- GPIO write enable
    oD_out : out STD_LOGIC_VECTOR (15 downto 0); -- data out to GPIO

    mWE : out STD_LOGIC; -- Physical memory write enable
    mD_addr : out STD_LOGIC_VECTOR (6 downto 0); -- Physical memory address
    mD_in : in  STD_LOGIC_VECTOR (31 downto 0); -- data in from physical memory
    mD_out : out STD_LOGIC_VECTOR (31 downto 0); -- data out to physical memory
    mI_addr : out STD_LOGIC_VECTOR (6 downto 0) -- instruction address for physical
memory

  );
end MMU;

architecture Behavioral of MMU is
  signal to_write : STD_LOGIC_VECTOR (31 downto 0);

  signal isMemAccess : STD_LOGIC;
begin

  -- Flag that determines whether this will be an access to physical memory
  isMemAccess <=
    '1' when unsigned(D_addr) >= 64 and unsigned(D_addr) < 64+(64*2) else
    '0';

  --Instructions
  mI_addr <= I_addr(6 downto 0);

  -- Output Reg
  oD_out <= D_in;
  oWE <= '1' when D_addr = X"01F8" and OEn = '1' else '0';

  -- Data to write to memory
```

```

to_write(31 downto 16) <=
  D_in when D_addr(0) = '0' else
  mD_in(31 downto 16);

to_write(15 downto 0) <=
  D_in when D_addr(0) = '0' else
  mD_in(15 downto 0);

-- map internal signal to output
mD_out <= to_write;

-- if its a memory access and datapath wants to write then set the physical memorys
write enable
mWE <=
  '1' when isMemAccess = '1' and OEn = '1' else
  '0';

-- set the physical memorys write enable
mD_addr <= std_logic_vector(unsigned(D_addr(7 downto 1)) + to_unsigned(64,7));

-- Data to processor
D_out <=
  mD_in(31 downto 16)      when isMemAccess = '1' and D_addr(0) = '1' else
  mD_in(15 downto 0)      when isMemAccess = '1' and D_addr(0) = '0' else
  X"ffff"                when D_addr = X"01F0" and start = '1'      else
  X"0000"                when D_addr = X"01F0" and start = '0'      else
  (others => 'U');

end Behavioral;

```


CONTROLFSM.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- ====
-- ControlFSM
-- The finite state machine that controls which stage of instruction processing
-- We are currently in. As well as deciding which stages of processing the
-- current instruction need to pass through. It also provide the STAGE and S
-- flags used else where in the CPU
-- ====

entity ControlFSM is
    Port (
        clk : in  STD_LOGIC; -- clock
        rst : in  STD_LOGIC; -- active high sync reset
        opcode : in  STD_LOGIC_Vector(5 downto 0); -- the opcode of the current
instruction
        S : out  STD_LOGIC_VECTOR (4 downto 1); -- Selection flags which control
multiplexers in the data path
        STAGE : out  STD_LOGIC_VECTOR(8 downto 0) -- The current stage of execution
    );
end ControlFSM;

architecture Behavioral of ControlFSM is

    type STATE_TYPE is ( S0, S1, S2, S3, S4, S5, S6, S7, S8);
    signal curr_state, next_state: STATE_TYPE;

    signal optype : STD_LOGIC_VECTOR(1 downto 0);

begin

    -- The next state assignment process for this FSM
    restart : process(clk,rst) is
    begin
        if rising_edge(clk) then
            if (rst='1') then -- sync reset
                curr_state <= S0; -- S0 is the reset state
            else
                curr_state <= next_state; -- if were not resetting move to the next state
            end if;
        end if;
    end process;

    -- The next state calculation process
    control : process(curr_state, opcode, optype) is
    begin

        -- Top two bits of the opcode tell us which type of instruction this is.
        -- e.g. arithmetic or branch
        optype <= opcode(opcode'length -1 downto opcode'length -2);

        -- Decide on what the next state is based of of the opcode and optype
        case curr_state is
            when S0 =>
```

```

        next_state <= S1;
    when S1 =>
        if (optype = "11") then
            -- Branch
            next_state <= S8;
        elsif (optype = "10") then
            -- Memory
            next_state <= S4;
        else
            -- Registers
            next_state <= S2;
        end if;
    when S2 =>
        next_state <= S3;
    when S3 =>
        next_state <= S0;
    when S4 =>
        if (opcode(1) = '1') then
            -- Store
            next_state <= S5;
        else
            -- Load
            next_state <= S6;
        end if;
    when S5 =>
        next_state <= S0;
    when S6 =>
        next_state <= S7;
    when S7 =>
        next_state <= S0;
    when S8 =>
        next_state <= S0;
    end case;
end process;

-- Set the bit flags for the STAGE signal
STAGE(0) <= '1' when curr_state = S0 else '0';
STAGE(1) <= '1' when curr_state = S1 else '0';
STAGE(2) <= '1' when curr_state = S2 else '0';
STAGE(3) <= '1' when curr_state = S3 else '0';
STAGE(4) <= '1' when curr_state = S4 else '0';
STAGE(5) <= '1' when curr_state = S5 else '0';
STAGE(6) <= '1' when curr_state = S6 else '0';
STAGE(7) <= '1' when curr_state = S7 else '0';
STAGE(8) <= '1' when curr_state = S8 else '0';

-- Set the flags for the select (S) signal
S(1) <=
    '-' when curr_state = S0 else
    '-' when curr_state = S1 and optype /= "11" else
    '1' when curr_state = S1 and optype = "11" else
    '0' when curr_state = S2 else
    '-' when curr_state = S3 else
    '1' when curr_state = S4 else
    '-' when curr_state = S5 else
    '-' when curr_state = S6 else
    '0' when curr_state = S7 else
    '0' when curr_state = S8 else
    'X';

S(2) <=

```

```

'1' when curr_state = S0 else
'-' when curr_state = S1 and optype /= "11" else
'1' when curr_state = S1 and optype = "11" else
'0' when curr_state = S2 else
'0' when curr_state = S3 else
'0' when curr_state = S4 else
'-' when curr_state = S5 else
'-' when curr_state = S6 else
'0' when curr_state = S7 else
'0' when curr_state = S8 else
'X';

```

```

S(3) <= '1' when opcode = "100001" and curr_state = S7 else
        '1' when opcode = "100101" and curr_state = S7 else
        '0';

```

```

S(4) <=
'-' when curr_state = S0 else
'-' when curr_state = S1 else
'0' when curr_state = S2 else
'0' when curr_state = S3 else
'-' when curr_state = S4 else
'-' when curr_state = S5 else
'1' when curr_state = S6 else
'-' when curr_state = S7 else
'-' when curr_state = S8 else
'X';

```

```

end Behavioral;

```

SEQUENCER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- ====
-- Sequencer
-- Decides on what instruction to execute next.
-- Handles branches and incrementing the PC
-- ====

entity Sequencer is
    Port (
        clk : in  STD_LOGIC; -- clock
        rst : in  STD_LOGIC; -- active high sync reset
        en : in  STD_LOGIC; -- enable
        STAGE : in  STD_LOGIC_VECTOR(8 downto 0); -- stage of execution flags
        instr : in  STD_LOGIC_VECTOR(31 downto 0); -- instruction
        PC_plus : in  STD_LOGIC_VECTOR(7 downto 0); -- PC + offset
        flags : in  STD_LOGIC_VECTOR(7 downto 0); -- flags
        PC : out  STD_LOGIC_VECTOR(7 downto 0); -- program counter
        MIA : out  STD_LOGIC_VECTOR(7 downto 0) -- memory address of instruction
    );
end Sequencer;

architecture Behavioral of Sequencer is
    signal PC_internal : STD_LOGIC_VECTOR(7 downto 0) := (others => '0'); -- current
    internal PC state
    signal PC_next : STD_LOGIC_VECTOR(7 downto 0); -- the next PC state

    signal cond_met : STD_LOGIC; -- whether the branching condition has been met

    signal opcode : STD_LOGIC_VECTOR(5 downto 0); -- the opcode part of the instruction
    signal cond : STD_LOGIC_VECTOR(2 downto 0); -- the condition part of the opcode

    signal cond_met_i : STD_LOGIC;
begin

    -- assign opcode and cond from the instruction
    opcode <= instr(31 downto 26);
    cond <= opcode(2 downto 0);

    -- Calculate whether the condition to branch has been met
    cond_met <=
        '1' when cond = "000" and flags(0) = '1' and STAGE(8) = '1' else -- ra = 0
        '1' when cond = "001" and flags(1) = '1' and STAGE(8) = '1' else -- ra != 0
        '1' when cond = "010" and flags(2) = '1' and STAGE(8) = '1' else -- ra = 1
        '1' when cond = "011" and flags(4) = '1' and STAGE(8) = '1' else -- ra < 0
        '1' when cond = "100" and flags(3) = '1' and STAGE(8) = '1' else -- ra > 0
        '1' when cond = "101" and flags(6) = '1' and STAGE(8) = '1' else -- ra <= 0
        '1' when cond = "110" and flags(5) = '1' and STAGE(8) = '1' else -- ra >= 0
        '1' when cond = "111" else -- jump
        '0';

    -- map internal signals to outputs
    PC <= PC_internal;
    MIA <= PC_internal;
```

```

-- The Instruction register update process
register_proc : process(clk, rst, en, STAGE, cond_met, opcode) is
begin
    if rising_edge(clk) then
        if rst = '1' then
            PC_internal <= (others => '0');
        elsif en = '1' and STAGE(0) = '1' then
            if opcode(5 downto 4) = "11" and cond_met_i = '1' then
                PC_internal <= PC_next;
            else
                PC_internal <= std_logic_vector(unsigned(PC_internal) + 1);
            end if;
        end if;
    end if;
end process;

-- Add a register for PC_PLUS so we can keep the value until after
-- the condition is evaluated.
stick_proc : process(clk, PC_plus, STAGE) is
begin
    if rising_edge(clk) and STAGE(8) = '1' then
        PC_next <= PC_plus;
    end if;
end process;

-- Add a register for cond met so we can keep the value until we need
-- to branch.
met_proc : process(clk, cond_met, STAGE) is
begin
    if rising_edge(clk) and STAGE(8) = '1' then
        cond_met_i <= cond_met;
    end if;
end process;

end Behavioral;

```

DECODER

```
library IEEE;
USE ieee.numeric_std.ALL;
use IEEE.STD_LOGIC_1164.ALL;

-- ====
-- Decoder
-- Decode from the current instruction to STAGE to the
-- Individual control signals need to drive the datapath.
-- ====

entity Decoder_Block is
  Port (
    instr : in  STD_LOGIC_VECTOR (31 downto 0); -- Instruction

    STAGE : in  STD_LOGIC_VECTOR(8 downto 0); -- Current stage flags
    OPCODE : out STD_LOGIC_VECTOR(5 downto 0); -- Opcode from instruction

    RA : out  STD_LOGIC_VECTOR (4 downto 0); -- Index of working register A
    RB : out  STD_LOGIC_VECTOR (4 downto 0); -- Index of working register B
    WA : out  STD_LOGIC_VECTOR (4 downto 0); -- Index of register to be written to.

    MA : out  STD_LOGIC_VECTOR (15 downto 0); -- Memory address from instruction.
    IMM : out  STD_LOGIC_VECTOR (15 downto 0); -- Intermediate value form
  instruction

    AL : out  STD_LOGIC_VECTOR (3 downto 0); -- Control code of the ALU
    SH : out  STD_LOGIC_VECTOR (3 downto 0); -- Amount of shift by

    WEN : out  STD_LOGIC; -- Write enable for the registers
    OEN : out  STD_LOGIC; -- Write enable for the memory
  );
end Decoder_Block;

architecture Behavioral of Decoder_Block is
  signal OPCODE_int : STD_LOGIC_VECTOR(5 downto 0);

  signal IMM_internal : STD_LOGIC_VECTOR(15 downto 0);

  signal InstrInternal1 : std_logic_vector(IMM_internal'range) := (others => '0');
  signal InstrInternal2 : std_logic_vector(IMM_internal'range) := (others => '0');
begin

  -- grab the opcode part of the instruction
  OPCODE_int <= instr(31 downto 26);

  -- map internal signal to output
  OPCODE <= OPCODE_int;

  -- RA and WA are always in the same place
  -- so they can be assigned with no logic
  RA <= instr(9 downto 5);
  WA <= instr(4 downto 0);

  -- RB moves so it needs
  RB <=
    instr(20 downto 16) when OPCODE_int(5 downto 4) = "00" else
```

```

instr(4 downto 0);

-- The IMM/Offset is the most variable of the data that is encoded into the
-- Instructions. it also changes it size. SO it has the most complicated decode
-- Logic
InstrInternal1 <= std_logic_vector(resize(signed(instr(19 downto 10)), 16));
InstrInternal2 <= std_logic_vector(resize(signed(instr(24 downto 16)), 16));

IMM_internal <=
  InstrInternal1 when OPCODE_int(5 downto 4) = "10" and OPCODE_int(1 downto 0) =
"11" else
  InstrInternal2 when OPCODE_int(5 downto 4) = "11" else
  instr(25 downto 10);

-- Map internal signals to the ouputs
IMM <= IMM_internal;
MA <= IMM_internal;

-- The instruction coding given to cannot be directly mapped to the
AL <=
  "1010" when STAGE(1) = '1' else -- calc branch
  "1010" when STAGE(8) = '1' else -- calc branch
  "0100" when OPCODE_int(5 downto 3) = "010" and OPCODE_int(1 downto 0) = "01"
else -- A & B
  "0101" when OPCODE_int(5 downto 3) = "010" and OPCODE_int(1 downto 0) = "10"
else -- A || B
  "0110" when OPCODE_int(5 downto 3) = "010" and OPCODE_int(1 downto 0) = "11"
else -- A xor B
  "0111" when OPCODE_int(5 downto 3) = "010" and OPCODE_int(1 downto 0) = "00"
else -- not A
  "1000" when OPCODE_int(5 downto 4) = "00" and OPCODE_int(3) = '1' and
OPCODE_int(4) = '0' else -- A + 1
  "1001" when OPCODE_int(5 downto 4) = "00" and OPCODE_int(3) = '1' and
OPCODE_int(4) = '0' else -- A - 1
  "1010" when OPCODE_int(5 downto 4) = "00" and OPCODE_int(2) = '1' and
OPCODE_int(0) = '0' else -- A + B
  "1011" when OPCODE_int(5 downto 4) = "00" and OPCODE_int(2) = '1' and
OPCODE_int(0) = '1' else -- A - B
  "1100" when OPCODE_int(5 downto 3) = "011" and OPCODE_int(2 downto 0) = "000"
else -- A sla X
  "1101" when OPCODE_int(5 downto 3) = "011" and OPCODE_int(2 downto 0) = "001"
else -- A sra X
  "1110" when OPCODE_int(5 downto 3) = "011" and OPCODE_int(2 downto 0) = "010"
else -- A rotl X
  "1111" when OPCODE_int(5 downto 3) = "011" and OPCODE_int(2 downto 0) = "011"
else -- A rotr X
  "0000"; -- A

-- Get the amount ot shift by.
SH <= instr(19 downto 16);
-- OEN is high for any opcode starting with 1001, i.e store instructions
OEN <=
  '1' when OPCODE_int(5 downto 2) = "1001" else
  '0';

-- Write enable is high for certian stages of exicution
WEN <=
  '1' when STAGE(3) = '1' else
  '1' when STAGE(7) = '1' else
  '0';

```

```
end Behavioral;
```

CONTROL UNIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- ====
-- ControlUnit
-- The main control unit for the processor.
-- Contains the decode, instruction register, sequencer and FSM.
-- ====

entity ControlUnit is
    Port (

        clk : in std_logic; -- clock
        rst : in std_logic; -- sync active high reset
        en : in STD_LOGIC; -- active high enable

        PC_Plus : in STD_LOGIC_VECTOR(7 downto 0); -- the PC plus offset
        instr : in STD_LOGIC_VECTOR (31 downto 0); -- the current instruction
        Flags : in STD_LOGIC_VECTOR(7 downto 0); -- the flags from the ALU

        Instr_addr : out STD_LOGIC_VECTOR (7 downto 0); -- The address of the next
instruction
        PC : out STD_LOGIC_VECTOR(7 downto 0); -- The program counter

        S : out STD_LOGIC_VECTOR (4 downto 1); -- Selects for the ALU multiplexers

        RA : out STD_LOGIC_VECTOR (4 downto 0); -- Index of working register A
        RB : out STD_LOGIC_VECTOR (4 downto 0); -- Index of working register B
        WA : out STD_LOGIC_VECTOR (4 downto 0); -- Index of working register to be
written to (Rt)

        MA : out STD_LOGIC_VECTOR (15 downto 0); -- Memory address from instruction
        IMM : out STD_LOGIC_VECTOR (15 downto 0); -- Intermediate value from
instruction

        AL : out STD_LOGIC_VECTOR (3 downto 0); -- The ALU control code
        SH : out STD_LOGIC_VECTOR (3 downto 0); -- The amount of bits to shift by

        WEN : out STD_LOGIC; -- Write enable for the registers
        OEN : out STD_LOGIC -- Write enable for the memory
    );
end ControlUnit;

architecture Behavioral of ControlUnit is

    signal OPCODE : STD_LOGIC_VECTOR (5 downto 0);

    signal STAGE : STD_LOGIC_VECTOR (8 downto 0);
begin

    -- The control FSM
    Inst_ControlFSM: entity work.ControlFSM PORT MAP(
        clk => clk ,
```



```

        rst => rst,
        opcode => OPCODE ,
        S => S,
        STAGE => STAGE
    );

-- The PC sequencer
Inst_Sequencer: entity work.Sequencer PORT MAP(
    clk => clk ,
    rst => rst,
    en => en,
    STAGE => STAGE,
    instr => instr ,
    PC_plus => PC_Plus,
    flags => Flags,
    PC => PC,
    MIA => Instr_addr
);

-- The combonational decoder
Inst_Decoder_Block: entity work.Decoder_Block PORT MAP(
    instr => instr,
    STAGE => STAGE,
    OPCODE => OPCODE,
    RA => RA,
    RB => RB,
    WA => WA,
    MA => MA,
    IMM => IMM,
    AL => AL,
    SH => SH,
    WEN => WEN,
    OEN => OEN
);

end Behavioral;

```

DATAPATHC.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.DigEng.ALL;

entity DataPath_C is
    GENERIC(
        data_size : natural := 16;
        num_registers : natural := 32
    );
    Port (
        clk : in STD_LOGIC;
        rst : in STD_LOGIC;
        en : in STD_LOGIC;

        -- Inputs
        R_A : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Read address A
        R_B : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Read address B
        W_EN : in STD_LOGIC; -- Register write
enable
        W_A : in STD_LOGIC_VECTOR (log2(num_registers)-1 downto 0); -- Write address

        IMM : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Immediate
value
        M_A : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory address
        M_in : in STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory input
(read)
        PC : in STD_LOGIC_VECTOR (15 downto 0); -- Current Program
Counter
        S : in STD_LOGIC_VECTOR (4 downto 1); -- Selector control
        AL : in STD_LOGIC_VECTOR (3 downto 0); -- ALU control
        SH : in STD_LOGIC_VECTOR (log2(data_size)-1 downto 0); -- Shift amount

        -- Outputs
        PC_plus : out STD_LOGIC_VECTOR (15 downto 0); -- Next Program
Counter
        Flags : out STD_LOGIC_VECTOR (7 downto 0); -- ALU flags
        M_DA : out STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory address
        M_out : out STD_LOGIC_VECTOR (data_size-1 downto 0); -- Memory output
(write)
    );
end DataPath_C;

architecture Behavioral of DataPath_C is

    -- Data to write to the registers
    signal reg_in : STD_LOGIC_VECTOR (data_size-1 downto 0);

    -- Outputs of the registers
    signal A_data : STD_LOGIC_VECTOR (data_size-1 downto 0);
    signal B_data : STD_LOGIC_VECTOR (data_size-1 downto 0);

    -- Output of the register on the A and B buses
    signal A_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);
    signal B_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

```

```

-- The Outputs of the two Muxes on the input to the ALU
signal A_mux : STD_LOGIC_VECTOR (data_size-1 downto 0);
signal B_mux : STD_LOGIC_VECTOR (data_size-1 downto 0);

-- The output of the combined ALU and shifter
signal ALU_out : STD_LOGIC_VECTOR (data_size-1 downto 0);
signal ALU_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

-- The output of the memory in register
signal M_in_reg_out : STD_LOGIC_VECTOR (data_size-1 downto 0);

```

begin

```

-- The two multiplexers on the input to the ALU
A_mux <= A_reg_out when S(2) = '0' else PC;
B_mux <= B_reg_out when S(1) = '0' else IMM;

-- The address multiplexer for the memory
M_DA <= M_A when s(3) = '1' else ALU_reg_out;

M_out <= B_reg_out;
PC_plus <= ALU_reg_out;

-- The register write multiplexer
reg_in <= ALU_reg_out when s(4) = '0' else M_in_reg_out;

-- The register on the A bus
A_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => A_data,
    data_out => A_reg_out
);

-- The register on the B bus
B_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => B_data,
    data_out => B_reg_out
);

-- The Register on the out put of the ALU
ALU_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,
    rst => rst,
    en => en,
    data_in => ALU_out,
    data_out => ALU_reg_out
);

-- The register on the memory read bus
M_in_reg: entity work.Reg Generic Map (data_size => data_size)
PORT MAP(
    clk => clk,

```

```

    rst => rst,
    en => en,
    data_in => M_in,
    data_out => M_in_reg_out
);

-- The ALU and shifter from Lab 1
ALU: entity work.ALU_param GENERIC MAP( N => data_size )
PORT MAP(
    A => A_mux,
    B => B_mux,
    X => SH,
    ctrl => AL,
    O => ALU_out,
    flags => flags
);

-- The register bank
Registers: entity work.regbank
PORT MAP(
    RSELA => R_A,
    RSELB => R_B,
    WSEL => W_A,
    D => reg_in,
    WEN => W_EN,
    clk => clk,
    A => A_data,
    B => B_data,
    rst => '0'
);

end Behavioral;
```

REG.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- A parameterisable synchronous reset D-type registers with enable
entity Reg is
  Generic(
    data_size: natural := 8 -- How many bits will the register deal with
  );
  Port (
    clk : in  STD_LOGIC;
    rst : in  STD_LOGIC; -- synchronus reset
    en  : in  STD_LOGIC; -- synchronus reset
    data_in : in  STD_LOGIC_VECTOR (data_size-1 downto 0); -- input
    data_out : out STD_LOGIC_VECTOR (data_size-1 downto 0) -- output
  );
end Reg;

architecture Behavioral of Reg is
begin

  process(clk)
  begin
    -- Synchronise to the clock
    if (rising_edge(clk)) then
      if (rst = '1') then
        -- Reset to zero
        data_out <= (others => '0');
      elsif (en = '1') then
        -- Pass the input to the output
        data_out <= data_in;
      end if;
    end if;

  end process;

end Behavioral;
```

OTHERREGBANK.VHD

```
-----
-- Company:
-- Engineer:
--
-- Create Date:      18:20:58 02/23/2009
-- Design Name:
-- Module Name:      regbank - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

---- Uncomment the following library declaration if instantiating
---- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity regbank is
    Port ( A : out  STD_LOGIC_VECTOR (15 downto 0);
          B : out  STD_LOGIC_VECTOR (15 downto 0);
          RSELA : in  STD_LOGIC_VECTOR (4 downto 0);
          RSELB : in  STD_LOGIC_VECTOR (4 downto 0);
          D : in  STD_LOGIC_VECTOR (15 downto 0);
          WSEL : in  STD_LOGIC_VECTOR (4 downto 0);
          WEN: in  STD_LOGIC;
          CLK, RST: in  STD_LOGIC);
end regbank;

architecture Behavioral of regbank is

    --type rbank is array (0 to 31) of std_logic_vector (15 downto 0);
    signal REG00 : std_logic_vector (15 downto 0);
    signal REG01 : std_logic_vector (15 downto 0);
    signal REG02 : std_logic_vector (15 downto 0);
    signal REG03 : std_logic_vector (15 downto 0);
    signal REG04 : std_logic_vector (15 downto 0);
    signal REG05 : std_logic_vector (15 downto 0);
    signal REG06 : std_logic_vector (15 downto 0);
    signal REG07 : std_logic_vector (15 downto 0);
    signal REG08 : std_logic_vector (15 downto 0);
    signal REG09 : std_logic_vector (15 downto 0);
    signal REG10 : std_logic_vector (15 downto 0);
    signal REG11 : std_logic_vector (15 downto 0);
    signal REG12 : std_logic_vector (15 downto 0);
    signal REG13 : std_logic_vector (15 downto 0);
    signal REG14 : std_logic_vector (15 downto 0);
```

```

signal REG15 : std_logic_vector (15 downto 0);
signal REG16 : std_logic_vector (15 downto 0);
signal REG17 : std_logic_vector (15 downto 0);
signal REG18 : std_logic_vector (15 downto 0);
signal REG19 : std_logic_vector (15 downto 0);
signal REG20 : std_logic_vector (15 downto 0);
signal REG21 : std_logic_vector (15 downto 0);
signal REG22 : std_logic_vector (15 downto 0);
signal REG23 : std_logic_vector (15 downto 0);
signal REG24 : std_logic_vector (15 downto 0);
signal REG25 : std_logic_vector (15 downto 0);
signal REG26 : std_logic_vector (15 downto 0);
signal REG27 : std_logic_vector (15 downto 0);
signal REG28 : std_logic_vector (15 downto 0);
signal REG29 : std_logic_vector (15 downto 0);
signal REG30 : std_logic_vector (15 downto 0);
signal REG31 : std_logic_vector (15 downto 0);

```

```
begin
```

```

    A <=
        REG00 when RSELA = "00000" else
        REG01 when RSELA = "00001" else
        REG02 when RSELA = "00010" else
        REG03 when RSELA = "00011" else
        REG04 when RSELA = "00100" else
        REG05 when RSELA = "00101" else
        REG06 when RSELA = "00110" else
        REG07 when RSELA = "00111" else
        REG08 when RSELA = "01000" else
        REG09 when RSELA = "01001" else
        REG10 when RSELA = "01010" else
        REG11 when RSELA = "01011" else
        REG12 when RSELA = "01100" else
        REG13 when RSELA = "01101" else
        REG14 when RSELA = "01110" else
        REG15 when RSELA = "01111" else
        REG16 when RSELA = "10000" else
        REG17 when RSELA = "10001" else
        REG18 when RSELA = "10010" else
        REG19 when RSELA = "10011" else
        REG20 when RSELA = "10100" else
        REG21 when RSELA = "10101" else
        REG22 when RSELA = "10110" else
        REG23 when RSELA = "10111" else
        REG24 when RSELA = "11000" else
        REG25 when RSELA = "11001" else
        REG26 when RSELA = "11010" else
        REG27 when RSELA = "11011" else
        REG28 when RSELA = "11100" else
        REG29 when RSELA = "11101" else
        REG30 when RSELA = "11110" else
        REG31 when RSELA = "11111" else
        "XXXXXXXXXXXXXXXXXXXX";

```

```

    B <=
        REG00 when RSELB = "00000" else
        REG01 when RSELB = "00001" else
        REG02 when RSELB = "00010" else
        REG03 when RSELB = "00011" else
        REG04 when RSELB = "00100" else
        REG05 when RSELB = "00101" else
        REG06 when RSELB = "00110" else

```

```

REG07 when RSELB = "00111" else
REG08 when RSELB = "01000" else
REG09 when RSELB = "01001" else
REG10 when RSELB = "01010" else
REG11 when RSELB = "01011" else
REG12 when RSELB = "01100" else
REG13 when RSELB = "01101" else
REG14 when RSELB = "01110" else
REG15 when RSELB = "01111" else
REG16 when RSELB = "10000" else
REG17 when RSELB = "10001" else
REG18 when RSELB = "10010" else
REG19 when RSELB = "10011" else
REG20 when RSELB = "10100" else
REG21 when RSELB = "10101" else
REG22 when RSELB = "10110" else
REG23 when RSELB = "10111" else
REG24 when RSELB = "11000" else
REG25 when RSELB = "11001" else
REG26 when RSELB = "11010" else
REG27 when RSELB = "11011" else
REG28 when RSELB = "11100" else
REG29 when RSELB = "11101" else
REG30 when RSELB = "11110" else
REG31 when RSELB = "11111" else
"XXXXXXXXXXXXXXXXXXXX";

```

```

REG00 <= "0000000000000000";

```

```

process (CLK)
begin
  if (CLK'event and CLK = '1') then
    if RST = '1' then
      REG01 <= "0000000000000000";
      REG02 <= "0000000000000000";
      REG03 <= "0000000000000000";
      REG04 <= "0000000000000000";
      REG05 <= "0000000000000000";
      REG06 <= "0000000000000000";
      REG07 <= "0000000000000000";
      REG08 <= "0000000000000000";
      REG09 <= "0000000000000000";
      REG10 <= "0000000000000000";
      REG11 <= "0000000000000000";
      REG12 <= "0000000000000000";
      REG13 <= "0000000000000000";
      REG14 <= "0000000000000000";
      REG15 <= "0000000000000000";
      REG16 <= "0000000000000000";
      REG17 <= "0000000000000000";
      REG18 <= "0000000000000000";
      REG19 <= "0000000000000000";
      REG20 <= "0000000000000000";
      REG21 <= "0000000000000000";
      REG22 <= "0000000000000000";
      REG23 <= "0000000000000000";
      REG24 <= "0000000000000000";
      REG25 <= "0000000000000000";
      REG26 <= "0000000000000000";
      REG27 <= "0000000000000000";
      REG28 <= "0000000000000000";
    end if
  end if
end process

```



```

REG29 <= "0000000000000000";
REG30 <= "0000000000000000";
REG31 <= "0000000000000000";
else
  if (WEN = '1') then
    case WSEL is
--      when "00000" => REG00 <= D;
      when "00001" => REG01 <= D;
      when "00010" => REG02 <= D;
      when "00011" => REG03 <= D;
      when "00100" => REG04 <= D;
      when "00101" => REG05 <= D;
      when "00110" => REG06 <= D;
      when "00111" => REG07 <= D;
      when "01000" => REG08 <= D;
      when "01001" => REG09 <= D;
      when "01010" => REG10 <= D;
      when "01011" => REG11 <= D;
      when "01100" => REG12 <= D;
      when "01101" => REG13 <= D;
      when "01110" => REG14 <= D;
      when "01111" => REG15 <= D;
      when "10000" => REG16 <= D;
      when "10001" => REG17 <= D;
      when "10010" => REG18 <= D;
      when "10011" => REG19 <= D;
      when "10100" => REG20 <= D;
      when "10101" => REG21 <= D;
      when "10110" => REG22 <= D;
      when "10111" => REG23 <= D;
      when "11000" => REG24 <= D;
      when "11001" => REG25 <= D;
      when "11010" => REG26 <= D;
      when "11011" => REG27 <= D;
      when "11100" => REG28 <= D;
      when "11101" => REG29 <= D;
      when "11110" => REG30 <= D;
      when "11111" => REG31 <= D;
      when others => REG31 <= REG31;
    end case;
  end if;
end if;
end process;

end Behavioral;

```

REGISTER.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity register is
    Port ( clk : in  STD_LOGIC;
          data_in : in  STD_LOGIC_VECTOR (3 downto 0);
          data_out : out STD_LOGIC_VECTOR (3 downto 0));
end register;

architecture Behavioral of register is

begin

end Behavioral;
```

ALUPARAM.VHD

```
-----
--
-- Uni      : University of York
-- Course   : Electronic Engineering
-- Module   : Computer Architectures
-- Engineers : Y3839090 & Y3840426
--
-- Create Date : 13:19:20 02/17/2017
-- Design Name : ALU_param - Behavioral
-- Description  : A paramateriable integer ALU.
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.DigEng.ALL;

entity ALU_param is
  Generic (
    N : natural := 8 -- data size in bits
  );
  Port (
    A : in  STD_LOGIC_VECTOR (N-1 downto 0);
    B : in  STD_LOGIC_VECTOR (N-1 downto 0);
    X : in  STD_LOGIC_VECTOR (log2(N)-1 downto 0); -- shift/rotate amount input
    ctrl : in  STD_LOGIC_VECTOR (3 downto 0); -- control signals from opcode
    O : out STD_LOGIC_VECTOR (N-1 downto 0);
    flags : out STD_LOGIC_VECTOR (7 downto 0) -- flags
  );
end ALU_param;

architecture Behavioral of ALU_param is

  -- internal signed signal for A and B inpy=uts
  signal A_itrn : SIGNED (N-1 downto 0);
  signal B_itrn : SIGNED (N-1 downto 0);

  -- internal integer for X
  signal X_itrn : integer;

  -- internal signed signal for output
  signal O_itrn : SIGNED (N-1 downto 0);

  -- max positive and negative N bit signed numbers
  constant max_pos : SIGNED (N-1 downto 0) := to_signed(( 2 ** (N-1) ) - 1, N);
  constant max_neg : SIGNED (N-1 downto 0) := to_signed( -2 ** (N-1) , N);

begin

  A_itrn <= signed(A); -- converts A to signed and maps the result to A_itrn
  B_itrn <= signed(B); -- converts A to signed and maps the result to B_itrn

  -- converts X to integer and maps the result to X_itrn
  X_itrn <= to_integer(unsigned(X));
```

```

-- converts O_itrn to a plain std_logic_vector and maps it to O
O <= std_logic_vector(O_itrn);

-- Main ALU multiplexer for each possible command
O_itrn <=
    A_itrn                when ctrl = "0000" else -- Output A
    A_itrn and B_itrn      when ctrl = "0100" else -- Output A & B
    A_itrn or B_itrn       when ctrl = "0101" else -- Output A || B
    A_itrn xor B_itrn      when ctrl = "0110" else -- Output A xor B
    not A_itrn             when ctrl = "0111" else -- Output not A
    A_itrn + 1             when ctrl = "1000" else -- Output A + 1
    A_itrn - 1             when ctrl = "1001" else -- Output A - 1
    A_itrn + B_itrn        when ctrl = "1010" else -- Output A + B
    A_itrn - B_itrn        when ctrl = "1011" else -- Output A - B
    SHIFT_LEFT (A_itrn , X_itrn) when ctrl = "1100" else -- Output A sla X
    SHIFT_RIGHT (A_itrn , X_itrn) when ctrl = "1101" else -- Output A sra X
    ROTATE_LEFT (A_itrn , X_itrn) when ctrl = "1110" else -- Output A rotl X
    ROTATE_RIGHT (A_itrn , X_itrn) when ctrl = "1111" else -- Output A rotr X
    (others => 'U');

-- Overflow flag
flags(7) <=
    -- Will overflow if you add one to the max positive value
    '1' when ctrl = "1000" and A_itrn = max_pos else

    -- Will overflow if you minus one to the max negative value
    '1' when ctrl = "1001" and A_itrn = max_neg else

    -- Will overflow if two neg values added give a pos result
    '1' when ctrl = "1010" and A_itrn(N-1) = '1' and B_itrn(N-1) = '1' and
O_itrn(N-1) = '0' else
    -- Will overflow if two pos values added give a neg result
    '1' when ctrl = "1010" and A_itrn(N-1) = '0' and B_itrn(N-1) = '0' and
O_itrn(N-1) = '1' else

    -- Will overflow if a pos value is subtracted from a neg value gives a pos
result
    '1' when ctrl = "1011" and A_itrn(N-1) = '1' and B_itrn(N-1) = '0' and
O_itrn(N-1) = '0' else
    -- Will overflow if a neg value is subtracted from a pos value gives a neg
result
    '1' when ctrl = "1011" and A_itrn(N-1) = '0' and B_itrn(N-1) = '1' and
O_itrn(N-1) = '1'

    -- If none of the above are true then the result hasn't overflown
    else '0';

-- Other flags
flags(6) <= '1' when O_itrn >= 0 else '0'; -- grater than or equal to zero
flags(5) <= '1' when O_itrn <= 0 else '0'; -- less than or equal to zero
flags(4) <= '1' when O_itrn > 0 else '0'; -- grater than zero
flags(3) <= '1' when O_itrn < 0 else '0'; -- less than zero
flags(2) <= '1' when O_itrn = 1 else '0'; -- one flag
flags(1) <= '1' when O_itrn /= 0 else '0'; -- not zero flag
flags(0) <= '1' when O_itrn = 0 else '0'; -- zero flag

end Behavioral;

```

DIGENG.VHD

```
-----
-- PACKAGE FOR DIGITAL ENGINEERING LABS
--
-- To use:
--
-- - Download file
-- - Use "Add copy" to add to Xilinx project
-- - Add "use work.DigEng.all" on top of entity
--
-----

package DigEng is

function log2 (x : natural ) return natural;
function size (x : natural ) return natural;

end DigEng;

package body DigEng is

-----
-- LOG BASE 2 FUNCTION
-- returns the ceiling of log base 2 of a (non-zero) integer
-- (1->0; 2->1; 3->2; 4->2; 5->3 ...)
--
-- This function is NOT SYNTHESIZABLE
-- should be used for indices, not circuit description
--
-- Examples:
-- - signal A : STD_LOGIC_VECTOR(log2(data_size)-1 downto 0);
--
-----

function log2 ( x : natural ) return natural is
    variable temp : natural := x ;
    variable n : natural := 0 ;
begin
    while temp > 1 loop
        temp := temp / 2 ;
        n := n + 1 ;
    end loop ;
    if (x > 2**n) then
        n := n + 1;
    end if;
    return n ;
end function log2;

-----
-- SIZE FUNCTION
-- returns the size of a vector that can encode a (non-zero) integer
-- (1->1; 2->2; 3->2; 4->3; 5->3 ...)
--
-- This function is NOT SYNTHESIZABLE
-- should be used for indices, not circuit description
--
-- Examples:
-- - signal A : STD_LOGIC_VECTOR(size(n)-1 downto 0);
--
-----
```

```
-----  
function size ( x : natural ) return natural is  
  variable temp : natural := x ;  
  variable n : natural := 0 ;  
begin  
  while temp >= 1 loop  
    temp := temp / 2 ;  
    n := n + 1 ;  
  end loop ;  
  return n ;  
end function size;  
  
end DigEng;
```

EASYPRINT.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
USE ieee.numeric_std.ALL;

package easyprint is

function s_tostr(val : std_logic_vector) return string;
function u_tostr(val : std_logic_vector) return string;

function to_bstring(sl : std_logic) return string;
function to_bstring(slv : std_logic_vector) return string;

end easyprint;

package body easyprint is

-- =====
-- From http://stackoverflow.com/a/24336034 By Morten Zilmer
-- Allows printing a std_logic_vector as a string that represents it's binary form.
-- =====
function to_bstring(sl : std_logic) return string is
    variable sl_str_v : string(1 to 3); -- std_logic image with quotes around
begin
    sl_str_v := std_logic'image(sl);
    return "\"" & sl_str_v(2); -- "\"" & character to get string
end function;

function to_bstring(slv : std_logic_vector) return string is
    alias slv_norm : std_logic_vector(1 to slv'length) is slv;
    variable sl_str_v : string(1 to 1); -- String of std_logic
    variable res_v : string(1 to slv'length);
begin
    for idx in slv_norm'range loop
        sl_str_v := to_bstring(slv_norm(idx));
        res_v(idx) := sl_str_v(1);
    end loop;
    return res_v;
end function;

-- =====

-- converts an std_logic_vector to a string that represents it's signed value
function s_tostr(val : std_logic_vector) return string is
begin
    return integer'image( to_integer(signed(val)) );
end function;

-- converts an std logic vector to a string that represents it's unsigned value
function u_tostr(val : std_logic_vector) return string is
begin
    return integer'image( to_integer(unsigned(val)) );
end function;
```

```
end easyprint;
```

PROCESSORTB.VHD

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.easyprint.ALL;

ENTITY ProcessorTB IS
END ProcessorTB;

ARCHITECTURE behavior OF ProcessorTB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Processor
    PORT (
        clk : IN std_logic;
        en : IN std_logic;
        rst : IN std_logic;
        start : IN std_logic;
        data_out : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal clk : std_logic := '0';
    signal en : std_logic := '0';
    signal rst : std_logic := '0';
    signal start : std_logic := '0';

    --Outputs
    signal data_out : std_logic_vector(15 downto 0);

    -- Clock period definitions
    constant clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Processor PORT MAP (
        clk => clk,
        en => en,
        rst => rst,
        start => start,
        data_out => data_out
    );

    -- Clock process definitions
    clk_process :process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;
```



```
-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    -- do an initial reset
    rst <= '1';

    wait until rising_edge(clk);

    rst <= '0';

    en <= '1';

    -- wait a while whilst the cpu is in a loop before
    -- taking start high
    wait for 50*clk_period;

    start <= '1';

    wait until rising_edge(clk);
    wait for 15*clk_period;
    start <= '0';

    wait;
end process;

END;
```

OUTPUTREGTB.VHD

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.easyprint.ALL;

ENTITY OutputRegTB IS
END OutputRegTB;

ARCHITECTURE behavior OF OutputRegTB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT OutputReg
    PORT (
        clk : IN  std_logic;
        data_in : IN  std_logic_vector(15 downto 0);
        WE : IN  std_logic;
        data_out : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal clk : std_logic := '0';
    signal data_in : std_logic_vector(15 downto 0) := (others => '0');
    signal WE : std_logic := '0';
    signal data_out : std_logic_vector(15 downto 0) := (others => '0');

    -- Clock period definitions
    constant clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: OutputReg PORT MAP (
        clk => clk,
        data_in => data_in,
        WE => WE,
        data_out => data_out
    );

    -- Clock process definitions
    clk_process :process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;
```

```

wait for clk_period*10;

-- insert stimulus here
WE <= '1';
data_in <= "1100110011001100";
wait for clk_period;

assert std_match(data_out, "1100110011001100")
report lf &
"DATA IN/DATA OUT BROKED"
severity error;

WE <= '0';
data_in <= "0011100000111111";
wait for clk_period;

assert std_match(data_out, "1100110011001100")
report lf &
"WE BROKED"
severity error;

wait;
end process;

END;

```

DUALPORTMEMORYTB.VHD

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.easyprint.ALL;

ENTITY DualPortMemoryTB IS
END DualPortMemoryTB;

ARCHITECTURE behavior OF DualPortMemoryTB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT DualPortMemory
    PORT (
        clk : IN  std_logic;
        I_addr : IN  std_logic_vector(6 downto 0);
        D_addr : IN  std_logic_vector(6 downto 0);
        D_in : IN  std_logic_vector(31 downto 0);
        WE : IN  std_logic;
        D_out : OUT std_logic_vector(31 downto 0);
        I_out : OUT std_logic_vector(31 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal clk : std_logic := '0';
    signal I_addr : std_logic_vector(6 downto 0) := (others => '0');
    signal D_addr : std_logic_vector(6 downto 0) := (others => '0');
    signal D_in : std_logic_vector(31 downto 0) := (others => '0');
    signal WE : std_logic := '0';

    --Outputs
    signal D_out : std_logic_vector(31 downto 0);
    signal I_out : std_logic_vector(31 downto 0);

    -- Clock period definitions
    constant clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: DualPortMemory PORT MAP (
        clk => clk,
        I_addr => I_addr,
        D_addr => D_addr,
        D_in => D_in,
        WE => WE,
        D_out => D_out,
        I_out => I_out
    );

    -- Clock process definitions
    clk_process :process
    begin
        clk <= '0';
```

```

        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    wait for clk_period*10;

    -- insert stimulus here

    I_addr <= "0000100";

    wait for clk_period;

    assert std_match(I_out, X"00000100")
    report lf &"BROKED"
    severity error;

    wait for clk_period;

    D_addr <= "0000010";
    WE <= '1';
    D_in <= "00011000110011001100110101011110";

    wait for clk_period;

    assert std_match(D_out, "00011000110011001100110101011110")
    report lf &"BROKED"
    severity error;

    wait;
end process;

END;
```

MMUTB.VHD

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.easyprint.ALL;

ENTITY MMU_TB IS
END MMU_TB;

ARCHITECTURE behavior OF MMU_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT MMU
    PORT (
        clk : IN  std_logic;
        I_addr : IN  std_logic_vector(7 downto 0);
        OEn : IN  std_logic;
        D_in : IN  std_logic_vector(15 downto 0);
        D_out : OUT std_logic_vector(15 downto 0);
        D_addr : IN  std_logic_vector(15 downto 0);
        start : IN  std_logic;
        oWE : OUT std_logic;
        oD_out : OUT std_logic_vector(15 downto 0);
        mWE : OUT std_logic;
        mD_addr : OUT std_logic_vector(6 downto 0);
        mD_in : IN  std_logic_vector(31 downto 0);
        mD_out : OUT std_logic_vector(31 downto 0);
        mI_addr : OUT std_logic_vector(6 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal clk : std_logic := '0';
    signal I_addr : std_logic_vector(7 downto 0) := (others => '0');
    signal OEn : std_logic := '0';
    signal D_in : std_logic_vector(15 downto 0) := (others => '0');
    signal D_addr : std_logic_vector(15 downto 0) := (others => '0');
    signal start : std_logic := '0';
    signal mD_in : std_logic_vector(31 downto 0) := (others => '0');

    --Outputs
    signal D_out : std_logic_vector(15 downto 0);
    signal oWE : std_logic;
    signal oD_out : std_logic_vector(15 downto 0);
    signal mWE : std_logic;
    signal mD_addr : std_logic_vector(6 downto 0);
    signal mD_out : std_logic_vector(31 downto 0);
    signal mI_addr : std_logic_vector(6 downto 0);

    -- Clock period definitions
    constant clk_period : time := 10 ns;

    -- Test Data
    type TEST_RECORD is record

        --Inputs
```

```

I_addr : std_logic_vector(7 downto 0);
OEn : std_logic;
D_in : std_logic_vector(15 downto 0);
D_addr : std_logic_vector(15 downto 0);
start : std_logic;
mD_in : std_logic_vector(31 downto 0);

--Outputs
D_out : std_logic_vector(15 downto 0);
oWE : std_logic;
oD_out : std_logic_vector(15 downto 0);
mWE : std_logic;
mD_addr : std_logic_vector(6 downto 0);
mD_out : std_logic_vector(31 downto 0);
mI_addr : std_logic_vector(6 downto 0);

end record TEST_RECORD;

type TEST_RECORD_ARRAY is array (NATURAL range <>) of TEST_RECORD;

constant test_data : TEST_RECORD_ARRAY := (
  -- I_addr, Oen, D_in, D_addr, Start, mD_in, D_out,
  oWE, oD_out, mWE, mD_addr, mD_out, mI_addr
  ("01010101", '0', "-----", X"007e", '0', X"00FF00FF", X"00FF",
  '0', "-----", '0', "1111111", "-----",
  "1010101"),
  ("11010101", '1', "-----", X"007e", '0', X"00FF00FF", "-----",
  "-----", '0', "-----", '1', "1111111", X"00FF00EE",
  "1010101"),

  -- I_addr, Oen, D_in, D_addr, Start, mD_in,
  D_out, oWE, oD_out, mWE, mD_addr, mD_out,
  mI_addr
  ("11011111", '1', X"00CC", X"01F8", '0', "-----",
  "-----", "-----", '1', X"00CC", '0', "-----", "-----",
  "-----", "1011111"),
  -- I_addr, Oen, D_in, D_addr, Start, mD_in,
  D_out, oWE, oD_out, mWE, mD_addr, mD_out,
  mI_addr
  ("01110111", '0', "-----", X"01F0", '1', "-----",
  "-----", X"FFFF", '0', "-----", '0', "-----", "-----",
  "-----", "1110111"),
  ("01110111", '0', "-----", X"01F0", '0', "-----",
  "-----", X"0000", '0', "-----", '0', "-----", "-----",
  "-----", "1110111")
);

BEGIN

  -- Instantiate the Unit Under Test (UUT)
  uut: MMU PORT MAP (
    clk => clk,
    I_addr => I_addr,
    OEn => OEn,
    D_in => D_in,
    D_out => D_out,
    D_addr => D_addr,
    start => start,
    oWE => oWE,
    oD_out => oD_out,

```

```

        mWE => mWE,
        mD_addr => mD_addr,
        mD_in => mD_in,
        mD_out => mD_out,
        mI_addr => mI_addr
    );

-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    wait until rising_edge(clk);

    for i in test_data'range loop

        -- assign test inputs
        I_addr <= test_data(i).I_addr;
        OEn <= test_data(i).OEn;
        D_in <= test_data(i).D_in;
        D_addr <= test_data(i).D_addr;
        start <= test_data(i).start;
        mD_in <= test_data(i).mD_in;

        wait until falling_edge(clk);

        -- Check to see if the out put was what we were expecting

        assert std_match(D_out, test_data(i).D_out)
        report lf & " [ERR!] Test " & integer'image(i) &
        " Actual D_out did not equal expected D_out."&
        " Actual [ " & to_bstring(D_out) & " ]" &
        " Expected [ " & to_bstring(test_data(i).D_out) & " ]" & lf
        severity error;

        assert std_match(oWE, test_data(i).oWE)
        report lf & " [ERR!] Test " & integer'image(i) &
        " Actual oWE did not equal expected oWE."&
        " Actual [ " & to_bstring(oWE) & " ]" &
        " Expected [ " & to_bstring(test_data(i).oWE) & " ]" & lf
        severity error;

        assert std_match(mWE, test_data(i).mWE)
        report lf & " [ERR!] Test " & integer'image(i) &
        " Actual mWE did not equal expected mWE."&
        " Actual [ " & to_bstring(mWE) & " ]" &
        " Expected [ " & to_bstring(test_data(i).mWE) & " ]" & lf
        severity error;

        assert std_match(mD_addr, test_data(i).mD_addr)

```



```

report lf & " [ERR!] Test " & integer'image(i) &
" Actual mD_addr did not equal expected mD_addr."&
" Actual [ " & to_bstring(mD_addr) & " ]" &
" Expected [ " & to_bstring(test_data(i).mD_addr) & " ]" & lf
severity error;

assert std_match(mD_out, test_data(i).mD_out)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual mD_out did not equal expected mD_out."&
" Actual [ " & to_bstring(mD_out) & " ]" &
" Expected [ " & to_bstring(test_data(i).mD_out) & " ]" & lf
severity error;

assert std_match(mI_addr, test_data(i).mI_addr)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual mI_addr did not equal expected mI_addr."&
" Actual [ " & to_bstring(mI_addr) & " ]" &
" Expected [ " & to_bstring(test_data(i).mI_addr) & " ]" & lf
severity error;

-- if there were no isses report that the test was successful
assert not (
    std_match(D_out, test_data(i).D_out) and
    std_match(oWE, test_data(i).oWE) and
    std_match(oD_out, test_data(i).oD_out) and
    std_match(mWE, test_data(i).mWE) and
    std_match(mD_addr, test_data(i).mD_addr) and
    std_match(mD_out, test_data(i).mD_out) and
    std_match(mI_addr, test_data(i).mI_addr)
)
report lf & " [ OK ] Test " & integer'image(i) & " was successful!" & lf
severity note;
wait until rising_edge(clk);

end loop;
wait;
end process;

END;

```

CONTROL_FSM_TB.VHD

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE work.DigEng.ALL;
USE work.easyprint.ALL;
USE ieee.numeric_std.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY ControlFSM_TB IS
END ControlFSM_TB;

ARCHITECTURE behavior OF ControlFSM_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT ControlFSM
    PORT (
        clk : IN  std_logic; -- clk
        rst : IN  std_logic; -- sync active high reset
        opcode : IN  std_logic_vector(5 downto 0); -- opcode from instruction
        S : OUT  std_logic_vector(3 downto 0) -- Selectors for muxes
    );
    END COMPONENT;

    --Inputs
    signal clk : std_logic := '0';
    signal rst : std_logic := '0';
    signal opcode : std_logic_vector(5 downto 0) := (others => '0');

    --Outputs
    signal S : std_logic_vector(3 downto 0);

    -- Clock period definitions
    constant clk_period : time := 10 ns;

    -- Test Data
    type TEST_RECORD is record
        opcode : std_logic_vector(5 downto 0);
        S : std_logic_vector(4 downto 1);
    end record TEST_RECORD;

    type TEST_RECORD_ARRAY is array (NATURAL range <>) of TEST_RECORD;

    constant test_data : TEST_RECORD_ARRAY := (
        -- Register
        ("000100", "--1-"), --add rt, ra, rb
        ("000100", "----"),
        ("000100", "--00"),
        ("000100", "0---"),

        ("010000", "--1-"), -- and rt, ra, rb
        ("010000", "----"),
        ("010000", "--00"),
```

```

    ("010000", "0---"),
    -- Memory
    ("100111", "--1-"), -- stor
    ("100111", "----"),
    ("100111", "--01"),
    ("100111", "-0--"),

    ("100101", "--1-"), -- load
    ("100101", "----"),
    ("100101", "--01"),
    ("100101", "-0--"),
    ("100101", "1---")
    -- Branch
);

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: ControlFSM PORT MAP (
    clk => clk,
    rst => rst,
    opcode => opcode,
    S => S
);

-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    rst <= '1';
    wait for 2*clk_period;
    rst <= '0';

    for i in test_data'range loop

        -- assign test inputs
        opcode <= test_data(i).opcode;

        wait until falling_edge(clk);

        -- Check to see if the out put was what we were expecting
        assert std_match(S, test_data(i).S)
        report 1f & " [ERR!] Test " & integer'image(i) &
        " Actual STATE did not equal expected STATE."&
        " Actual [ " & to_bstring(S) & " ]" &
        " Expected [ " & to_bstring(test_data(i).S) & " ]" & 1f
        severity error;
    end loop;
end process;

```

```
-- if there were no issues report that the test was successful
assert not (std_match(S, test_data(i).S))
report lf & " [ OK ] Test " & integer'image(i) & " was successful!" & lf
severity note;
wait until rising_edge(clk);

end loop;

-- End of test
wait;
end process;

END;
```

SEQUENCERTB.VHD

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.easyprint.ALL;

ENTITY SequencerTB IS
END SequencerTB;

ARCHITECTURE behavior OF SequencerTB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Sequencer
    PORT (
        clk : IN std_logic;
        rst : IN std_logic;
        en : IN std_logic;
        FETCH : in STD_LOGIC;
        PC_plus : IN std_logic_vector(7 downto 0);
        instr : IN std_logic_vector(31 downto 0);
        flags : IN std_logic_vector(7 downto 0);
        PC : OUT std_logic_vector(7 downto 0);
        MIA : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal clk : std_logic := '0';
    signal rst : std_logic := '1';
    signal en : std_logic := '0';
    signal FETCH : std_logic := '0';
    signal PC_plus : std_logic_vector(7 downto 0) := (others => '0');
    signal instr : std_logic_vector(31 downto 0) := (others => '0');
    signal flags : std_logic_vector(7 downto 0) := (others => '0');

    --Outputs
    signal PC : std_logic_vector(7 downto 0);
    signal MIA : std_logic_vector(7 downto 0);

    -- Clock period definitions
    constant clk_period : time := 10 ns;

    -- Test Data
    type TEST_RECORD is record

        instr : std_logic_vector(31 downto 0);
        PC_plus : std_logic_vector(7 downto 0);
        flags : std_logic_vector(7 downto 0);

        PC : std_logic_vector(7 downto 0);
        MIA : std_logic_vector(7 downto 0);

    end record;

    type TEST_RECORD_ARRAY is array (NATURAL range <>) of TEST_RECORD;
```

```

constant test_data : TEST_RECORD_ARRAY := (
-- Instruction , PCplus , Flags , PC , MIA
(X"01010101", "-----", "-----", X"00", X"00"),
(X"200000A5", "-----", "-----", X"01", X"01"),
(X"100C00A8", "-----", "-----", X"02", X"02"),
(X"C40A00C0", X"0C" , "-----1-", X"03", X"03"),
(X"00000000", "-----", "-----", X"0C", X"0C")
);

```

BEGIN

```

-- Instantiate the Unit Under Test (UUT)

```

```

uut: Sequencer PORT MAP (
    clk => clk,
    rst => rst,
    en => en,
    FETCH => FETCH,
    PC_plus => PC_plus,
    instr => instr,
    flags => flags,
    PC => PC,
    MIA => MIA
);

```

```

-- Clock process definitions

```

```

clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

```

```

-- Stimulus process

```

```

stim_proc: process
begin
    wait for 100 ns;
    rst <= '1';
    en <= '1';
    wait until rising_edge(clk);

    for i in test_data'range loop

        rst <= '0';

        -- assign test inputs
        instr <= test_data(i).instr;
        PC_plus <= test_data(i).PC_plus;
        flags <= test_data(i).flags;
        FETCH <= '1';

        wait for clk_period;
        FETCH <= '0';
        wait for 5*clk_period;

        -- Check to see if the out put was what we were expecting
        assert std_match(PC, test_data(i).PC)
        report 1f & " [ERR!] Test " & integer'image(i) &
        " Actual PC did not equal expected PC."&
        " Actual [ " & to_bstring(PC) & " ]" &

```

```

    " Expected [ " & to_bstring(test_data(i).PC) & " ]" & lf
    severity error;

    assert std_match(MIA, test_data(i).MIA)
    report lf & " [ERR!] Test " & integer'image(i) &
    " Actual MIA did not equal expected MIA."&
    " Actual [ " & to_bstring(MIA) & " ]" &
    " Expected [ " & to_bstring(test_data(i).MIA) & " ]" & lf
    severity error;

    -- if there were no issues report that the test was successful
    assert not (std_match(PC, test_data(i).PC) and std_match(MIA,
test_data(i).MIA))
    report lf & " [ OK ] Test " & integer'image(i) & " was successful!" & lf
    severity note;

    end loop;

    -- End of test
    wait;
    end process;

END;

```

DECODERTB.VHD

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.easyprint.ALL;

ENTITY Decoder_TB IS
END Decoder_TB;

ARCHITECTURE behavior OF Decoder_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Decoder_Block
    PORT (
        instr : IN  std_logic_vector(31 downto 0);
        OPCODE : OUT std_logic_vector(5 downto 0);
        RA : OUT  std_logic_vector(4 downto 0);
        RB : OUT  std_logic_vector(4 downto 0);
        WA : OUT  std_logic_vector(4 downto 0);
        MA : OUT  std_logic_vector(15 downto 0);
        IMM : OUT  std_logic_vector(15 downto 0);
        AL : OUT  std_logic_vector(3 downto 0);
        SH : OUT  std_logic_vector(3 downto 0);
        WEN : OUT  std_logic;
        OEN : OUT  std_logic
    );
    END COMPONENT;

    --Inputs
    signal instr : std_logic_vector(31 downto 0) := (others => '0');

    --Outputs
    signal OPCODE : std_logic_vector(5 downto 0);
    signal RA : std_logic_vector(4 downto 0);
    signal RB : std_logic_vector(4 downto 0);
    signal WA : std_logic_vector(4 downto 0);
    signal MA : std_logic_vector(15 downto 0);
    signal IMM : std_logic_vector(15 downto 0);
    signal AL : std_logic_vector(3 downto 0);
    signal SH : std_logic_vector(3 downto 0);
    signal WEN : std_logic;
    signal OEN : std_logic;

    -- Test Data
    type TEST_RECORD is record
        --Inputs
        instr : std_logic_vector(31 downto 0);

        --Outputs
        OPCODE : std_logic_vector(5 downto 0);
        RA : std_logic_vector(4 downto 0);
        RB : std_logic_vector(4 downto 0);
        WA : std_logic_vector(4 downto 0);
        MA : std_logic_vector(15 downto 0);
        IMM : std_logic_vector(15 downto 0);
        AL : std_logic_vector(3 downto 0);
```



```

        SH : std_logic_vector(3 downto 0);
        WEN : std_logic;
        OEN : std_logic;

end record;

type TEST_RECORD_ARRAY is array (NATURAL range <>) of TEST_RECORD;

constant test_data : TEST_RECORD_ARRAY := (
-- INSTRUCTION,          IMM,          ALU,          SH,          RA,          RB,          WA,
MA,
("011000-----0010-----1001110011", "011000", "10011", "-----",
"10011", "-----", "-----", "1100", "0010", '1', '0'),
("0001100011001100110101011110", "000110", "01010", "-----",
"11110", "-----", "0011001100110011", "1010", "-----", '1', '0'),
("000100-----00011-----0001000010", "000100", "00010", "00011",
"00010", "-----", "-----", "1010", "-----", '1', '0'),
("1000010000000111110000000001111", "100001", "-----", "-----",
"01111", "X"01F0", "-----", "-----", "-----", '1', '0')
);

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: Decoder_Block PORT MAP (
    instr => instr,
    OPCODE => OPCODE,
    RA => RA,
    RB => RB,
    WA => WA,
    MA => MA,
    IMM => IMM,
    AL => AL,
    SH => SH,
    WEN => WEN,
    OEN => OEN
  );

-- Stimulus process
stim_proc: process
begin
  -- hold reset state for 100 ns.
  wait for 100 ns;

  for i in test_data'range loop

    -- assign test inputs
    instr <= test_data(i).instr;

    wait for 100 ns;

    -- Check to see if the out put was what we were expecting
    assert std_match(OPCODE, test_data(i).OPCODE)
    report 1f & " [ERR!] Test " & integer'image(i) &
    " Actual OPCODE did not equal expected OPCODE."&
    " Actual [ " & to_bstring(OPCODE) & " ]" &
    " Expected [ " & to_bstring(test_data(i).OPCODE) & " ]" & 1f
    severity error;

    assert std_match(RA, test_data(i).RA)

```

```

report lf & " [ERR!] Test " & integer'image(i) &
" Actual RA did not equal expected RA."&
" Actual [ " & to_bstring(RA) & " ]" &
" Expected [ " & to_bstring(test_data(i).RA) & " ]" & lf
severity error;

assert std_match(RB, test_data(i).RB)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual RB did not equal expected RB."&
" Actual [ " & to_bstring(RB) & " ]" &
" Expected [ " & to_bstring(test_data(i).RB) & " ]" & lf
severity error;

assert std_match(WA, test_data(i).WA)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual PC did not equal expected RB."&
" Actual [ " & to_bstring(WA) & " ]" &
" Expected [ " & to_bstring(test_data(i).WA) & " ]" & lf
severity error;

assert std_match(MA, test_data(i).MA)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual MA did not equal expected MA."&
" Actual [ " & to_bstring(MA) & " ]" &
" Expected [ " & to_bstring(test_data(i).MA) & " ]" & lf
severity error;

assert std_match(IMM, test_data(i).IMM)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual IMM did not equal expected IMM."&
" Actual [ " & to_bstring(IMM) & " ]" &
" Expected [ " & to_bstring(test_data(i).IMM) & " ]" & lf
severity error;

assert std_match(AL, test_data(i).AL)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual AL did not equal expected AL."&
" Actual [ " & to_bstring(AL) & " ]" &
" Expected [ " & to_bstring(test_data(i).AL) & " ]" & lf
severity error;

assert std_match(SH, test_data(i).SH)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual SH did not equal expected SH."&
" Actual [ " & to_bstring(SH) & " ]" &
" Expected [ " & to_bstring(test_data(i).SH) & " ]" & lf
severity error;

assert std_match(WEN, test_data(i).WEN)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual WEN did not equal expected WEN."&
" Actual [ " & to_bstring(WEN) & " ]" &
" Expected [ " & to_bstring(test_data(i).WEN) & " ]" & lf
severity error;

assert std_match(OEN, test_data(i).OEN)
report lf & " [ERR!] Test " & integer'image(i) &
" Actual OEN did not equal expected OEN."&
" Actual [ " & to_bstring(WEN) & " ]" &
" Expected [ " & to_bstring(test_data(i).OEN) & " ]" & lf
severity error;

```

```

-- if there were no issues report that the test was successful
assert not (
    std_match(OPCODE, test_data(i).OPCODE) and
    std_match(RA, test_data(i).RA) and
    std_match(RB, test_data(i).RB) and
    std_match(WA, test_data(i).WA) and
    std_match(MA, test_data(i).MA) and
    std_match(IMM, test_data(i).IMM) and
    std_match(AL, test_data(i).AL) and
    std_match(SH, test_data(i).SH) and
    std_match(OEN, test_data(i).OEN) and
    std_match(WEN, test_data(i).WEN)
)
report lf & " [ OK ] Test " & integer'image(i) & " was successful!" & lf
severity note;

end loop;

-- End of test

-- insert stimulus here

wait;
end process;

END;

```

DATAPATHCTB.VHD

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE work.DigEng.ALL;
USE work.easyprint.ALL;
USE ieee.numeric_std.ALL;

ENTITY DataPath_C_TB IS
END DataPath_C_TB;

ARCHITECTURE behavior OF DataPath_C_TB IS

    -- Constants
    constant data_size : NATURAL := 16;
    constant num_registers : NATURAL := 32;

    -- Clock period definitions
    constant clk_period : time := 10 ns;

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT DataPath_C
        GENERIC (
            data_size : natural;
            num_registers : natural
        );
        PORT (
            clk      : IN      std_logic;
            rst      : IN      std_logic;
            en       : IN      std_logic;

            R_A      : IN      std_logic_vector (log2(num_registers)-1 downto 0);
            R_B      : IN      std_logic_vector (log2(num_registers)-1 downto 0);
            W_EN     : IN      std_logic;
            W_A      : IN      std_logic_vector (log2(num_registers)-1 downto 0);
            IMM      : IN      std_logic_vector (data_size-1 downto 0);
            M_A      : IN      std_logic_vector (data_size-1 downto 0);
            M_in     : IN      std_logic_vector (data_size-1 downto 0);
            PC       : IN      std_logic_vector (15 downto 0);
            S        : IN      std_logic_vector (4 downto 1);
            AL       : IN      std_logic_vector (3 downto 0);
            SH       : IN      std_logic_vector (log2(data_size)-1 downto 0);

            PC_plus  : OUT     std_logic_vector (15 downto 0);
            Flags    : OUT     std_logic_vector (7 downto 0);
            M_DA     : OUT     std_logic_vector (data_size-1 downto 0);
            M_out    : OUT     std_logic_vector (data_size-1 downto 0)
        );
    END COMPONENT;

    --Inputs
    signal clk      : std_logic := '0';
    signal rst      : std_logic := '1';
    signal en       : std_logic := '0';

    signal R_A      : std_logic_vector (log2(num_registers)-1 downto 0) := (others =>
'0');

```

```

    signal R_B : std_logic_vector (log2(num_registers)-1 downto 0) := (others =>
'0');
    signal W_EN : std_logic := '0';
    signal W_A : std_logic_vector (log2(num_registers)-1 downto 0) := (others =>
'0');
    signal IMM : std_logic_vector (data_size-1 downto 0) := (others =>
'0');
    signal M_A : std_logic_vector (data_size-1 downto 0) := (others =>
'0');
    signal M_in : std_logic_vector (data_size-1 downto 0) := (others =>
'0');
    signal PC : std_logic_vector (15 downto 0) := (others =>
'0');
    signal S : std_logic_vector (4 downto 1) := (others =>
'0');
    signal AL : std_logic_vector (3 downto 0) := (others =>
'0');
    signal SH : std_logic_vector (log2(data_size)-1 downto 0) := (others =>
'0');

--Outputs
signal PC_plus : std_logic_vector (15 downto 0);
signal Flags : std_logic_vector (7 downto 0);
signal M_DA : std_logic_vector (data_size-1 downto 0);
signal M_out : std_logic_vector (data_size-1 downto 0);
signal OEN : std_logic := '0';

-- Test data definitions
type TEST_VECTOR is RECORD
    R_A : STD_LOGIC_VECTOR(log2(num_registers)-1 downto 0);
    R_B : std_logic_vector(log2(num_registers)-1 downto 0);

    W_EN : std_logic;
    W_A : std_logic_vector(log2(num_registers)-1 downto 0);

    IMM : std_logic_vector(data_size-1 downto 0);
    M_A : std_logic_vector(data_size-1 downto 0);
    M_in : std_logic_vector(data_size-1 downto 0);
    PC : std_logic_vector(15 downto 0);
    S : std_logic_vector(4 downto 1);
    AL : std_logic_vector(3 downto 0);
    SH : std_logic_vector(log2(data_size)-1 downto 0) ;

    PC_plus: std_logic_vector(15 downto 0);
    flags : std_logic_vector(7 downto 0);
    M_DA : std_logic_vector(data_size-1 downto 0);
    M_out : std_logic_vector(data_size-1 downto 0);

    OEN : std_logic;
end RECORD;
type TEST_VECTOR_ARRAY is ARRAY(NATURAL RANGE <>) of TEST_VECTOR;

-- Test Data
constant test_vectors : TEST_VECTOR_ARRAY := (
    --R_A,      R_B,      W_EN,      W_A,      IMM,      M_A,
M_in,      PC,      S,      AL,      SH,      PC_plus,      flags,
M_DA,      M_out

    -- inc R1, R0

```

```

( "-----", "-----", '0', "-----", "-----",
--", "-----", "-----", X"00FF", "--1-", "1000", "-----", "-----",
"01010010", "-----", "-----", '0' ),
( "00000", "-----", '0', "-----", "-----",
--", "-----", "-----", X"00FF", "-----", "-----", "-----", X"0100",
--", "-----", "-----", "-----", '0' ),
( "-----", "-----", '0', "-----", "-----",
--", "-----", "-----", X"00FF", "--0-", "1000", "-----", "-----",
"01010110", "-----", "-----", "-----", '0' ),
( "-----", "-----", '1', "00001", "-----",
--", "-----", "-----", X"00FF", "0-----", "-----", "-----",
--", "-----", "-----", "-----", '0' ),

-- addi R2, R0, 0x0005
( "-----", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0100", "--1-", "1000", "-----", "-----",
"01010010", "-----", "-----", "-----", '0' ),
( "00000", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0100", "-----", "-----", "-----", X"0101",
--", "-----", "-----", "-----", '0' ),
( "-----", "-----", '0', "-----", "-----", X"0005",
--", "-----", "-----", X"0100", "--01", "1010", "-----", "-----",
"01010010", "-----", "-----", "-----", '0' ),
( "-----", "-----", '1', "00010", "-----",
--", "-----", "-----", X"0100", "0-----", "-----", "-----",
--", "-----", "-----", "-----", '0' ),

-- shl R3, R1, 3
( "-----", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0101", "--1-", "1000", "-----", "-----",
"01010010", "-----", "-----", "-----", '0' ),
( "00001", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0101", "-----", "-----", "-----", X"0102",
--", "-----", "-----", "-----", '0' ),
( "-----", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0101", "--0-", "1100", "0011", "-----",
"01010010", "-----", "-----", "-----", '0' ),
( "-----", "-----", '1', "00011", "-----",
--", "-----", "-----", X"0101", "0-----", "-----", "-----",
--", "-----", "-----", "-----", '0' ),

-- storr R2, R3
( "-----", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0102", "--1-", "1000", "-----", "-----",
"01010010", "-----", "-----", "-----", '0' ),
( "00011", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0102", "-----", "-----", "-----", X"0103",
--", "-----", "-----", "-----", '0' ),
( "-----", "00010", '0', "-----", "-----",
--", "-----", "-----", X"0102", "--00", "0000", "-----", "-----",
"01010010", "-----", "-----", "-----", '0' ),
( "-----", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0102", "0-----", "-----", "-----",
--", X"0008", X"0005", '1' ),

-- loadi R5, 1f1f
( "-----", "-----", '0', "-----", "-----",
--", "-----", "-----", X"0103", "--1-", "1000", "-----", "-----",
"01010010", "-----", "-----", "-----", '0' ),

```

```

( "-----", "-----", '0', "-----", "-----", X"1F1F",
X"CCCC", X"0103", "-1-", "-----", "-----", X"0104", "-----",
X"1f1f", "-----", '0' ),
( "-----", "-----", '1', "00101", "-----", "-----",
--, "-----", X"0103", "1-", "-----", "-----", "-----",
--, "-----", "-----", '0' ),

-- brneq R2, 010F
( "-----", "-----", '0', "-----", "-----", "-----",
--, "-----", X"0104", "-1-", "1000", "-----", "-----",
"01010010", "-----", "-----", '0' ),
( "00010", "00000", '0', "-----", X"010f", "-----",
--, "-----", X"0104", "-11", "1010", "-----", X"0105",
"01010010", "-----", "-----", '0' ),
( "-----", "-----", '0', "-----", "-----", "-----",
--, "-----", X"0104", "-00", "1010", "-----", X"0213", "-----",
10", "-----", "-----", '0' )

);

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: DataPath_C
Generic Map(
  data_size => data_size,
  num_registers => num_registers
)
PORT MAP (
  clk => clk,
  rst => rst,
  en => en,

  -- Inputs
  R_A => R_A,
  R_B => R_B,

  W_EN => W_EN,
  W_A => W_A,

  IMM => IMM,
  M_A => M_A,
  M_in => M_in,
  PC => PC,
  S => S,
  AL => AL,
  SH => SH,

  -- Outputs
  PC_plus => PC_plus,
  Flags => Flags,
  M_DA => M_DA,
  M_out => M_out
);

-- Clock process definitions
clk_process :process
begin
  clk <= '0';
  wait for clk_period/2;
  clk <= '1';

```

```

        wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin

    -- hold reset state for 100 ns.
    wait for 100 ns;

    -- enable the system
    rst <= '0';
    en <= '1';
    wait for 2*clk_period;

    -- run the test for every set of data
    for i in test_vectors'range loop

        wait until rising_edge(clk);

        -- assign test inputs
        R_A <= test_vectors(i).R_A;
        R_B <= test_vectors(i).R_B;

        W_EN <= test_vectors(i).W_EN;
        W_A <= test_vectors(i).W_A;

        IMM <= test_vectors(i).IMM;
        M_A <= test_vectors(i).M_A;
        M_in <= test_vectors(i).M_in;
        PC <= test_vectors(i).PC;
        S <= test_vectors(i).S;
        AL <= test_vectors(i).AL;
        SH <= test_vectors(i).SH;

        OEN <= test_vectors(i).OEN;

        wait until falling_edge(clk);

        -- Check to see if the out put was what we were expecting
        -- Have to use std_match() instead of = when comparing meta values like '-'
        assert std_match(test_vectors(i).flags, flags)
        report lf & " [ERR!] Test " & integer'image(i) &
            " Actual flags did not equal expected flags."&
            " Actual [ " & to_bstring(flags) & " ]" &
            " Expected [ " & to_bstring(test_vectors(i).flags) & " ]" & lf
        severity error;

        assert std_match(test_vectors(i).M_out, M_out)
        report lf & " [ERR!] Test " & integer'image(i) &
            " Actual value to memory did not equal expected value to memory."&
            " Actual [ " & u_tostr(M_out) & " ]" &
            " Expected [ " & u_tostr(test_vectors(i).M_out) & " ]" & lf
        severity error;

        assert std_match(M_DA , test_vectors(i).M_DA)
        report lf & " [ERR!] Test " & integer'image(i) &
            " Actual memory address did not equal expected memory address."&
            " Actual [ " & u_tostr(M_DA) & " ]" &
            " Expected [ " & u_tostr(test_vectors(i).M_DA) & " ]" & lf

```



```

severity error;

assert std_match(PC_plus, test_vectors(i).PC_plus)
report lf & " [ERR!] Test " & integer'image(i) &
    " Actual program counter did not equal expected program counter."&
    " Actual [ " & u_tostr(PC_plus) & " ]" &
    " Expected [ " & u_tostr(test_vectors(i).PC_plus) & " ]" & lf
severity error;

-- if there were no isses report that the test was successful
assert not (
    std_match(flags, test_vectors(i).flags) and
    std_match(M_out, test_vectors(i).M_out) and
    std_match(M_DA, test_vectors(i).M_DA) and
    std_match(PC_plus, test_vectors(i).PC_plus)
)
report lf & " [ OK ] Test " & integer'image(i) & " was successful!" & lf
severity note;

end loop;


-- End of test
wait;
end process;

END;

```

Component Simulations


MMU TESTBENCH SIMULATION

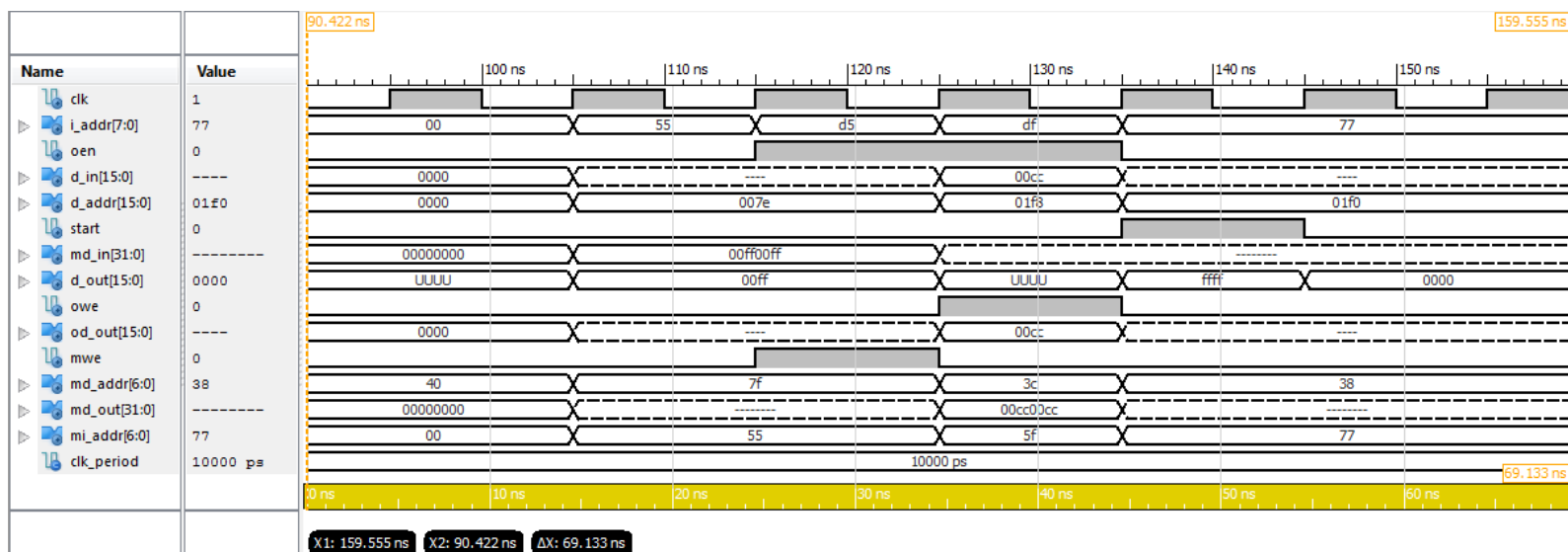

ISIM CONSOLE LOG (MMU TB)

```
ISim P.28xd (signature 0xa0883be4)
This is a Full version of ISim.
Time resolution is 1 ps
WARNING: Simulation object /mmu_tb/test_data was not traceable in the design for the
following reason:
ISim does not yet support tracing of constant and generic multi-dimensional arrays.
Simulator is doing circuit initialization process.
Finished circuit initialization process.
at 110 ns(1): Note:
  [ OK ] Test 0 was successful!
  (/mmu_tb/).
at 120 ns(1): Note:
  [ OK ] Test 1 was successful!
  (/mmu_tb/).
at 130 ns(1): Note:
  [ OK ] Test 2 was successful!
  (/mmu_tb/).
at 140 ns(1): Note:
  [ OK ] Test 3 was successful!
  (/mmu_tb/).
at 150 ns(1): Note:
  [ OK ] Test 4 was successful!
  (/mmu_tb/).
ISim>
```

DECODER TESTBENCH SIMULATION

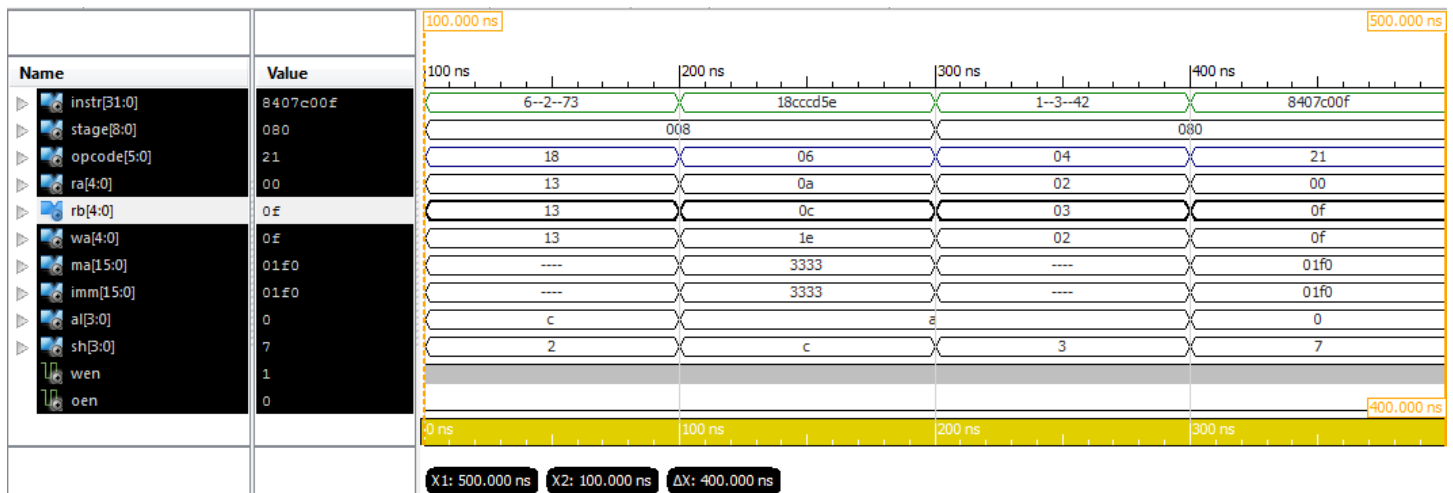


ISIM CONSOLE LOG (DECODER TB)

ISim P.28xd (signature 0xa0883be4)
This is a Full version of ISim.

```
# run 1000 ns
Simulator is doing circuit initialization process.
Finished circuit initialization process.
at 200 ns: Note:
  [ OK ] Test 0 was successful!
  (/decoder_tb/).
at 300 ns: Note:
  [ OK ] Test 1 was successful!
  (/decoder_tb/).
at 400 ns: Note:
  [ OK ] Test 2 was successful!
  (/decoder_tb/).
at 500 ns: Note:
  [ OK ] Test 3 was successful!
  (/decoder_tb/).
ISim>
```

CONTROL-FSM TESTBENCH SIMULATION

 


ISIM CONSOLE LOG (CONTROL FSM TB)

```
ISim P.28xd (signature 0xa0883be4)
This is a Full version of ISim.
Time resolution is 1 ps
WARNING: Simulation object /controlfsm_tb/test_data was not traceable in the design for
the following reason:
ISim does not yet support tracing of constant and generic multi-dimensional arrays.
Simulator is doing circuit initialization process.
Finished circuit initialization process.
at 120 ns(1): Note:
  [ OK ] Test 0 was successful!
  (/controlfsm_tb/).
at 130 ns(1): Note:
  [ OK ] Test 1 was successful!
  (/controlfsm_tb/).
at 140 ns(1): Note:
  [ OK ] Test 2 was successful!
  (/controlfsm_tb/).
```

```
at 150 ns(1): Note:
[ OK ] Test 3 was successful!
(/controlfsm_tb/).
at 160 ns(1): Note:
[ OK ] Test 4 was successful!
(/controlfsm_tb/).
at 170 ns(1): Note:
[ OK ] Test 5 was successful!
(/controlfsm_tb/).
at 180 ns(1): Note:
[ OK ] Test 6 was successful!
(/controlfsm_tb/).
at 190 ns(1): Note:
[ OK ] Test 7 was successful!
(/controlfsm_tb/).
at 200 ns(1): Note:
[ OK ] Test 8 was successful!
(/controlfsm_tb/).
at 210 ns(1): Note:
[ OK ] Test 9 was successful!
(/controlfsm_tb/).
at 220 ns(1): Note:
[ OK ] Test 10 was successful!
(/controlfsm_tb/).
at 230 ns(1): Note:
[ OK ] Test 11 was successful!
(/controlfsm_tb/).
at 240 ns(1): Note:
[ OK ] Test 12 was successful!
(/controlfsm_tb/).
at 250 ns(1): Note:
[ OK ] Test 13 was successful!
(/controlfsm_tb/).
at 260 ns(1): Note:
[ OK ] Test 14 was successful!
(/controlfsm_tb/).
at 270 ns(1): Note:
[ OK ] Test 15 was successful!
(/controlfsm_tb/).
at 280 ns(1): Note:
[ OK ] Test 16 was successful!
(/controlfsm_tb/).
ISim>
```

DUAL PORT MEMORY TESTBENCH SIMULATION

 


ISIM CONSOLE LOG (DUAL PORT MEMORY TB)

ISim P.28xd (signature 0xa0883be4)
This is a Full version of ISim.

```
# run 1000 ns
Simulator is doing circuit initialization process.
Finished circuit initialization process.
at 210 ns: Note:
Works (/dualportmemorytb/).
at 230 ns: Note:
Works (/dualportmemorytb/).
ISim>
```

OUTPUT REG TESTBENCH SIMULATION

 



ISIM CONSOLE LOG (OUTPUT REG TB)

ISim P.28xd (signature 0xa0883be4)
This is a Full version of ISim.

```
# run 1000 ns
Simulator is doing circuit initialization process.
Finished circuit initialization process.
at 210 ns: Note:
DATA IN/DATA OUT WORKS (/outputregtb/).
at 220 ns: Note:
WE Works (/outputregtb/).
ISim>
```


Top Level Processor Testing

SIMPLE BRANCH PROGRAM

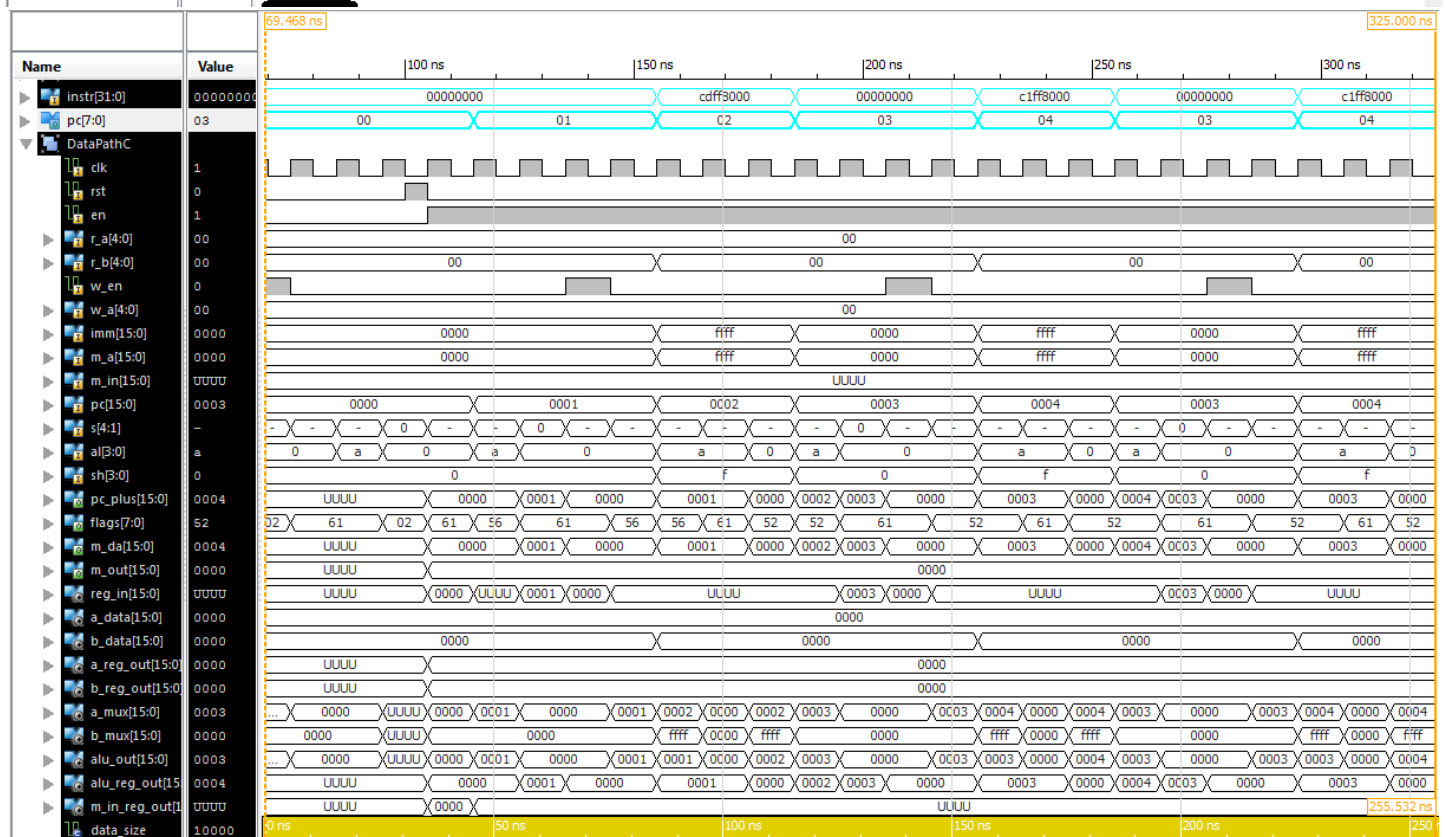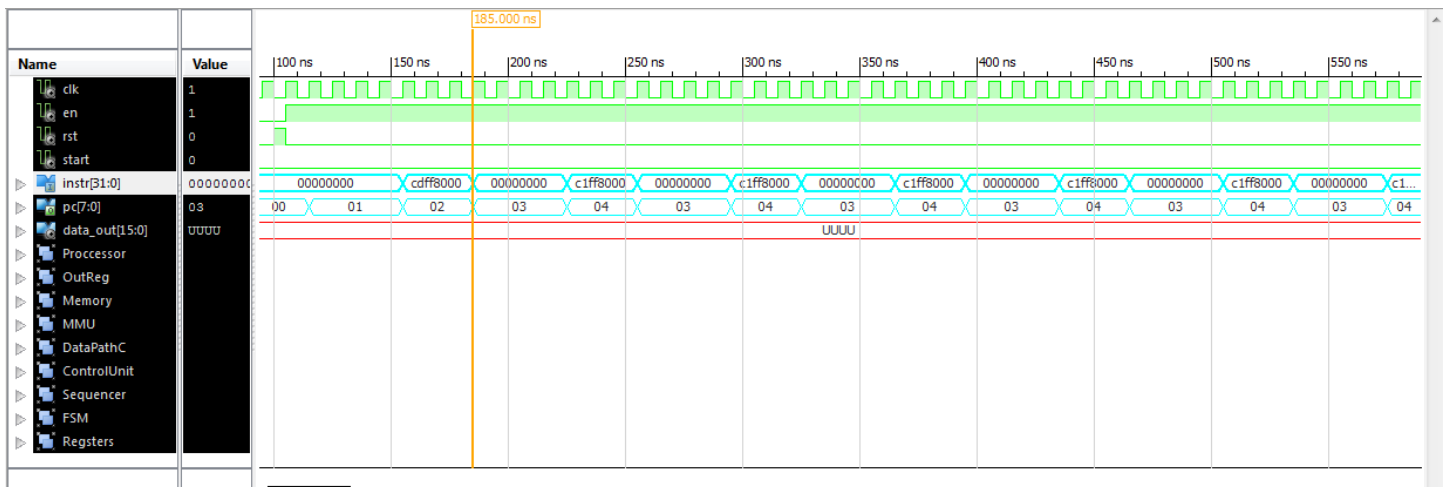

```
-- simple branches test program
00000000
00000000
CDFF8000
00000000
C1FF8000
```


Simple 'And' Program (Processor TB)

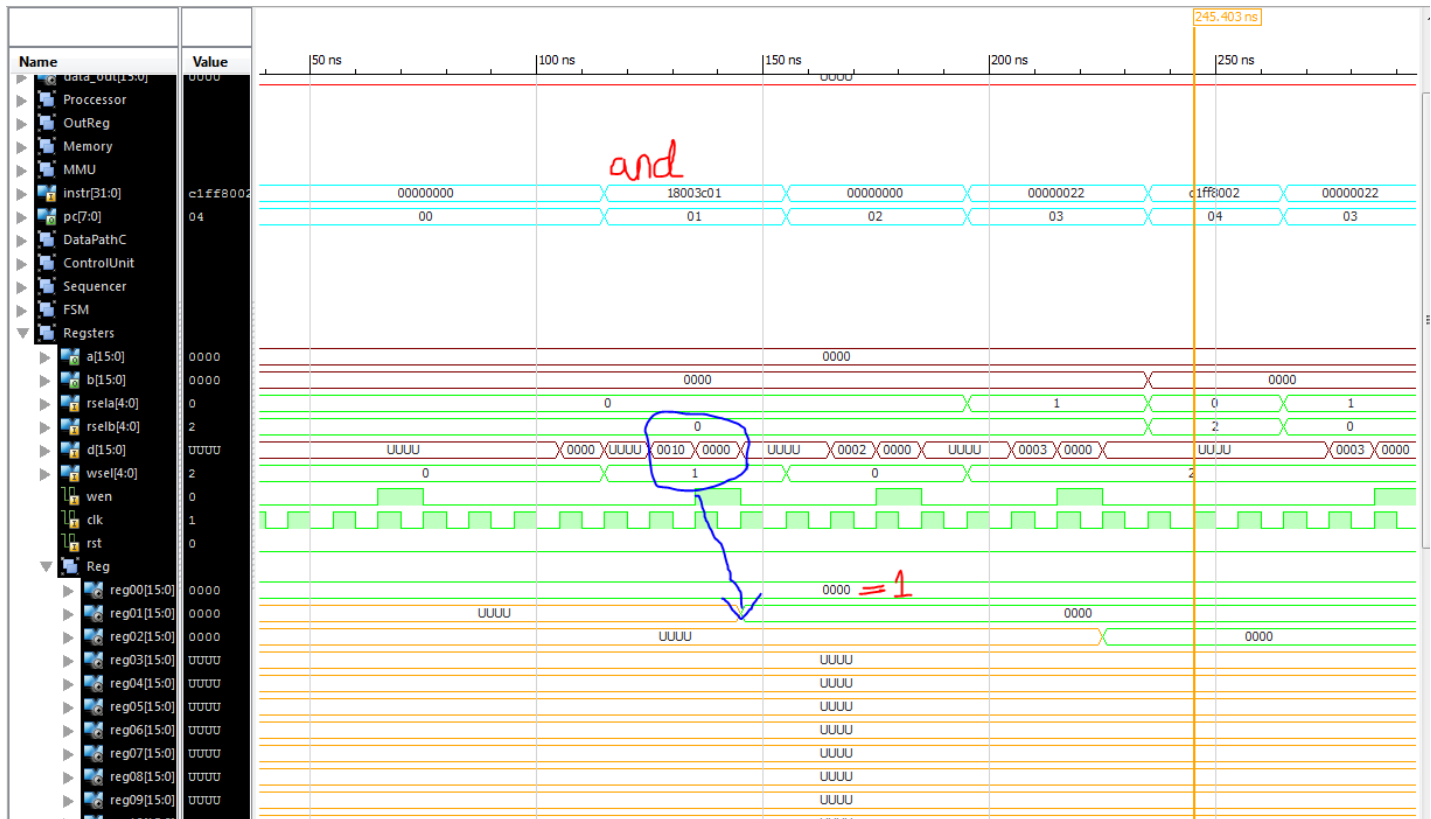

```
-- simple adds test program
00000000
18003C01
00000000
00000022
C1FF8002
```

In the simulation above you can see the output of the data bus, “0010” is not being written into register one as we would expect. Instead, the value at Register 1 is equal to 0. The problem we are having in this test is probably the same as the one we are having in our full program simulation, as both times the registers get set to 0.

Full Program (Processor TB)

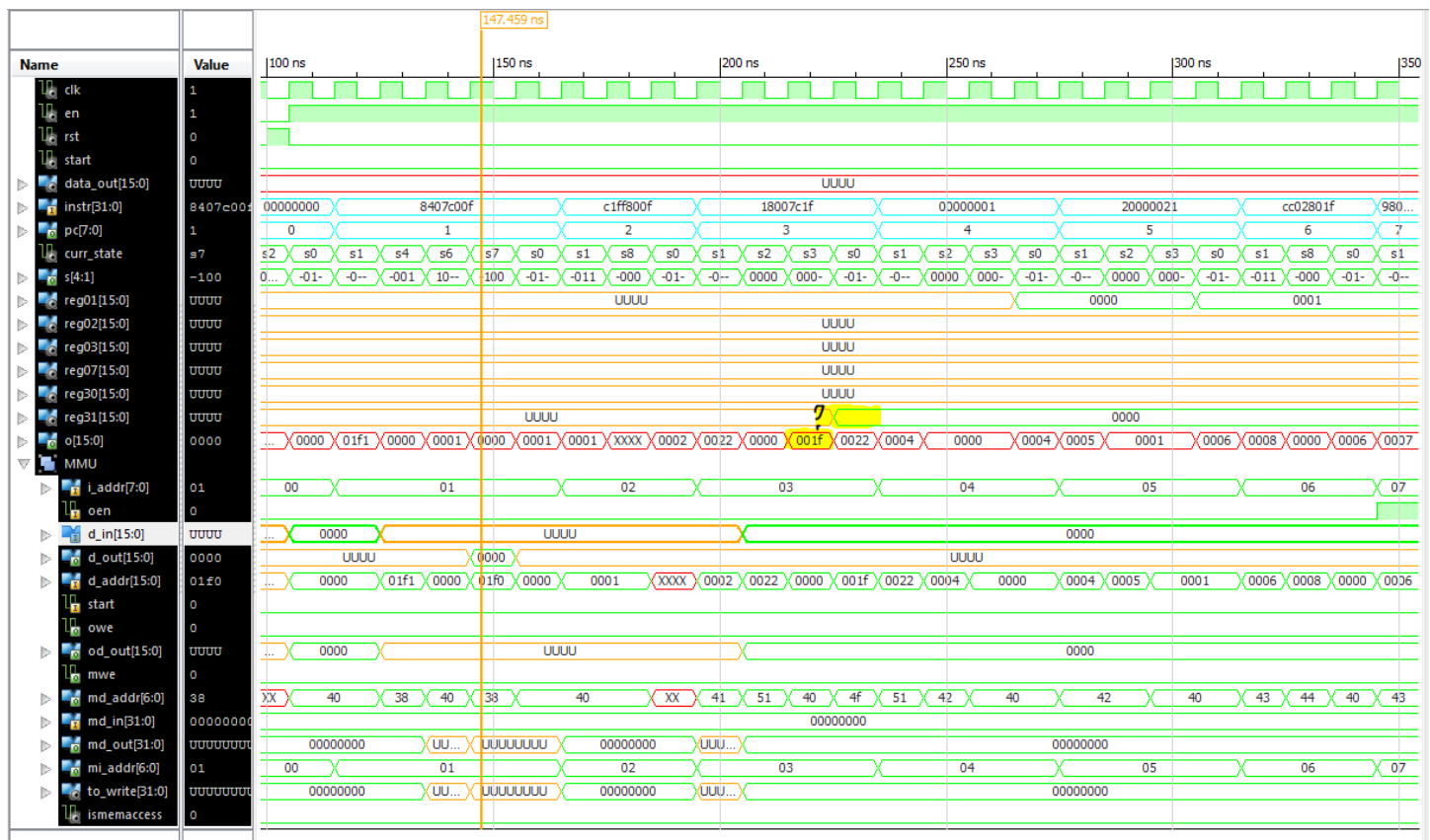

As highlighted in the simulation above, we encountered a bug in our implementation that stopped our processor from writing anything but zeros to memory. We tried isolating this into a simple test case, which is where the two simple programs above came from. After spending a lot of time trying to fix this, we were not able to find the solution. We believe that this is caused by a timing issue with the signal 'S'. We are expecting the value of 31 (01F) to be written to memory but instead we get zero. The value of 31 makes it all the way to the data input of the register banks. At some point we were able to get 31 written to memory but it was overridden by 0000 on the next clock cycle.

HDL Synthesis

* HDL Synthesis *

Synthesizing Unit <Processor>.

```
Related source file is "E:\University\Second Year\Computer Architectures\assesment\MyMicroProcessor\Project\Project\Processor.vhd".  
WARNING:Xst:2935 - Signal 'PC_16<15:8>', unconnected in block 'Processor', is tied to its initial value (00000000).
```

Summary:

no macro.

Unit <Processor> synthesized.

```
Synthesizing Unit <OutputReg>.
```

Related source file is "E:\University_Second Year\Computer Architectures\assesment\MyMicroProccessor\Project\Project\OutputReg.vhd".
Found 16-bit register for signal <data_out>.

Summary:

inferred 16 D-type flip-flop(s).

Unit <OutputReg> synthesized.

Synthesizing Unit <DualPortMemory>.

Related source file is "E:\University_Second Year\Computer Architectures\assesment\MyMicroProccessor\Project\Project\DualPortMemory.vhd".
Found 128x32-bit dual-port RAM <Mram_ram> for signal <ram>.

Summary:

inferred 1 RAM(s).

Unit <DualPortMemory> synthesized.

Synthesizing Unit <MMU>.

Related source file is "E:\University_Second Year\Computer Architectures\assesment\MyMicroProccessor\Project\Project\MMU.vhd".
WARNING:Xst:647 - Input <I_addr<7:7>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.

Found 7-bit adder for signal <mD_addr> created at line 70.

Found 16-bit comparator lessequal for signal <n0000> created at line 42

Found 16-bit comparator greater for signal <D_addr[15]_GND_7_o_LessThan_2_o> created at line 42

Summary:

inferred 1 Adder/Subtractor(s).

inferred 2 Comparator(s).

inferred 3 Multiplexer(s).

Unit <MMU> synthesized.

Synthesizing Unit <DataPath_C>.

Related source file is "E:\University_Second Year\Computer Architectures\assesment\MyMicroProccessor\Project\Project\DataPath_C.vhd".

data_size = 16

num_registers = 32

Summary:

inferred 4 Multiplexer(s).

Unit <DataPath_C> synthesized.

Synthesizing Unit <Reg>.

Related source file is "E:\University_Second Year\Computer Architectures\assesment\MyMicroProccessor\Project\Project\Reg.vhd".

data_size = 16

Found 16-bit register for signal <data_out>.

Summary:

inferred 16 D-type flip-flop(s).

Unit <Reg> synthesized.

Synthesizing Unit <ALU_param>.

Related source file is "E:\University_Second Year\Computer Architectures\assesment\MyMicroProccessor\Project\Project\ALU_param.vhd".

N = 16

Found 16-bit adder for signal <A_itr[15]_B_itr[15]_add_27_OUT> created at line 69.

Found 16-bit adder for signal <A_itr[15]_GND_11_o_add_31_OUT> created at line 1253.

Found 16-bit subtractor for signal <A_itr[15]_B_itr[15]_sub_26_OUT<15:0>> created at line 70.

Found 16-bit subtractor for signal <A_itr[15]_GND_11_o_sub_30_OUT<15:0>> created at line 1320.

Found 16-bit shifter rotate right for signal <A_itr[15]_X_itr[30]_rotate_right_17_OUT> created at line 3021

Found 16-bit shifter rotate left for signal <A_itr[15]_X_itr[30]_rotate_left_19_OUT> created at line 3012

Found 16-bit shifter arithmetic right for signal <A_itr[15]_X_itr[30]_shift_right_21_OUT> created at line 2982

Found 16-bit shifter logical left for signal <A_itr[15]_X_itr[30]_shift_left_23_OUT> created at line 2973

Found 16-bit 13-to-1 multiplexer for signal <O_itr> created at line 42.

Found 16-bit comparator greater for signal <flags<3>> created at line 99

Found 16-bit comparator greater for signal <flags<4>> created at line 100

Summary:

inferred 1 Adder/Subtractor(s).

inferred 2 Comparator(s).

inferred 16 Multiplexer(s).

inferred 4 Combinational logic shifter(s).

Unit <ALU_param> synthesized.

Synthesizing Unit <regbank>.

Related source file is "E:\University\Second Year\Computer Architectures\assessment\MyMicroProcessor\Project\Project\otherRegBank.vhd".

Found 16-bit register for signal <REG02>.

Found 16-bit register for signal <REG03>.

Found 16-bit register for signal <REG04>.

Found 16-bit register for signal <REG05>.

Found 16-bit register for signal <REG06>.

Found 16-bit register for signal <REG07>.

Found 16-bit register for signal <REG08>.

Found 16-bit register for signal <REG09>.

Found 16-bit register for signal <REG10>.

Found 16-bit register for signal <REG11>.

Found 16-bit register for signal <REG12>.

Found 16-bit register for signal <REG13>.

Found 16-bit register for signal <REG14>.

Found 16-bit register for signal <REG15>.

Found 16-bit register for signal <REG16>.

Found 16-bit register for signal <REG17>.

Found 16-bit register for signal <REG18>.

Found 16-bit register for signal <REG19>.

Found 16-bit register for signal <REG20>.

Found 16-bit register for signal <REG21>.

Found 16-bit register for signal <REG22>.

Found 16-bit register for signal <REG23>.

Found 16-bit register for signal <REG24>.

Found 16-bit register for signal <REG25>.

Found 16-bit register for signal <REG26>.

Found 16-bit register for signal <REG27>.

Found 16-bit register for signal <REG28>.

Found 16-bit register for signal <REG29>.

Found 16-bit register for signal <REG30>.

Found 16-bit register for signal <REG31>.

Found 16-bit register for signal <REG01>.

Found 16-bit 32-to-1 multiplexer for signal <A> created at line 30.

Found 16-bit 32-to-1 multiplexer for signal created at line 31.

```

Summary:
    inferred 496 D-type flip-flop(s).
    inferred 2 Multiplexer(s).
Unit <regbank> synthesized.

```

```

Synthesizing Unit <ControlUnit>.
Related source file is "E:\University\Second Year\Computer
Architectures\assesment\MyMicroProcessor\Project\Project\ControlUnit.vhd".

```

```

Summary:
    no macro.
Unit <ControlUnit> synthesized.

```

```

Synthesizing Unit <ControlFSM>.
Related source file is "E:\University\Second Year\Computer
Architectures\assesment\MyMicroProcessor\Project\Project\ControlFSM.vhd".

```

```

Found 4-bit register for signal <curr_state>.
Found finite state machine <FSM_0> for signal <curr_state>.

```

States	9	
Transitions	12	
Inputs	3	
Outputs	10	
Clock	clk (rising_edge)	
Reset	rst (positive)	
Reset type	synchronous	
Reset State	s0	
Power Up State	s0	
Encoding	auto	
Implementation	LUT	

```

Summary:
    inferred 4 Multiplexer(s).
    inferred 1 Finite State Machine(s).
Unit <ControlFSM> synthesized.

```

```

Synthesizing Unit <Sequencer>.
Related source file is "E:\University\Second Year\Computer
Architectures\assesment\MyMicroProcessor\Project\Project\Sequencer.vhd".

```

```

WARNING:Xst:647 - Input <STAGE<7:1>> is never used. This port will be preserved and
left unconnected if it belongs to a top-level block or it belongs to a sub-block and
the hierarchy of this sub-block is preserved.

```

```

WARNING:Xst:647 - Input <instr<25:0>> is never used. This port will be preserved and
left unconnected if it belongs to a top-level block or it belongs to a sub-block and
the hierarchy of this sub-block is preserved.

```

```

WARNING:Xst:647 - Input <flags<7:7>> is never used. This port will be preserved and
left unconnected if it belongs to a top-level block or it belongs to a sub-block and
the hierarchy of this sub-block is preserved.

```

```

Found 8-bit register for signal <PC_next>.

```

```

Found 1-bit register for signal <cond_met_i>.

```

```

Found 8-bit register for signal <PC_internal>.

```

```

Found 8-bit adder for signal <PC_internal[7]_GND_46_o_add_13_OUT> created at line
1241.

```

```

Summary:
    inferred 1 Adder/Subtractor(s).
    inferred 17 D-type flip-flop(s).
    inferred 7 Multiplexer(s).
Unit <Sequencer> synthesized.

```

Synthesizing Unit <Decoder_Block>.

Related source file is "E:\University\Second Year\Computer Architectures\assesment\MyMicroProccessor\Project\Project\Decoder.vhd".

WARNING:Xst:647 - Input <STAGE<0:0>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.

WARNING:Xst:647 - Input <STAGE<2:2>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.

WARNING:Xst:647 - Input <STAGE<6:4>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.

Summary:

inferred 17 Multiplexer(s).

Unit <Decoder_Block> synthesized.

=====

HDL Synthesis Report

Macro Statistics

# RAMs	: 1
128x32-bit dual-port RAM	: 1
# Adders/Subtractors	: 3
16-bit addsub	: 1
7-bit adder	: 1
8-bit adder	: 1
# Registers	: 39
1-bit register	: 1
16-bit register	: 36
8-bit register	: 2
# Comparators	: 4
16-bit comparator greater	: 3
16-bit comparator lessequal	: 1
# Multiplexers	: 53
1-bit 2-to-1 multiplexer	: 17
16-bit 2-to-1 multiplexer	: 18
16-bit 32-to-1 multiplexer	: 2
32-bit 2-to-1 multiplexer	: 1
4-bit 2-to-1 multiplexer	: 13
5-bit 2-to-1 multiplexer	: 1
8-bit 2-to-1 multiplexer	: 1
# Logic shifters	: 4
16-bit shifter arithmetic right	: 1
16-bit shifter logical left	: 1
16-bit shifter rotate left	: 1
16-bit shifter rotate right	: 1
# FSMs	: 1
# Xors	: 1
16-bit xor2	: 1

Synthesis Warnings

```
WARNING:HDLCompiler:634 - "E:\University\_Second Year\Computer Architectures\assesment\MyMicroProccessor\Project\Project\Proccessor.vhd" Line 62: Net <PC_16[15]> does not have a driver.
WARNING:Xst:2935 - Signal 'PC_16<15:8>', unconnected in block 'Processor', is tied to its initial value (00000000).
WARNING:Xst:647 - Input <I_addr<7:7>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.
WARNING:Xst:647 - Input <STAGE<7:1>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.
WARNING:Xst:647 - Input <instr<25:0>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.
WARNING:Xst:647 - Input <flags<7:7>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.
WARNING:Xst:647 - Input <STAGE<0:0>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.
WARNING:Xst:647 - Input <STAGE<2:2>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.
WARNING:Xst:647 - Input <STAGE<6:4>> is never used. This port will be preserved and left unconnected if it belongs to a top-level block or it belongs to a sub-block and the hierarchy of this sub-block is preserved.
```

UCF File

```
# PlanAhead Generated physical constraints
```

```
NET "data_out[15]" LOC = N12;
NET "data_out[14]" LOC = P16;
NET "data_out[13]" LOC = D4;
NET "data_out[12]" LOC = M13;
NET "data_out[11]" LOC = L14;
NET "data_out[10]" LOC = N14;
NET "data_out[9]" LOC = M14;
NET "data_out[8]" LOC = U18;
NET "clk" LOC = L15;
NET "en" LOC = T15;
NET "rst" LOC = P3;
NET "start" LOC = F6;
```